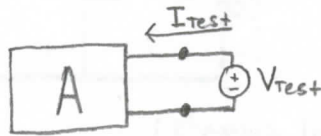



## Thenevin Equivilant



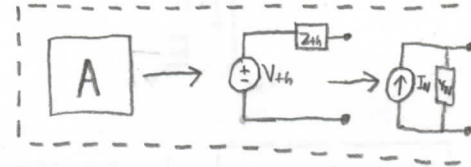
### How to Calculate $Z_{th}$ :

- ① Connect Test voltage  $V_{Test}$  (1 V)
- ② Calculate  $I_{Test}$

$$\therefore Z_{th} = \frac{V_{Test}}{I_{Test}}$$



## Norton Equivilant

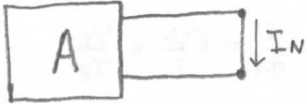


### How to Calculate $Y_N$ :

- ① Connect Test Current  $I_{Test}$  (1 A)
- ② Calculate  $V_{Test}$

$$\textcircled{3} Y_N = \frac{I_{Test}}{V_{Test}}$$

## Millers Theorem

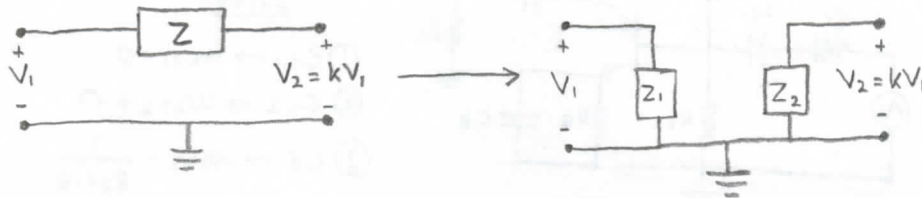


### Where:

$$Z_1 = \frac{Z}{1-k}$$

$$Z_2 = \frac{Z}{1-1/k}$$

## Circuit Behaviour

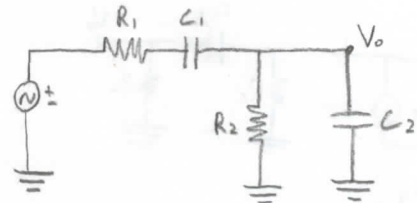

## Frequency Response

$$T(s) = \underbrace{A_M}_{\text{MidBand}} \cdot \underbrace{F_L(s)}_{\text{Low Freq Response}} \cdot \underbrace{F_H(s)}_{\text{High Freq Response}}$$

$$F_L(s) = \frac{(s + \omega_{z1L})(s + \omega_{z2L}) \dots (s + \omega_{znL})}{(s + \omega_{p1L})(s + \omega_{p2L}) \dots (s + \omega_{pnL})}$$

$$F_H(s) = \frac{(1 + \frac{s}{\omega_{z1H}})(1 + \frac{s}{\omega_{z2H}}) \dots (1 + \frac{s}{\omega_{znH}})}{(1 + \frac{s}{\omega_{p1H}})(1 + \frac{s}{\omega_{p2H}}) \dots (1 + \frac{s}{\omega_{pnH}})}$$

### ① At DC ( $\omega=0$ ):

$C_1, C_2$  are open,  $V_o = 0$   $C_1 \gg C_2$

### ② At low frequency:

$C_1$  is conducting,  $C_2$  is open  
 $\therefore V_o = \text{Some Value}$

### ③ At high frequency:


$C_1$  is shorted,  $C_2$  is conducting  
 $\therefore V_o = \text{Some Value}$

### ④ At $\omega \rightarrow \infty$ :

$C_1, C_2$  are shorted,  $V_o = 0$

### BAND-PASS
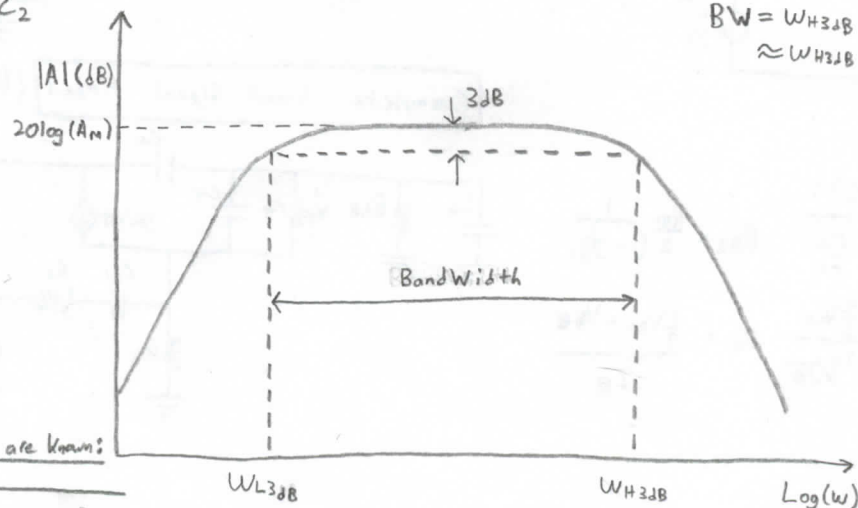
## Magnitude Response (Generic Band-Pass Filter)



$$BW = \omega_{H3dB} - \omega_{L3dB}$$

$$\approx \omega_{H3dB} \text{ [for } \omega_{H3dB} \gg \omega_{L3dB}]$$


## Finding Cut-off Frequencies

### ① If locations of poles and Zeros are known:

$$\omega_{L3dB} = \sqrt{\omega_{p1L}^2 + \omega_{p2L}^2 \dots - 2\omega_{z1L}^2 - 2\omega_{z2L}^2 \dots}$$

$$\omega_{H3dB} = \sqrt{\left(\frac{1}{\omega_{p1H}}\right)^2 + \left(\frac{1}{\omega_{p2H}}\right)^2 \dots - 2\left(\frac{1}{\omega_{z1H}}\right)^2 - 2\left(\frac{1}{\omega_{z2H}}\right)^2}$$

# NPN BJT Transistor

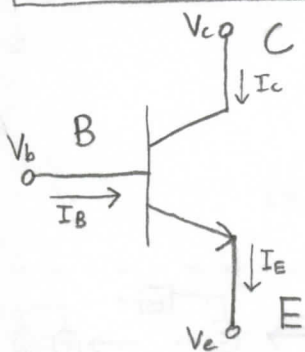

Collector Current:


$$I_C = \alpha I_E$$

$$I_C = \beta I_B$$

$$I_C = I_{Se}^{V_{BE}/V_T}$$

$$\alpha = \frac{\beta}{\beta + 1}$$

## Complete Small Signal Model

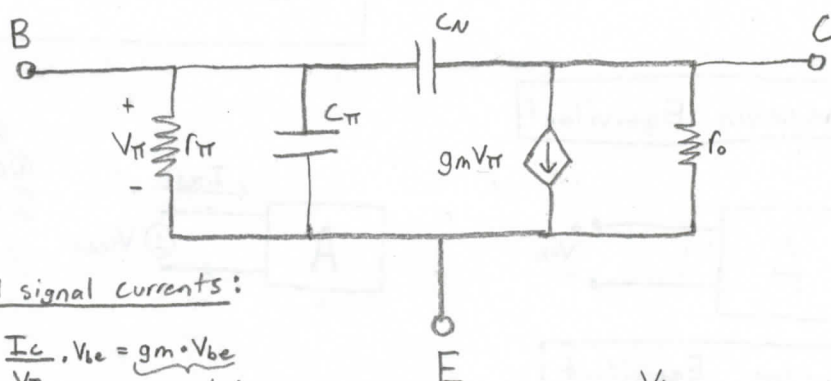

Small signal currents:

$$i_c = \frac{I_C}{V_T} \cdot V_{be} = g_m \cdot V_{be}$$


transconductance

$$i_b = \frac{g_m}{\beta} \cdot V_{be}$$

$$r_o \approx \frac{V_A}{I_C}$$

$$r_{\pi} = \frac{V_{be}}{i_b} = \frac{\beta}{g_m} = \frac{\beta V_T}{I_C} = \frac{V_T}{I_B}$$

## Bias Circuit

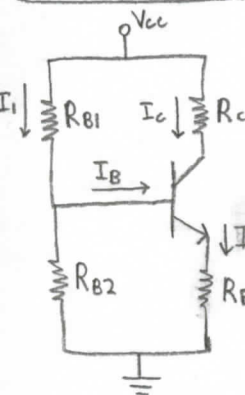

1/3 Rule (Version 2):

$$① V_C = \frac{2}{3} V_{CC}$$

$$② V_E = \frac{1}{3} V_{CC}$$

$$③ I_1 = \frac{I_E}{\beta}$$

Resistor Values:


$$① R_C = \frac{1}{3} \frac{V_{CC}}{I_C} \approx R_E$$

$$② R_{B1} = \frac{\frac{2}{3} V_{CC} - V_{BE}}{I_E / \beta}$$

$$③ R_{B2} = \frac{\frac{1}{3} V_{CC} + V_{BE}}{I_E / \beta - I_B}$$

$$V_{BE} = 0.7V$$

## Common Base Amplifier

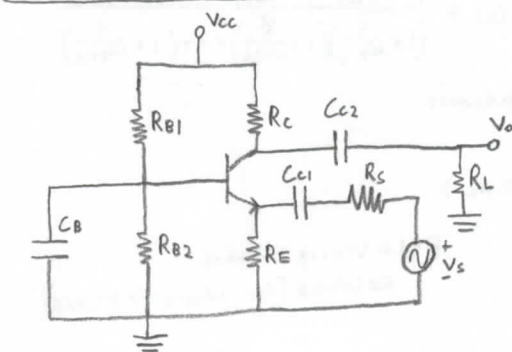

1/3 Rule (Version 1):

$$① V_B = \frac{1}{3} V_{CC} \quad R_C = \frac{1}{3} \frac{V_{CC}}{I_C} \quad R_{B2} = \frac{R_{B1}}{2} \left( 1 - \frac{1}{\beta} \right)$$

$$② V_C = \frac{2}{3} V_{CC} \quad R_{B1} = \frac{\frac{2}{3} V_{CC}}{I_E / \beta} \quad R_E = \frac{\frac{1}{3} V_{CC} - V_{BE}}{I_E}$$


$$③ I_1 = \frac{I_E}{\beta}$$

Useful:

$$g_m = \frac{I_C}{V_T}$$

$$r_{\pi} = \frac{\beta}{g_m}$$


## Common Emitter Amplifier

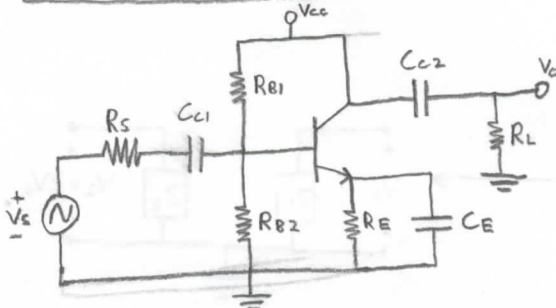

Zeros:


- ①  $C_{C1} \rightarrow \omega_{LZ1} = 0$
- ②  $C_{C2} \rightarrow \omega_{LZ2} = 0$
- ③  $C_E \rightarrow \omega_{LZ3} = \frac{1}{R_E C_E}$

## Complete Small Signal Model (Emitter)

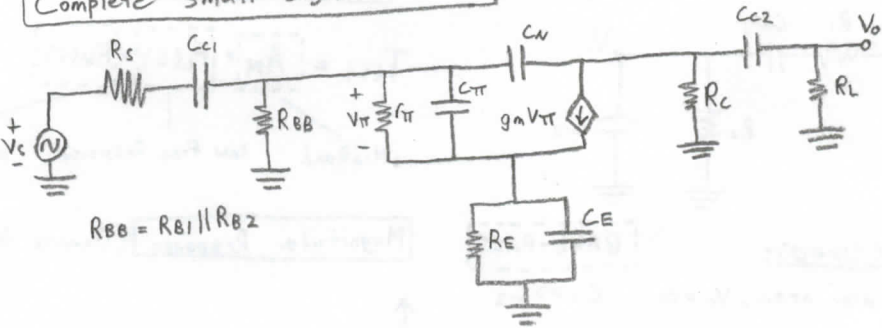

$$R_{BB} = R_{B1} \parallel R_{B2}$$


## Complete Small Signal Model (Base)

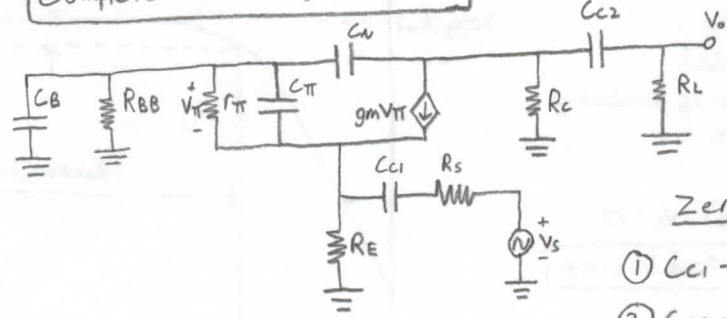

Zeros:

- ①  $C_{C1} \rightarrow \omega_{LZ1} = 0$
- ②  $C_{C2} \rightarrow \omega_{LZ2} = 0$
- ③  $C_B \rightarrow \omega_{LZ3} = \frac{1}{R_{BB} C_B}$


# Cascode Amplifier

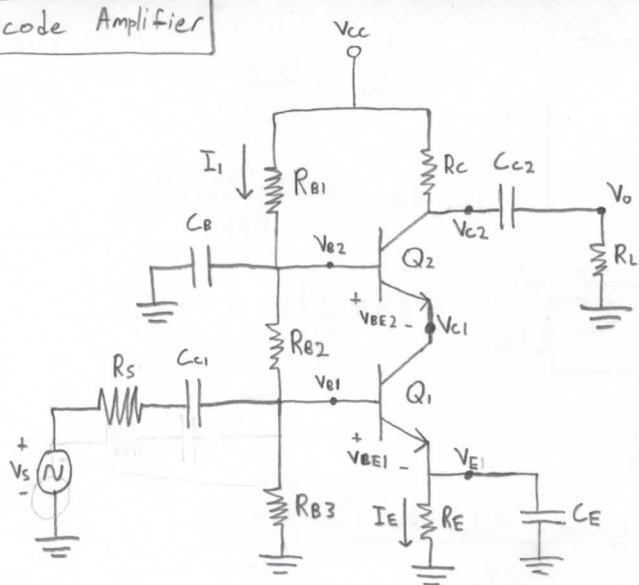

## 1/4 Rule Biasing:


- ①  $V_{C2} = 3/4 V_{CC}$
- ②  $V_{C1} = 1/2 V_{CC}$
- ③  $V_E = 1/4 V_{CC}$
- ④  $I_1 = 0.1 I_E$

## Small signal Model at Mid Band:

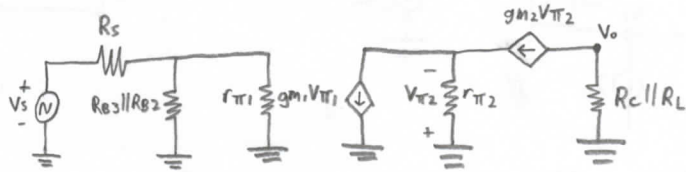

$$A_M = -g_{m2}(R_C || R_L) \cdot \frac{R_{B3} || R_{B2} || r_{\pi 1}}{R_S + R_{B3} || R_{B2} || r_{\pi 1}}$$

## Small signal model at High FREQ:

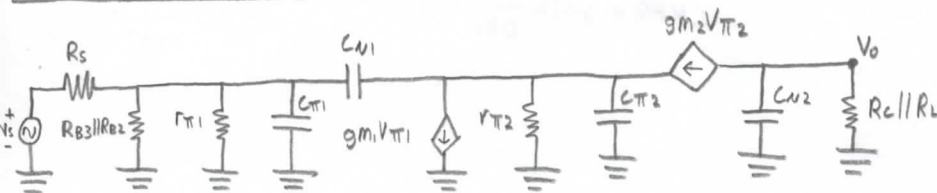


$$W_{HP1} = \frac{1}{[R_S || R_{B2} || R_{B3} || r_{\pi 1}](C_{\pi 1} + 2C_{N1})}$$


$$W_{HP2} = \frac{1}{\left(\frac{r_{\pi 2}}{1 + \beta_2}\right)(C_{\pi 2} + 2C_{N1})}$$

$$W_{HP3} = \frac{1}{(R_C || R_L)(C_{N2})}$$

## Common Collector Amplifier

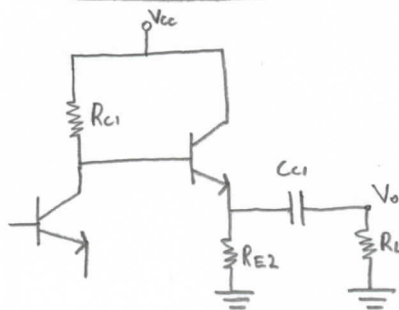


## Small signal model at Mid Band:

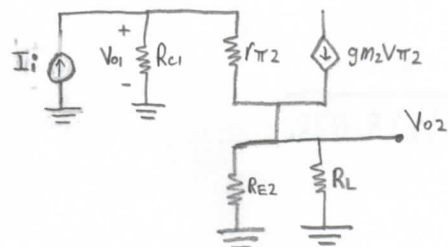

$$R_o = R_{E2} || \frac{r_{\pi 2} + R_{C1}}{1 + \beta_2}$$

$$\frac{i_{e2}}{I_i} = \frac{R_{C1}}{R_{E2} || R_L}$$

## Small signal model at high FREQ:

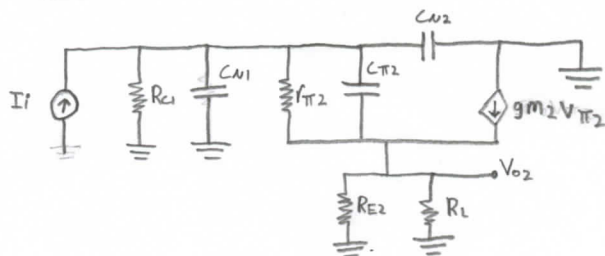


$$W_{HP1} = \frac{1}{R_{C1}(C_{N1} + C_{N2})}$$

$$W_{HP2} = \frac{1 + \beta_2}{r_{\pi 2} C_{\pi 2}} \quad \left. \begin{array}{l} \text{Pole-zero} \\ \text{Cancellation} \end{array} \right\}$$

$$W_{ZH} = \frac{1 + \beta_2}{r_{\pi 2} C_{\pi 2}}$$

## Differential Amplifier

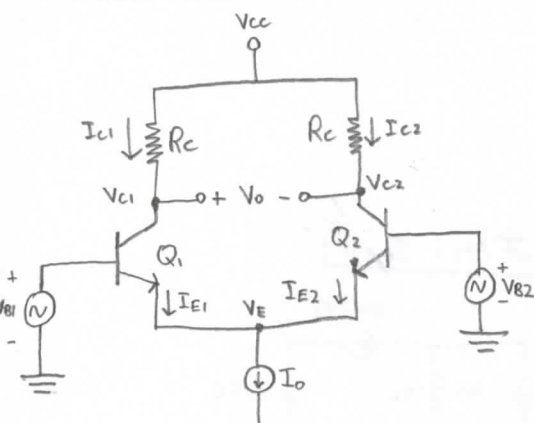


$$A_M = -g_m R_c \left[ \frac{2r_\pi}{2r_\pi + R_s} \right] \left[ \frac{R_L}{R_L + 2R_c} \right]$$

$$k = -g_m R_c \cdot \frac{R_L}{R_L + 2R_c}$$

$$W_{HP1} = \frac{1}{\left[ \frac{C_\pi}{2} + \frac{C_u}{2}(1-k) \right] 2r_\pi \parallel R_s}$$

$$W_{HP2} = \frac{1}{\frac{C_u}{2} \left( 1 - \frac{1}{k} \right) R_L \parallel 2R_c}$$

## Current Mirror

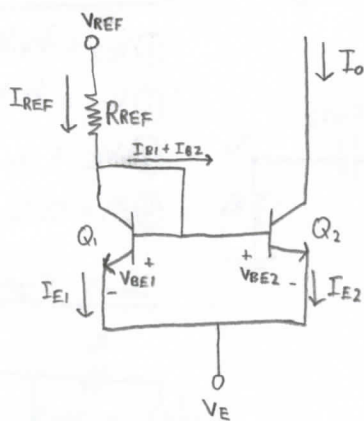

$$I_o = \frac{I_{REF}}{1 + 2/\beta}$$

$$I_{REF} = \frac{V_{REF} - (V_E + V_{BE1})}{R_{REF}}$$

$$g_m = \frac{\alpha I_o}{2V_T}$$

Common Mode Rejection Ratio:

$$A_{cm} = \frac{\Delta R_c}{2R}$$

$$CMRR = g_m 2R \frac{R_c}{\Delta R_c}$$

### Useful information.

$$i_C = I_C + i_c$$

$$I_C = \alpha I_E$$

$$I_C = \beta I_B$$

$$I_C = I_S e^{\frac{V_{BE}}{V_T}}$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$v_{BE} = V_{BE} + v_{be}$$

$$i_C = I_S e^{\frac{v_{BE}}{V_T}} = I_S e^{\frac{V_{BE}}{V_T}} e^{\frac{v_{be}}{V_T}} = I_C e^{\frac{v_{be}}{V_T}}$$

$$i_C \approx I_C + \frac{I_C}{V_T} v_{be}$$

$$i_c = \frac{I_C}{V_T} v_{be} = g_m v_{be}$$

$$g_m = \left. \frac{\partial i_C}{\partial v_{BE}} \right|_{i_C = I_C}$$

$$i_B = I_B + i_b = \frac{i_C}{\beta} = \frac{I_C}{\beta} + \frac{i_c}{\beta} = \frac{I_C}{\beta} + \frac{g_m}{\beta} v_{be}$$

$$i_b = \frac{g_m}{\beta} v_{be}$$


$$r_\pi \equiv \frac{v_{be}}{i_b}$$

$$r_\pi = \frac{v_{be}}{i_b} = \frac{\beta}{g_m} = \beta \frac{V_T}{I_C} = \frac{\beta V_T}{\beta I_B} = \frac{V_T}{I_B}$$

$$C \equiv \frac{dQ}{dV}$$

$$r_o = \left[ \left. \frac{\partial i_C}{\partial v_{CE}} \right|_{v_{BE} = \text{constant}} \right]^{-1}$$

$$r_o \approx \frac{V_A}{I_C}$$

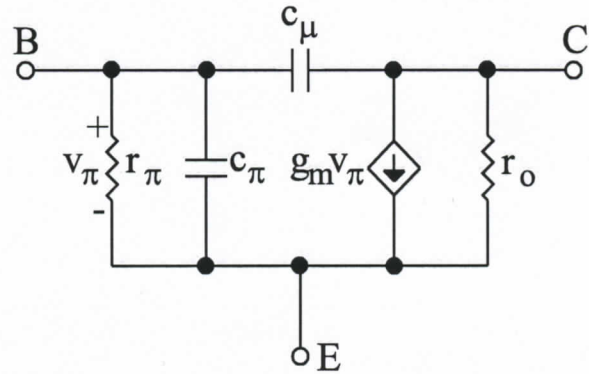

Small-Signal Model

$$A_f = \frac{A}{1 + A\beta}$$

h-parameters

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

y-parameters

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

z-parameters

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

g-parameters

$$I_1 = g_{11} V_1 + g_{12} I_2$$

$$V_2 = g_{21} V_1 + g_{22} I_2$$