
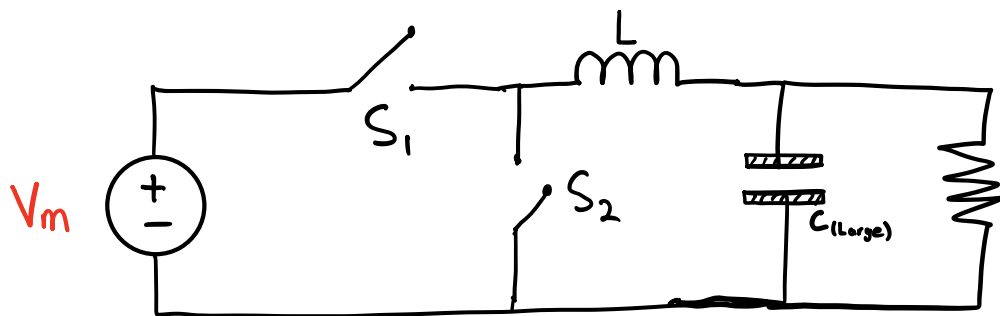



Buck Converter:

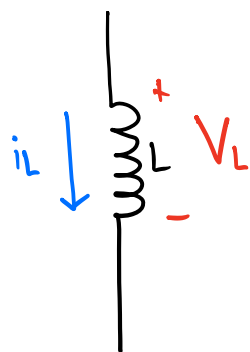

— S1 and S2 complementary, not on at the same time


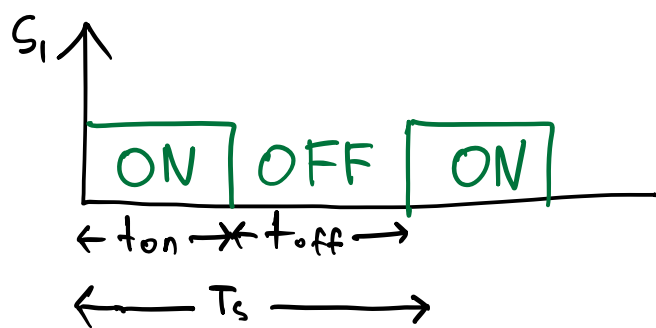
$$i_L = \frac{1}{L} \int V_L dt \rightarrow i_L(t) = \frac{V_L(t)}{L} + \overset{\text{Initial Conditions}}{i_L(0)}$$



Duty Cycle:

$$D = t_{on} / T_s$$

$$V_o(D) = V_{in} \cdot D$$

