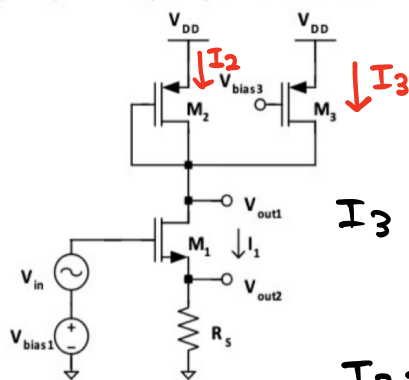


1. In the following circuit assume that all transistors are operating in the saturation region. Also, assume that $\lambda=\gamma=0$, $V_{DD}=3V$, $V_{bias3}=1.9V$, $V_{TH(NMOS)}=0.5V$, $V_{TH(PMOS)}=-0.6V$, $\mu_n C_{ox}=200 \mu A/V^2$, $(W/L)_1=40$, $\mu_p C_{ox}=100 \mu A/V^2$, $(W/L)_2=40$, $(W/L)_3=40$, and $R_S=50\Omega$.



$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$I_3 = \frac{1}{2} \cdot (100 \times 10^{-6}) \cdot 40 \cdot (1.9 - 3 + 0.6)^2 = 0.5mA$$

$$I_2 + I_3 = I_1$$

$$\therefore I_2 = 0.5mA$$

- Find V_{bias1} such that the bias current of M_1 is $I_1=1mA$.
- Calculate the small-signal voltage gain $A_{V1}=V_{out1}/V_{in}$.
- Calculate the small-signal voltage gain $A_{V2}=V_{out2}/V_{in}$.
- Calculate the small-signal output impedance seen at the output node V_{out1} .
- Calculate the small-signal output impedance seen at the output node V_{out2} .

$$a) 1mA = \frac{1}{2} \cdot (200 \times 10^{-6}) \cdot 40 \cdot V_{eff,1}^2 \therefore V_{eff,1} = 0.5V$$


$$V_{bias1} = V_{th} + V_{eff,1} = 0.5 + 0.5 = 1V$$

Transconductance:

$$= \mu_n \cdot C_{ox} \cdot \frac{W}{L} \cdot (V_{GS} - V_{TH})$$

$$g_{m1} = 200 \cdot 10^{-6} \cdot 40 \cdot (0.5) = 0.004$$

Small signal Model:

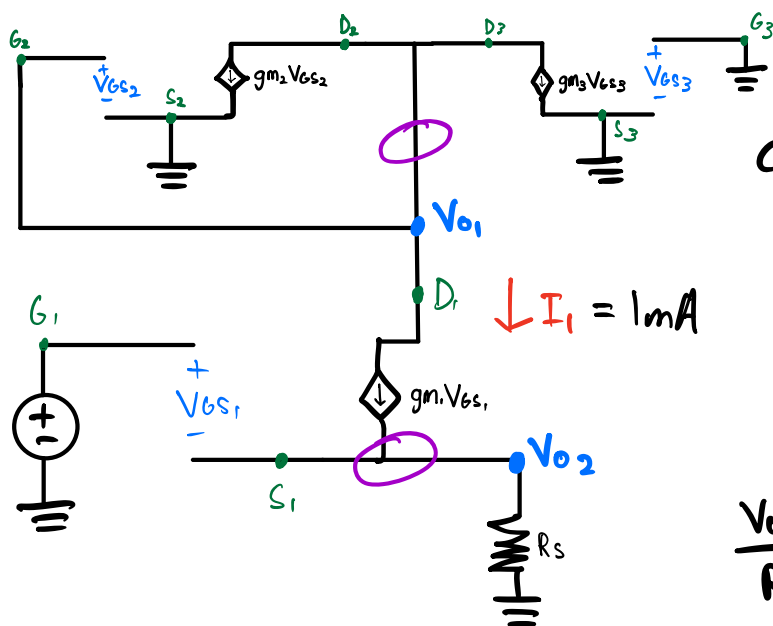

$$g_{m1} V_{GS1} = \frac{V_{O2}}{R_S}$$

$$c) V_{in} - V_{GS1} = V_{O2}$$

$$\frac{V_{O2}}{R_S} = g_{m1} (V_{in} - V_{O2})$$

$$\frac{V_{O2}}{R_S} = g_{m1} V_{in} - V_{O2} g_{m1}$$

$$\frac{V_{O2}}{R_S} + V_{O2} g_{m1} = g_{m1} V_{in}$$

$$\frac{V_{O2}}{V_{in}} = \frac{g_{m1}}{(\frac{1}{R_S} + g_{m1})} = 0.167 V/V$$

$$V_{GS3} = 0$$

$$0 + V_{GS2} = V_{O1}$$

$$V_{in} - V_{GS1} = V_{O2}$$

$$0 = g_{m2} V_{GS2} + g_{m3} V_{GS3} + g_{m1} V_{GS1}$$

$$g_{m1} V_{GS1} = \frac{V_{O2}}{R_S}$$

2. Design a common-source amplifier with a current source load based on the topology shown below with the following design specifications:

- $V_{DD} = 3\text{ V}$
- Total power consumption of 1.5 mW
- Peak to peak output signal swing of 2.5 V
- Absolute value of gain of 40
- $L = 0.4\text{ }\mu\text{m}$ for all the devices

Use the following assumptions for your design


- The nominal dc level of the output node is 1.5 V

The technology parameters are:

$$\lambda_{(NMOS)} = 0.1\text{ V}^{-1}, \lambda_{(PMOS)} = 0.1\text{ V}^{-1}, \gamma = 0, V_{TH(NMOS)} = 0.5\text{ V} \text{ and } V_{TH(PMOS)} = -0.5\text{ V},$$

$$\mu_n C_{ox} = 0.2\text{ mA/V}^2, \mu_p C_{ox} = 0.1\text{ mA/V}^2.$$

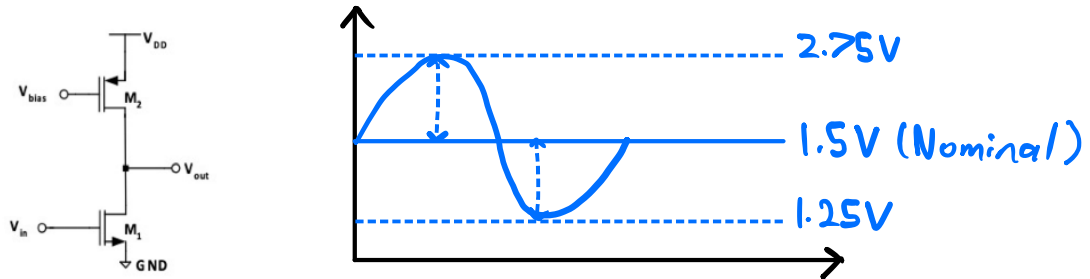Note: Use the parameter λ only for calculating the small-signal output resistance (r_o) of the transistors. Do not use λ in any other calculation including the bias current calculations.



Find V_{bias} , DC level of the input, the transistor widths (i.e., W_1 and W_2), and the gain of the circuit.

$$V_{oMax} \rightarrow V_{DG2} < |V_{th}|, V_{DG2Max} = |V_{th}|$$

$$V_{bias} = 2.75\text{ V} - 0.5\text{ V} = 2.25\text{ V}$$

$$V_{oMin} \rightarrow V_{GD1} < |V_{th}|, V_{GD1min} = |V_{th}|$$

$$V_{in} = V_{G1} = 0.5\text{ V} + 0.25\text{ V} = 0.75\text{ V}$$

Transistors are connected,

$$\text{So } I_{D1} = I_{D2} = I_D$$

$$\frac{1}{2} \cdot (0.2 \times 10^{-3}) \cdot \left(\frac{W}{L}\right)_1 \cdot (0.75 - 0.5)^2 = \frac{1}{2} \cdot (0.1 \times 10^{-3}) \cdot \left(\frac{W}{L}\right)_2 \cdot (3 - 2.25 - 0.5)^2$$

$\xrightarrow{0.4\mu\text{m}} \quad \quad \quad \xrightarrow{0.4\mu\text{m}}$

$$W_1 = 32\mu\text{m}$$

$$W_2 = 2 \times W_1 = 64\mu\text{m}$$


$$\begin{aligned} \frac{V_o}{V_{in}} &= -g_{m1} (r_{o1} \parallel r_{o2}) \\ &= -g_{m1} \left(\frac{1}{\lambda I_{D1}} \parallel \frac{1}{\lambda I_{D2}} \right) \\ &= -g_{m1} \left(\frac{1}{\lambda I_D} \parallel \frac{1}{\lambda I_D} \right) \end{aligned} \quad \rightarrow \quad \begin{aligned} &= \frac{1}{\lambda V_{eff1}} \\ &= -40\text{ V/V} \end{aligned}$$

3. It is possible to use the bulk terminal of a transistor as an input of an amplifier. Consider the single-stage NMOS amplifier shown below. For $V_{bias}=1.5V$:


a) What is the region of operation of the transistor?

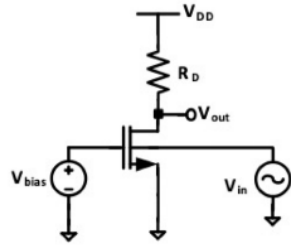b) Calculate the small-signal gain ($A_v=V_{out}/V_{in}$) of the amplifier. Recall that $g_{mb}=\eta g_m$.

Assume, $\lambda = 0$, $\eta=0.2$, $V_{TH(NMOS)}= 0.5V$, $\mu_n C_{ox}=100 \mu A/V^2$, $R_D=1k\Omega$, $(W/L)_{NMOS}= 20$, and $V_{DD}=3V$.



Small signal Model:

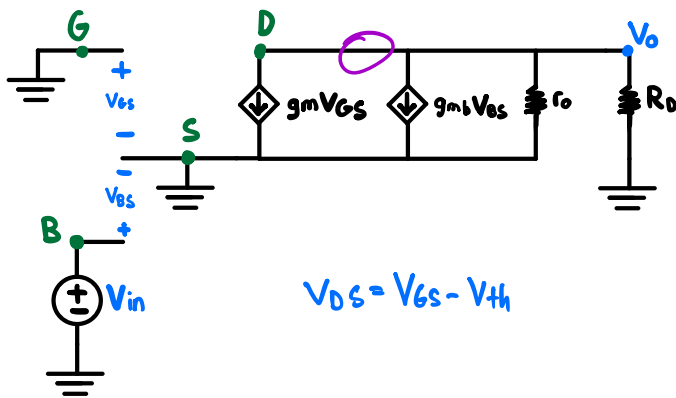

KCL: $0 = g_{mb} V_{GS} + \frac{V_o}{R_D}$

$$0 = (0.0004)(V_{in}) + \frac{V_o}{R_D}$$

$$-\frac{V_o}{R_D} = (0.0004)V_{in}$$

$$\frac{V_o}{V_{in}} = -(0.0004)R_D$$

$$A_v = -0.4 V/V$$

SATURATION

$$V_{eff} = V_{GS} - |V_{th}| = 1.5 - 0 - 0.5 = 1V$$

$$g_{mb} = \eta g_m = \eta \mu_n C_{ox} \frac{W}{L} \cdot V_{eff}$$

$$= (0.2)(100\mu)(20)(1) = 0.0004$$

$$I_D = \frac{1}{2} (100\mu)(20)(1)^2 = 1mA$$


$$V_D = V_{DD} - I_D R_D = 3 - 1 = 2V$$

$$V_{DS} = 2 - 0 = 2V \rightarrow V_{DS} > V_{GS} - V_{th}$$

$$V_{GS} - V_{th} = 1V$$

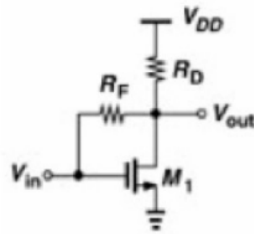
4. Note: In this problem you do not need to use any numerical value for the process parameters. If needed express your answers in terms of R_D , R_F and/or transistor small-signal parameters g_m and r_o .

In the following circuit, assuming the MOSFET is in active region:



- Calculate the small-signal voltage gain (assume $\lambda \neq 0$).
- Find the value of R_F for which the gain of the circuit is +1.
- Find the value of R_F for which the gain of the circuit is -1.
- State any condition that may be required so that the R_F calculated in part c is realizable.

Small Signal Model

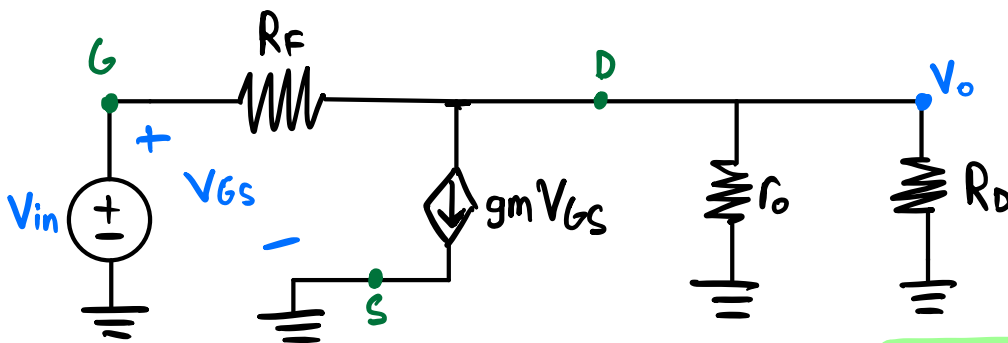

a) $V_{in} = V_{GS}$

$$\frac{V_{in} - V_o}{R_F} = g_m V_{GS} + \frac{V_o}{r_o} + \frac{V_o}{R_D}$$

$$\frac{V_{in}}{R_F} - \frac{V_o}{R_F} = g_m V_{in} + \frac{V_o}{r_o} + \frac{V_o}{R_D}$$

$$\frac{V_o}{r_o} + \frac{V_o}{R_D} + \frac{V_o}{R_F} = \frac{V_{in}}{R_F} - g_m V_{in}$$

$$V_o \left(\frac{1}{r_o} + \frac{1}{R_D} + \frac{1}{R_F} \right) = V_{in} \left(\frac{1}{R_F} - g_m \right)$$

$$\therefore \frac{V_o}{V_{in}} = \frac{\left(\frac{1}{R_F} - g_m \right)}{\left(\frac{1}{r_o} + \frac{1}{R_D} + \frac{1}{R_F} \right)} = \frac{R_D r_o - R_D R_F r_o g_m}{R_F r_o + R_D R_F + R_D r_o}$$

b) $R_F = 0 \Omega$

c) $R_F = \frac{2 R_D r_o}{R_D r_o g_m - R_D - r_o}$

d) $R_D r_o g_m - R_D - r_o > 0$

$$R_D r_o g_m > R_D + r_o$$

$$g_m > \frac{R_D + r_o}{R_D r_o}$$