

# EECE 451 - POWER ELECTRONICS

Instructor: Dr. Martin Ordonez  
TAs: Franco Degioanni  
Daniel Hsu  
Lucas Sinopoli

## Assignment #2

Due December 10<sup>th</sup>, 2021

Submit a typed report (Canvas submission).

Include the procedure, steps and any relevant comment to obtain the results.

### 1. Design a PWM DC/AC Converter (Inverter) with the following specifications:

- DC Input Voltage ( $V_{dc}$ ) = 380 V
  - Desired AC Output Voltage ( $V_o$ ) = 220 V<sub>RMS</sub> / 50 Hz
  - Switching Frequency ( $F_{sw}$ ) = 20 kHz
  - Output Current ( $I_o$ ) = 10 A<sub>RMS</sub>
- 
- a) Select the corresponding topology and justify.
  - b) Calculate the required modulation index ( $m_a$ ) to achieve the desired output voltage.
  - c) Select the value of the load resistor ( $R_L$ ) to obtain the desired output current.
  - d) Find the value of the filter inductor ( $L$ ) and capacitor ( $C$ ) for a characteristic impedance ( $Z_o$ ) of 5  $\Omega$  and cut-off frequency ( $F_o$ ) of 600 Hz.
  - e) Simulate the designed converter in PSIM. Analyze the obtained results and include relevant waveforms.
  - f) Redesign the output filter ( $L$  &  $C$ ) for:
    - i.  $F_o = 1200 \text{ Hz}, Z_o = 5 \Omega$
    - ii.  $F_o = 300 \text{ Hz}, Z_o = 5 \Omega$

By using the FFT tool in PSIM, explain the effects of the filter cut-off frequency in the obtained output voltage.

2. Design a DC/DC **isolated** power supply using a full-bridge converter with the following specifications:

- DC Input Voltage ( $V_{dc}$ ) = 170 V
  - DC Output Voltage ( $V_o$ ) = 5 V
  - Output Voltage Ripple ( $\Delta V_o$ ) = +/- 1%
  - Maximum Output Current ( $I_o$ ) = 75 A
  - Inductor Current Ripple ( $\Delta i_L$ ) = 3%
  - Switching Frequency ( $F_{sw}$ ) = 150 kHz
- 
- a) Derive the converter's gain equation  $\left(\frac{V_o}{V_{in}}\right)$  and find the corresponding duty cycle ( $D$ ) for this design.
  - b) Select the value of the load resistor ( $R_L$ ) to obtain the maximum output current.
  - c) Select the value of the filter inductor ( $L$ ) and capacitor ( $C$ ) to obtain the desired current and voltage ripples.
  - d) Simulate the designed converter using PSIM. Include relevant waveforms and comments.
  - e) Find the value of the load resistor to operate the converter in the boundary of discontinuous conduction mode. Simulate the converter under this operating mode and include relevant waveforms.