

---

# EECE488: Analog CMOS Integrated Circuit Design

## Set 3

### Differential Amplifiers

Shahriar Mirabbasi  
Department of Electrical and Computer Engineering  
University of British Columbia  
shahriar@ece.ubc.ca

# Overview

---



- Reading: Chapter 4 of the Textbook      most important circuit inventions.
- Their invention dates back to vacuum tube era (1930s).
- Alan Dower Blumlein (a British Electronics Engineer, 1903-1942) is regarded as the inventor of the vacuum-tube version of differential pair.



- Differential operation offers many useful properties and is widely used in analog and mixed-signal integrated circuits
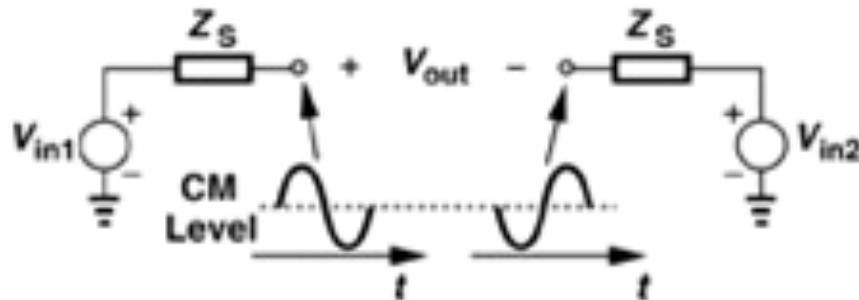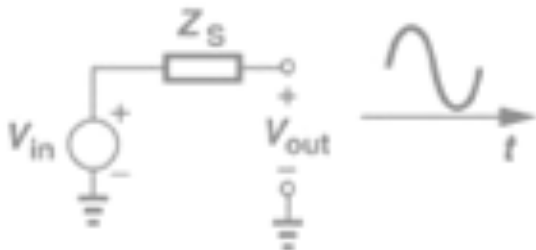
# Single-ended and Differential Signals

- A “single-ended” signal is a signal that is measured with respect to a fixed potential (typically ground).
- “Differential signal” is generally referred to a signal that is measured as a difference between two nodes that have equal but opposite-phase signal excursions around a fixed potential (the fixed potential is called common-mode (CM) level).



# Board Notes (Differential Amplifiers)



---

# Why Differential?

---

- Better immunity to environmental noise
- Improved linearity
- Higher signal swing compared to single-ended


# Higher Immunity to Noise Coupling

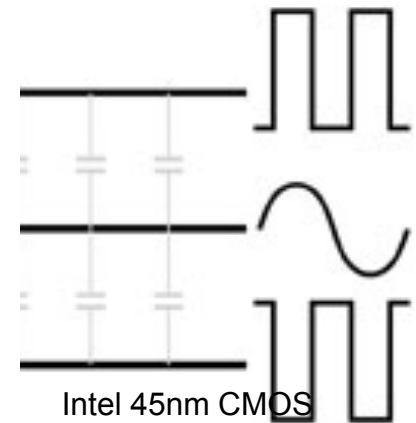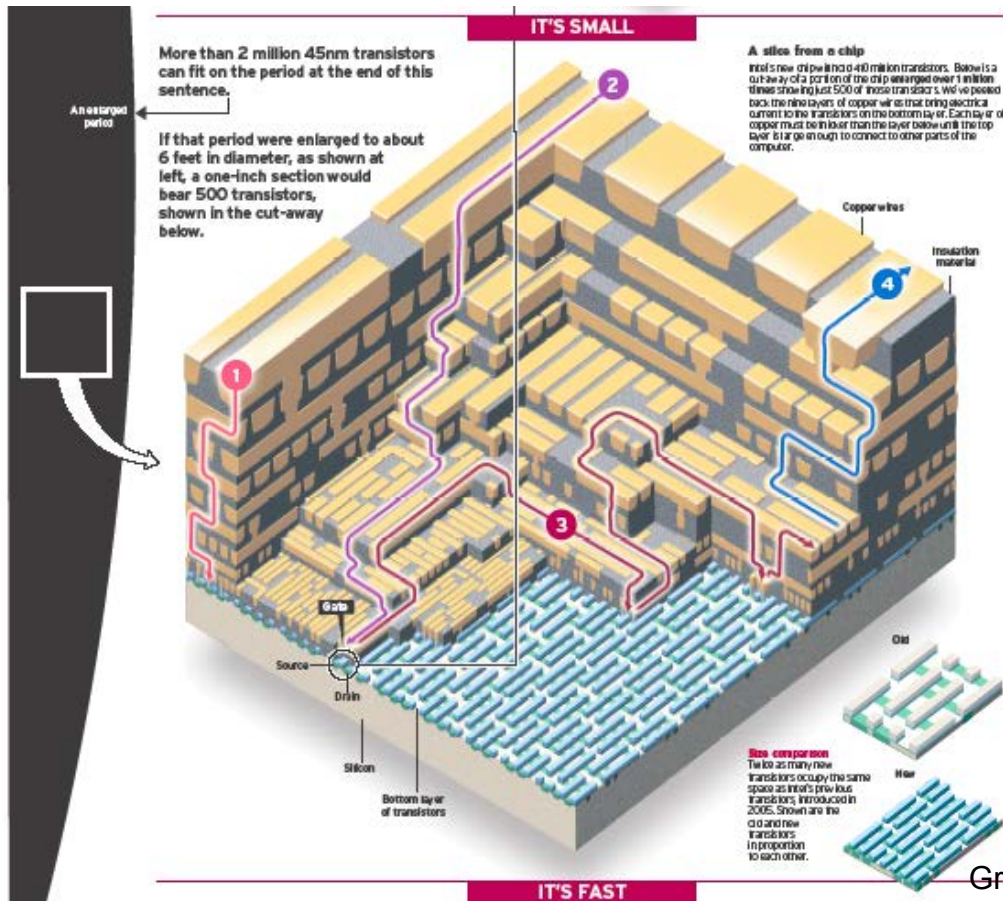

Graphics: Steve Cowden, Oregonian, 2007

# Supply Noise Reduction

---

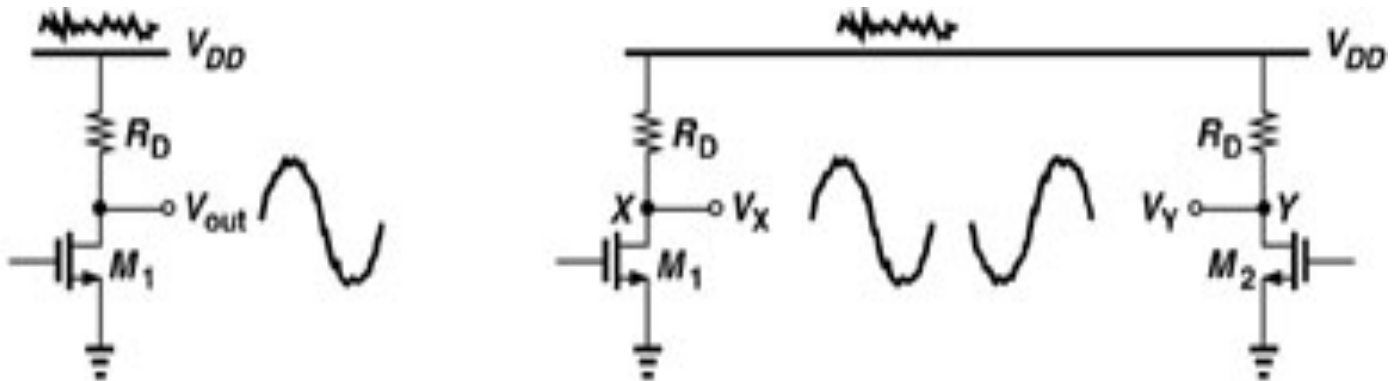


# Board Notes (Improved Linearity)


---



# Basic Differential Pair

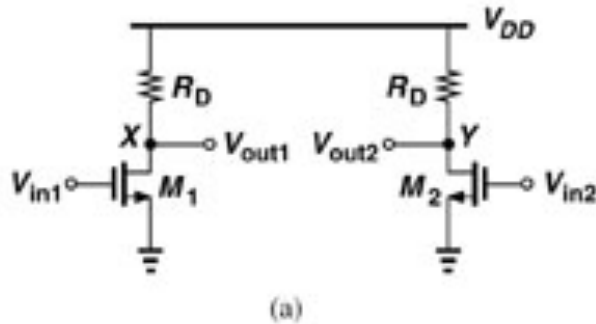


# Basic Differential Pair


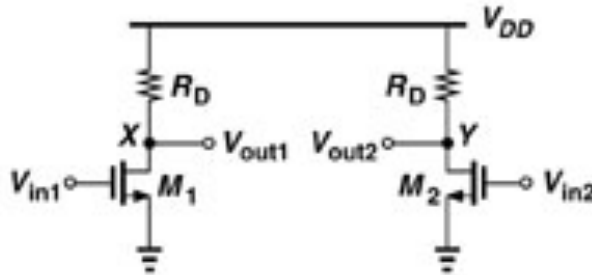


- Problem: Sensitive to input common-mode (CM) level
  - Bias currents of the transistors  $M_1$  and  $M_2$  changes as the input CM level changes
  - $g_m$  of the devices as well as output CM level change
- Can we think of a solution?


# Differential Pair

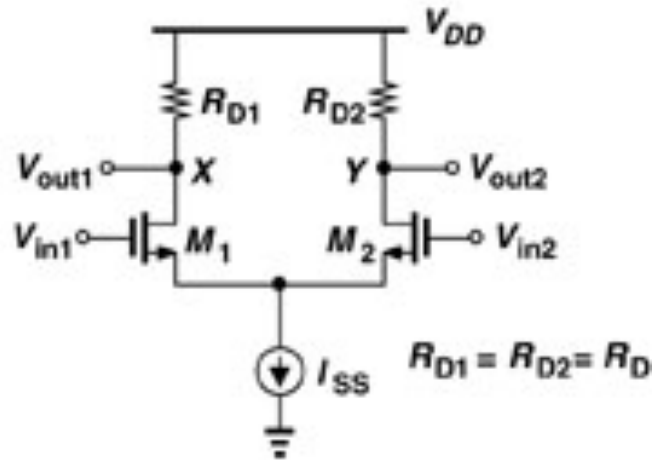

# Common-Mode Response

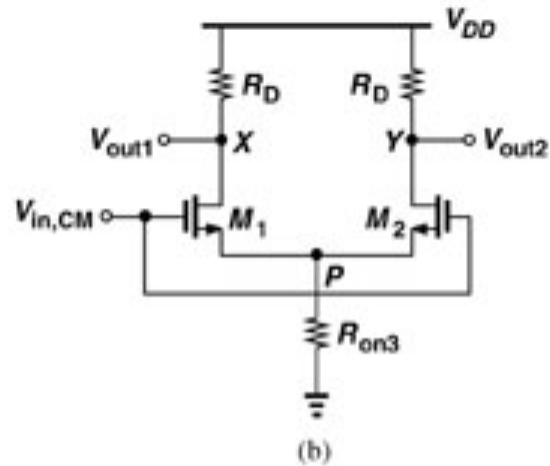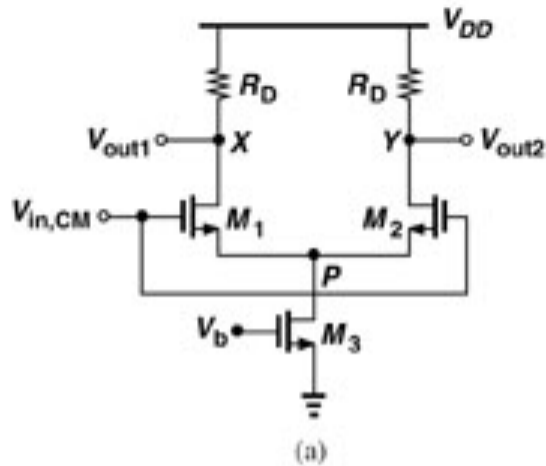

# Common-Mode Input versus Output Swing

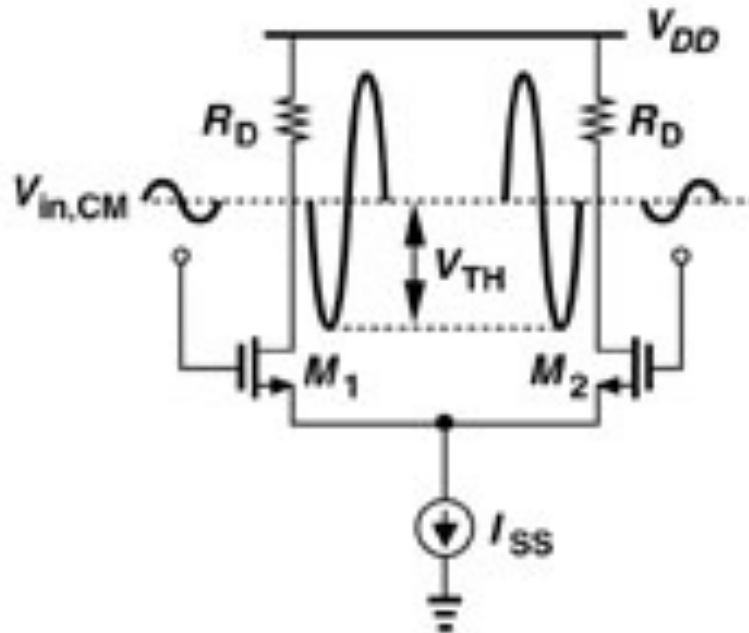


# Board Notes (“Half-Circuit” Concept)

---


# Board Notes (“Half-Circuit” Concept)

---

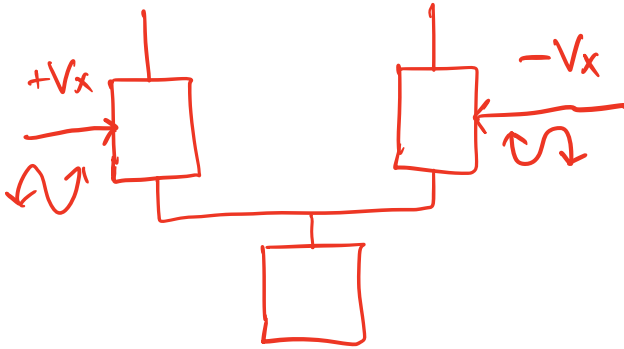
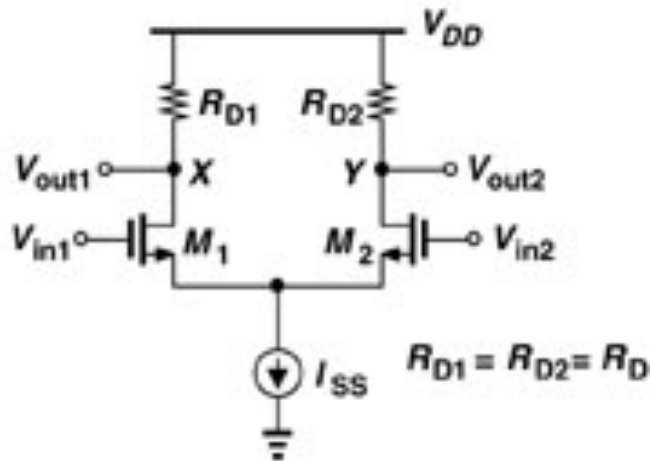
## Example


- Using the half-circuit concept, calculate the small-signal differential gain of the following circuit (for two cases of  $\lambda=0$  and  $\lambda \neq 0$ ).




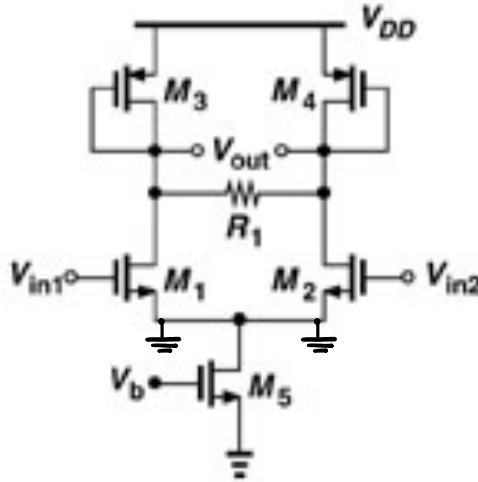
## Example

- Using the half-circuit concept, calculate the small-signal differential gain of the following circuit (for two cases of  $\lambda=0$  and  $\lambda \neq 0$ ).




- Common Source Amplifier with diode connected load in parallel with resistive load


$$\frac{V_{od}}{V_{id}} = -g_{m_1} \left( \frac{1}{g_{m_3}} \parallel \frac{R_1}{2} \right) \quad \frac{V_{od}}{V_{id}} = -g_{m_1} \left( \frac{1}{g_{m_3}} \parallel r_{o_3} \parallel r_{o_1} \right)$$
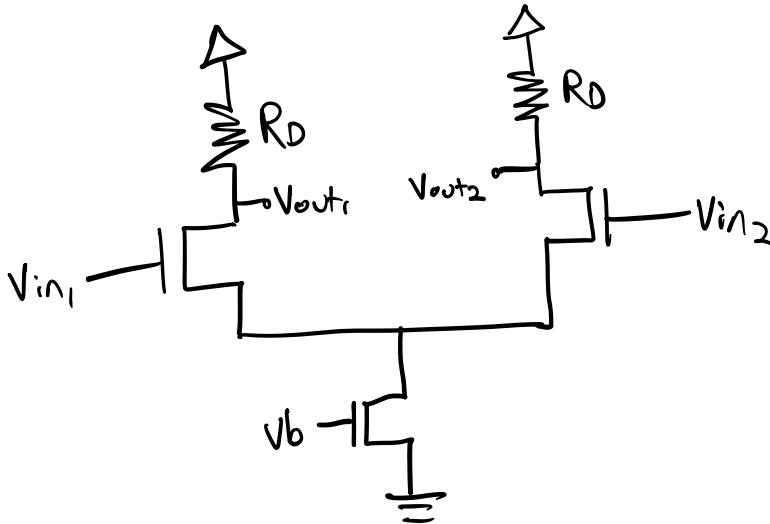
## Example

- Sketch the small-signal gain of a differential pair as a function of its input common-mode level.



# Analysis of Differential Amplifier

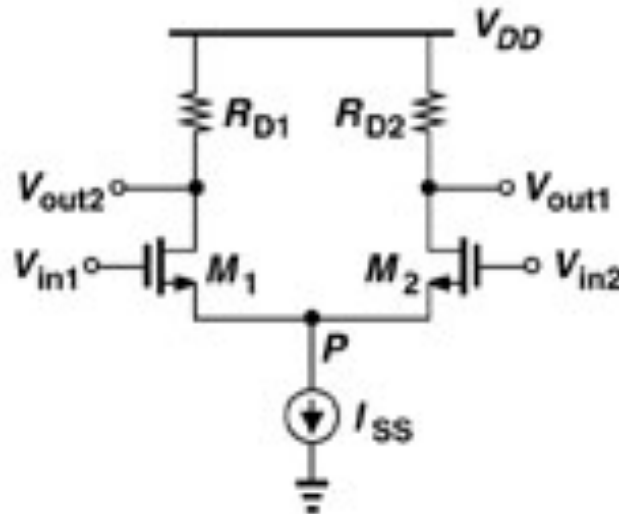

$$V_{in1} - V_{in2} = V_{GS1} - V_{GS2}, \quad V_{GS} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH}$$

# Analysis of Differential Amplifier

---

$$V_{in1} - V_{in2} = \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \frac{W}{L}}}$$

$$(V_{in1} - V_{in2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} (I_{D1} + I_{D2} - 2\sqrt{I_{D1}I_{D2}})$$

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 - I_{SS} = -2\sqrt{I_{D1}I_{D2}}$$

$$\frac{1}{4} (\mu_n C_{ox} \frac{W}{L})^2 (V_{in1} - V_{in2})^4 + I_{SS}^2 - I_{SS} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 = 4I_{D1}I_{D2}$$

# Analysis of Differential Amplifier

Using:

$$4I_{D1}I_{D2} = (I_{D1} + I_{D2})^2 - (I_{D1} - I_{D2})^2 = I_{SS}^2 - (I_{D1} - I_{D2})^2$$

and

$$4I_{D1}I_{D2} = \frac{1}{4}(\mu_n C_{ox} \frac{W}{L})^2 (V_{in1} - V_{in2})^4 + I_{SS}^2 - I_{SS} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2$$



We have:

$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \underbrace{(V_{in1} - V_{in2})}_{\text{Differential input voltage}} \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$
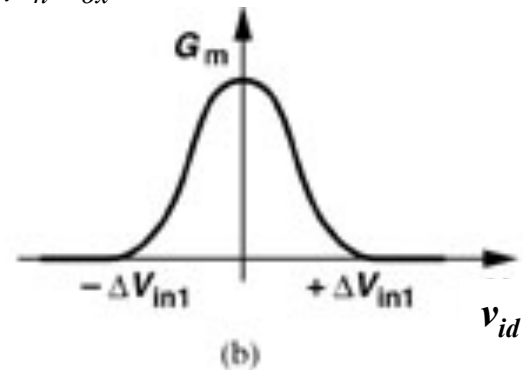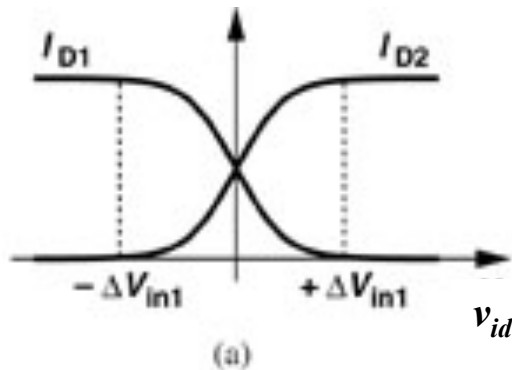
# Analysis of Differential Amplifier

$$i_d = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} v_{id} \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - v_{id}^2}$$

$$\frac{\partial i_d}{\partial v_{id}} = G_m = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \frac{\frac{4I_{SS}}{\mu_n C_{ox} W / L} - v_{id}^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} W / L} - v_{id}^2}}$$



# Analysis of Differential Amplifier

---

- For small  $v_{id}$ :


$$G_m = \frac{\partial i_d}{\partial v_{id}} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} = g_{m1} = g_{m1}$$

- We have:

$$V_{out1} - V_{out2} = R_D (I_{D1} - I_{D2}) = R_D G_m (V_{in1} - V_{in2})$$

$$\frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}} = g_{m1} R_D$$

# Differential Gain

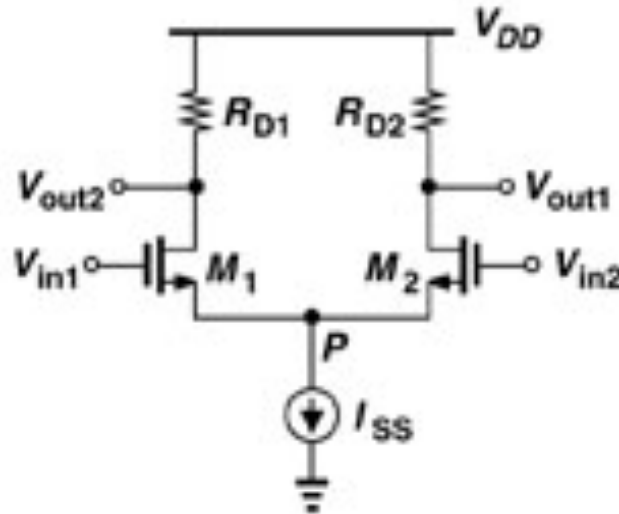


$$A_v(diff) = \frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}} = g_m R_D$$

$$A_v(Single - Ended) = \frac{g_m}{2} R_D$$




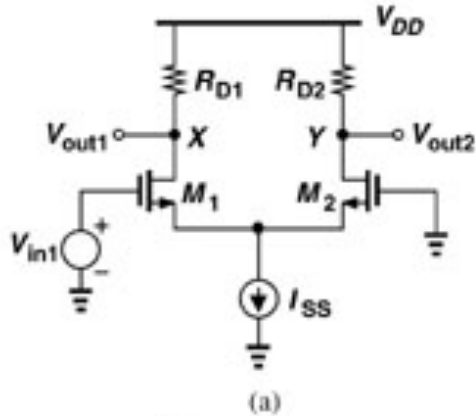
# Differential Pair as a CS and CD-CG Amplifier






$$A_v = -\frac{g_m R_D}{1 + g_m R_S}$$

$$= -\frac{g_m}{2} R_D, \quad (S.E.)$$

$$= g_m R_D, \quad (diff)$$

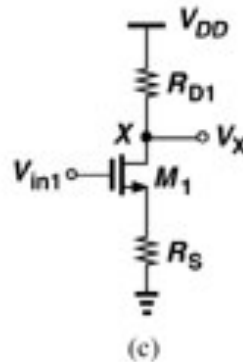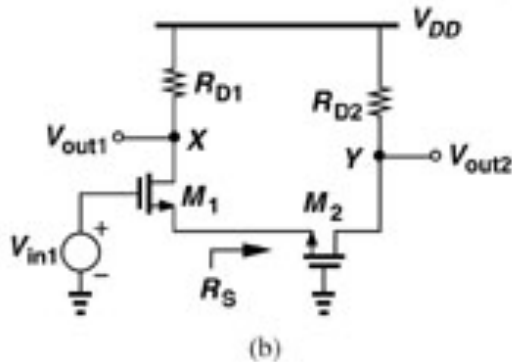

# Common-Mode Response

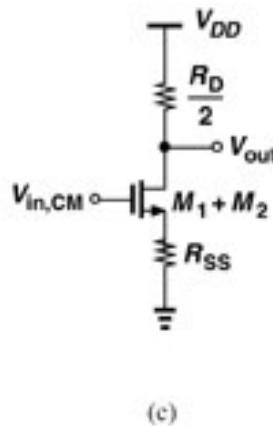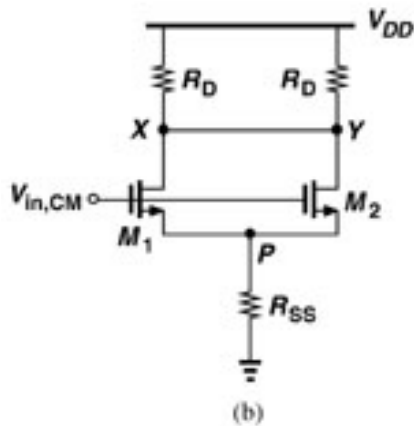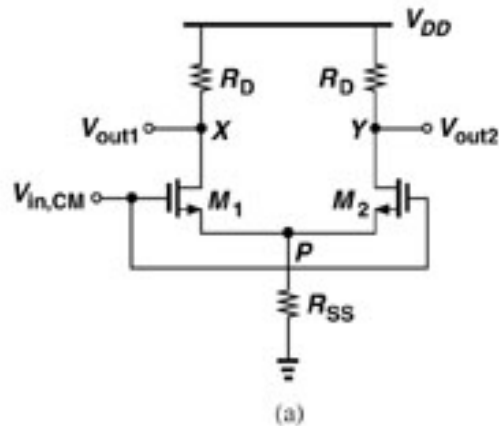

$$A_v = \frac{V_{out}}{V_{in,CM}}$$


$$= -\frac{R_D / 2}{1 / (2g_m) + R_{SS}}$$

# Board Notes

---
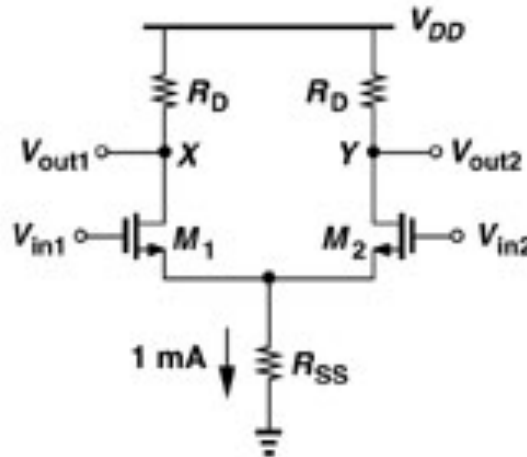
## Example

- In the following circuit assume that  $R_{SS}=500\Omega$  and  $W/L=25/0.5$ ,  $\mu_n C_{ox}=50\mu A/V^2$ ,  $V_{TH}=0.6$ ,  $\lambda=\gamma=0$  and  $V_{DD}=3V$ .




- What is the required input CM for which  $R_{SS}$  sustains  $0.5V$ ?
- Calculate  $R_D$  for a differential gain of  $5V/V$ .
- What happens at the output if the input CM level is  $50\text{mV}$  higher than the value calculated in part (a)?

# Board Notes


---

# Common-Mode Response


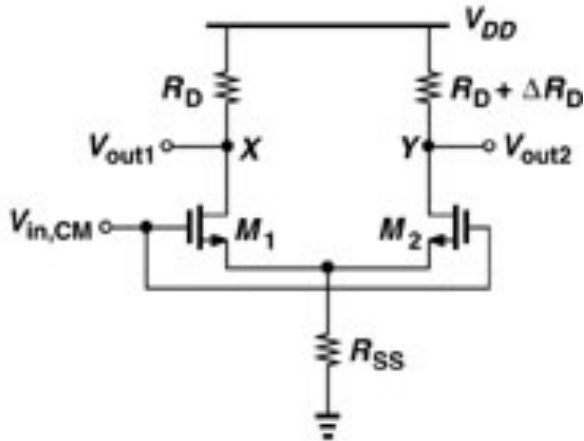


$$\frac{\Delta V_X}{\Delta V_{in,CM}} = -\frac{g_m}{1 + 2g_m R_{SS}} R_D$$
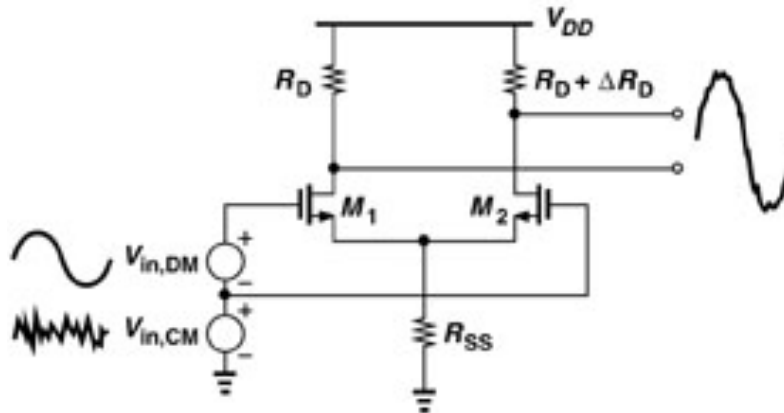
$$\frac{\Delta V_Y}{\Delta V_{in,CM}} = -\frac{g_m}{1 + 2g_m R_{SS}} (R_D + \Delta R_D)$$




# Common-Mode Response

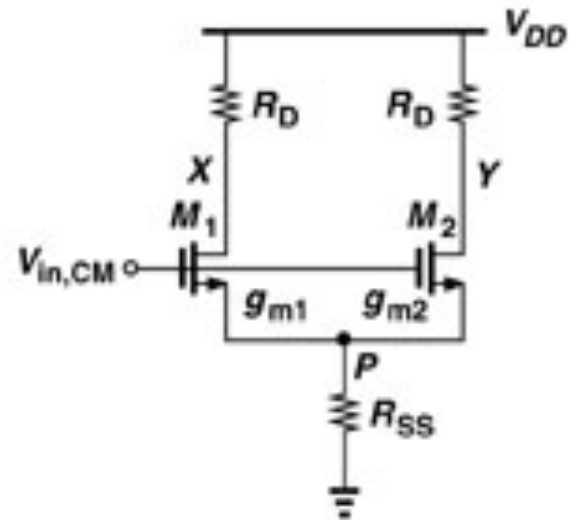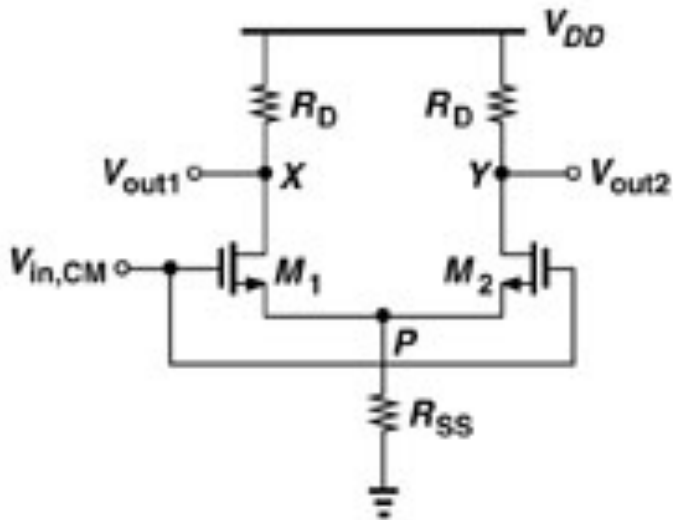

$$\frac{V_X - V_Y}{V_{in,CM}} = - \frac{g_{m1} - g_{m2}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D$$



# Common-Mode Response

---

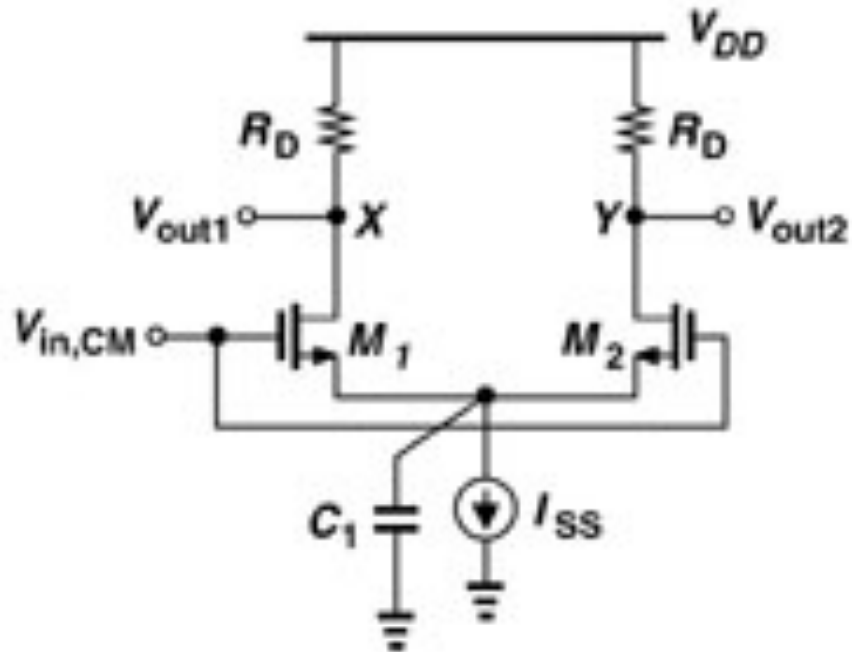



# Differential Pair with MOS Loads

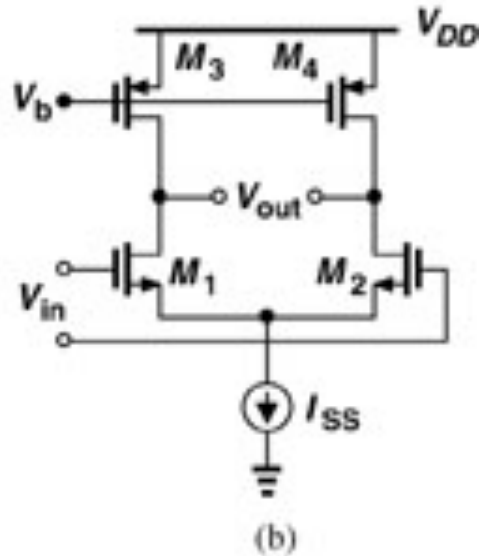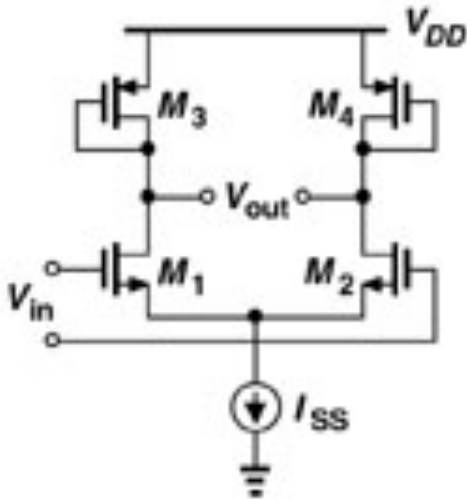


$$A_v = -g_{mN}(g_{mP}^{-1} \parallel r_{oN} \parallel r_{oP})$$



$$\approx -\frac{g_{mN}}{g_{mP}}$$

$$A_v = -g_{mN}(r_{oN} \parallel r_{oP})$$

# MOS Loads


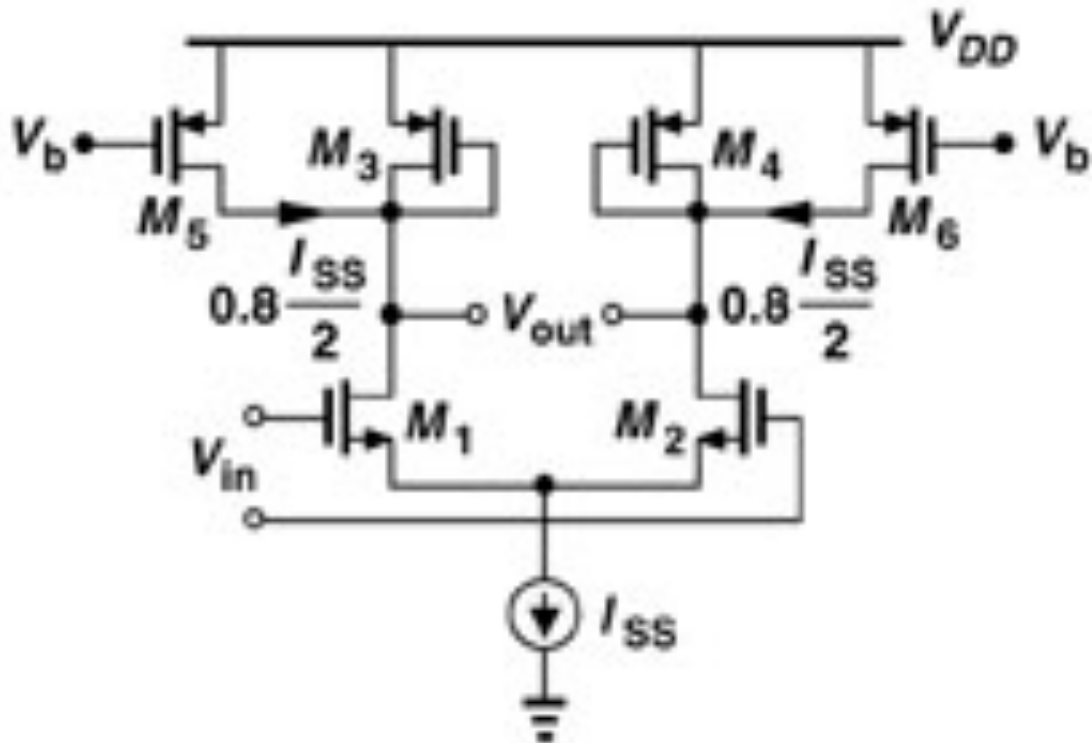


# MOS Loads

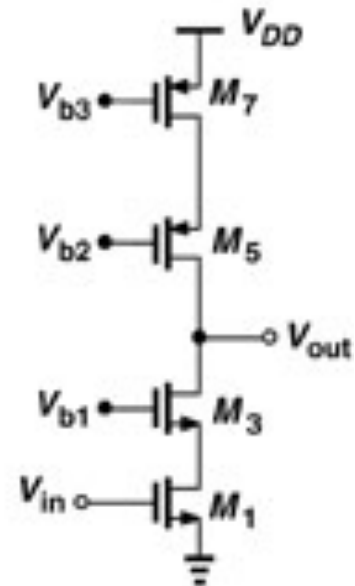
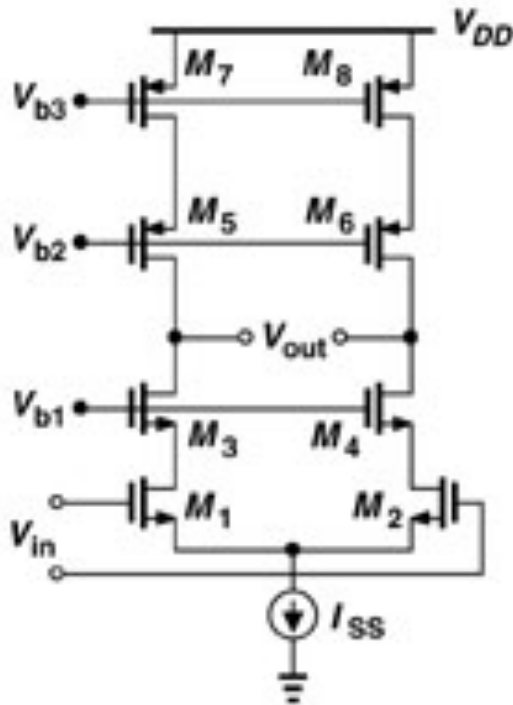


$$A_v \approx g_{m1}[(g_{m3}r_{o3}r_{o1}) \parallel (g_{m5}r_{o5}r_{o7})]$$



# Gilbert Cell

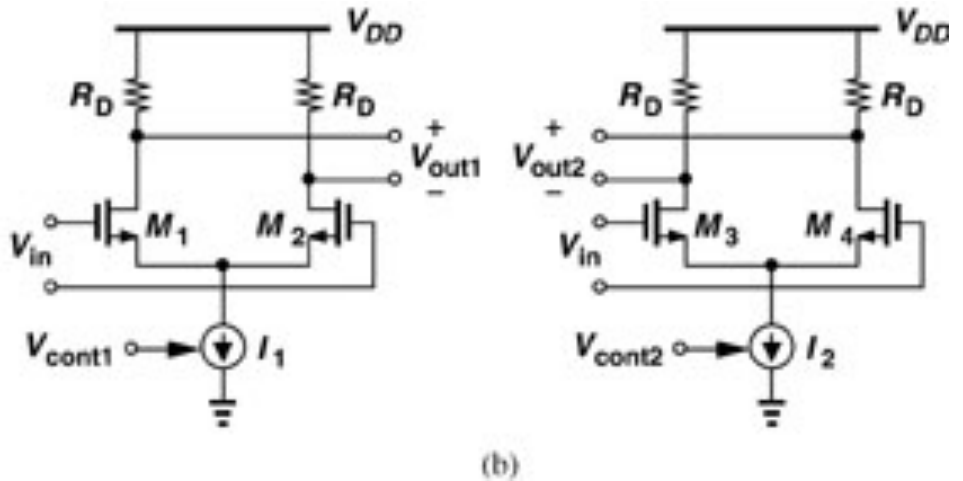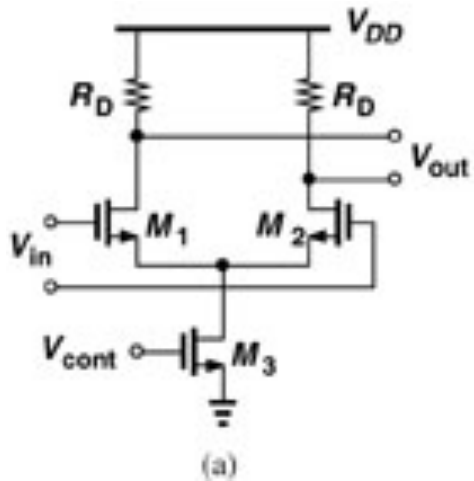

# Gilbert Cell

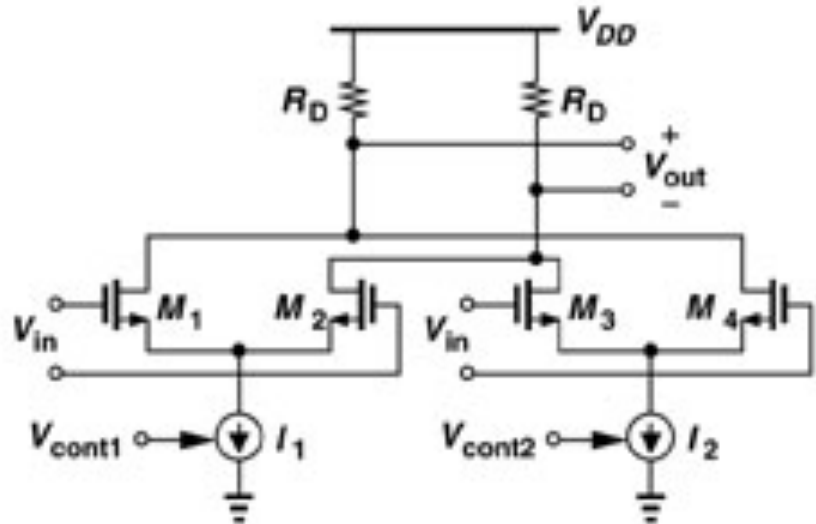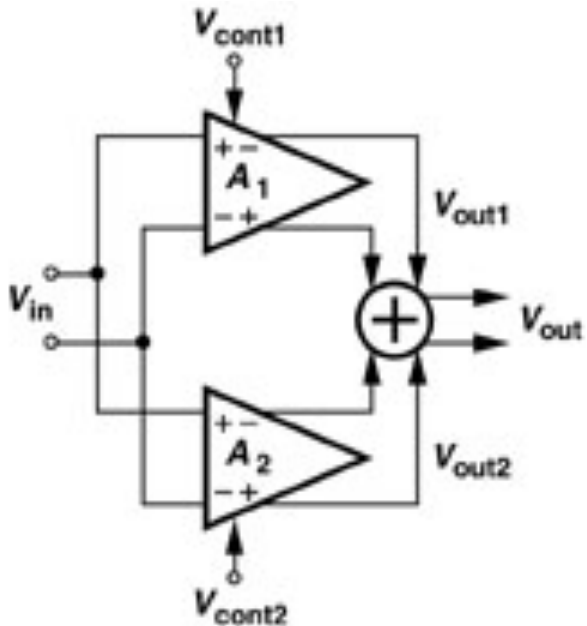

# Gilbert Cell

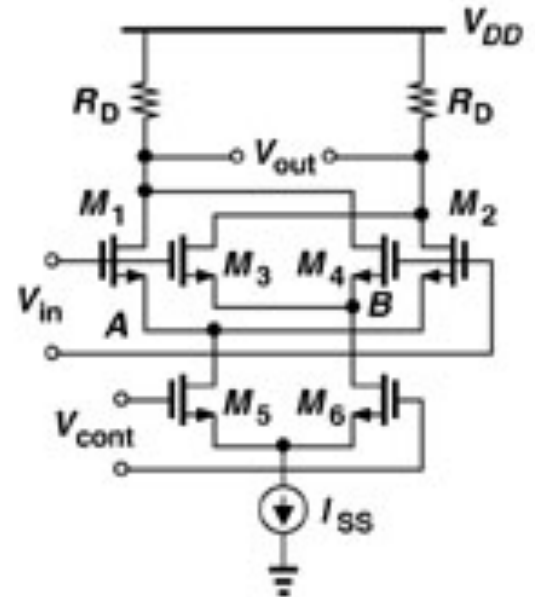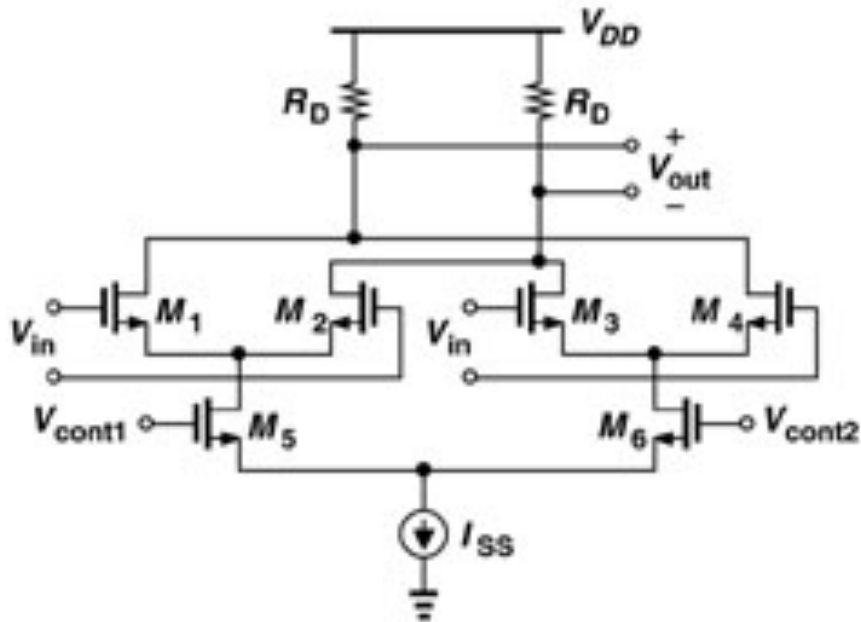

$$V_{OUT} = k V_{in} V_{cont}$$