

Differential Signals:


- Measured between two nodes as opposed to node to ground

V_A, V_B :

$$V_A = \frac{V_A + V_B}{2} + \frac{V_A - V_B}{2} \quad V_B = \frac{V_A + V_B}{2} - \frac{V_A - V_B}{2}$$

- CM: Common Mode DC Level
- DM: Differential Mode Signal


Common Mode Response:

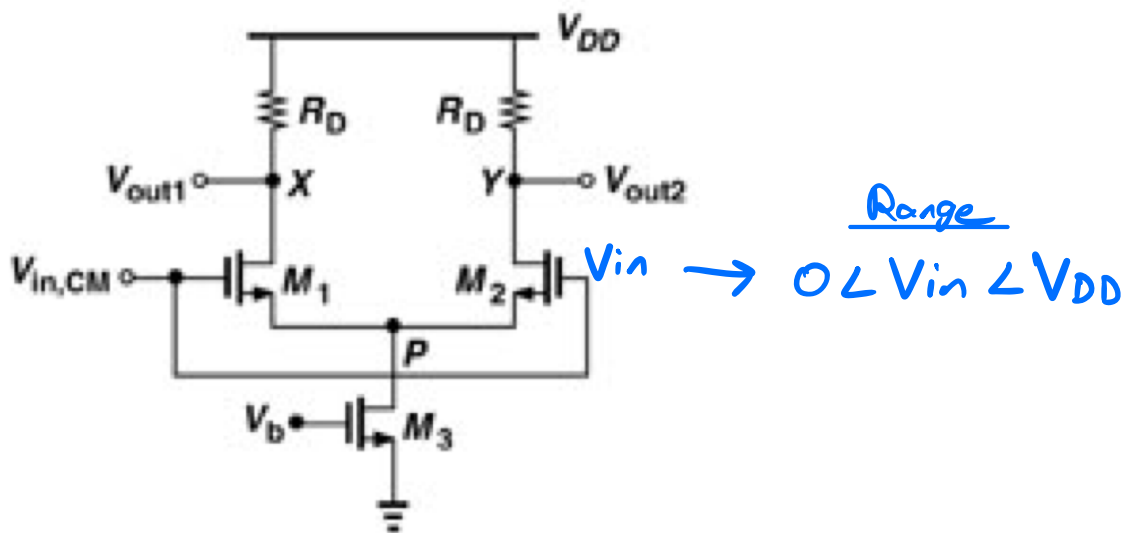

if: $V_{in} = 0$; $V_G = 0$, transistors are off. No current

$V_{GS1} + (V_b - V_{th3}) \rightarrow$ minimum voltage needed to operate

Half - Circuit Model :

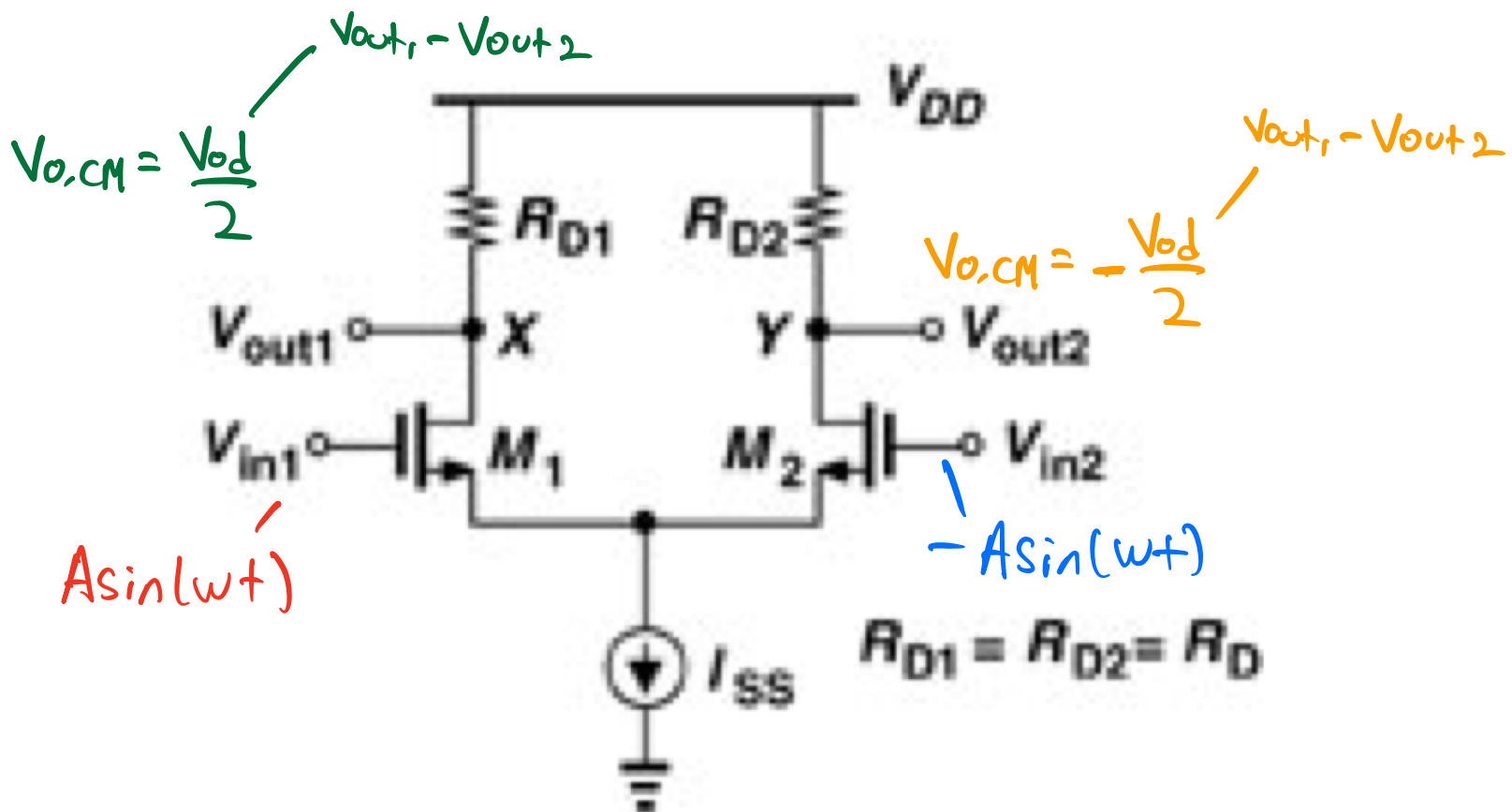

Case 1: (small signal Gain $\lambda = 0$)

$$V_{in1} = \frac{V_{in1} + V_{in2}}{2} + \frac{V_{in1} - V_{in2}}{2} : V_{CM} = \frac{V_{id}}{2} = V_{OC} + A \sin(\omega t)$$

$$V_{in2} = \frac{V_{in1} + V_{in2}}{2} + \frac{V_{in1} - V_{in2}}{2} : V_{CM} = \frac{V_{id}}{2} = V_{OC} - A \sin(\omega t)$$