

Charge/Current/Voltage

Charge

$$q_e = -1.602 \times 10^{-19} \text{ C}$$

$$q_p = 1.602 \times 10^{-19} \text{ C}$$

q

- measured in Coulombs (C)

$$q = \int_{t_1}^{t_2} i dt$$

Current


i

- measured in A, C/s
ampere = C/s

Voltage

V

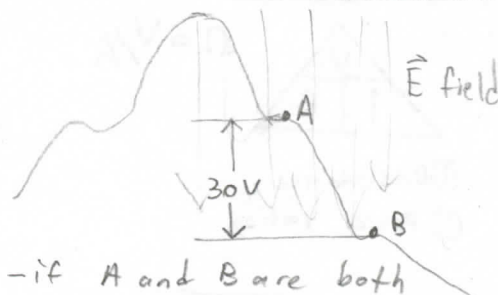- measured in Volts
- Electric height
Volt = J/C



- if A and B are both 1C of charge
- A → B, delivers 30J of energy
- B → A, costs 30J of energy

Average Current

$q(t)$

- How many ^{net} C of charge have passed the checkpoint to the right at a given time

$$i_{avg} = \frac{\Delta q}{\Delta t}$$

instantaneous Current

$$i(t) = \lim_{\Delta t \rightarrow 0} \frac{\Delta q}{\Delta t}$$

$$i = \frac{dq}{dt}$$

Energy

W

- measured in Joules

$$W = \int_{t_1}^{t_2} V i dt$$

Power

P

- measured in Watts
Watt = J/s

$$P = Vi$$

$$P = \frac{dW}{dt}; t = \frac{W}{Vi}$$

$$W = \int_{t_1}^{t_2} P dt$$

Current flowing:


uphill → Delivering power
downhill → absorbing power

Tellegen's Theorem

$$\sum P_{abs} - \sum P_{del} = 0$$

- Total absorbed power equals total delivered power in a circuit

$$P_{abs} = (V_o - V_d) i$$

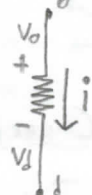

Circuits

Branch

- a link between two proper nodes
- may have zero or more binary nodes

Binary Node

- Does not affect the shape of the circuit

Atomic Branch

- Branch with no binary nodes

Branch


- The path that joins two true nodes. Atomic if no binary nodes inside

Binary Node



(true) Node

- 3 or more

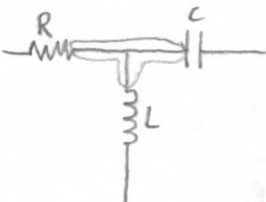

Series

- Elements in the same branch are in series

Parallel

① Both elements are in atomic branches
② Both atomic branches share the same true nodes. Must share both

Series/Parallel

- Two elements in series have the same current.
But two elements that have the same current aren't necessarily in series

- Two elements in parallel have the same voltage but not the other way

Circuit with no true nodes

- Promote one B-node to rank of true node (arbitrary)

Active Element

Battery, generator, etc., sources
Deliver power (usually)

Passive Element

Resistor, inductor, capacitor
Absorb power (sometimes)

Resistance

- resists currents i

Inductance

- resists changes in currents $\frac{di}{dt}$

Capacitance

- Resists changes in voltages $\frac{dV}{dt}$

Passive element

- Assume water falls from the sky

Ohm's Law - R in Ohms (Ω)



$$\Omega = V/A$$

- ① Resistance
- ② Power rating

Inductor - L in Henrys (H)

$$V = L \frac{di}{dt}$$

- ① Inductance
- ② Current rating


Capacitor - C in Farads (F)

$$i = C \frac{dV}{dt}; V = \frac{q}{C}$$


- ① Capacitance
- ② Voltage rating

Active (Sources)

Independent:

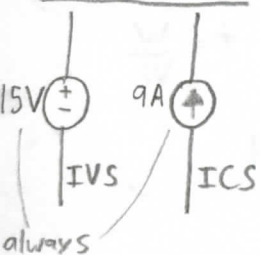

Dependent:

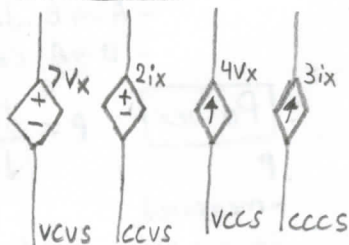

Kirchoff's Current Law

$$\sum_{\text{node}} i_{\text{in}} = \sum_{\text{node}} i_{\text{out}}$$

$$\sum_{\text{Gauss}} i_{\text{in}} = \sum_{\text{Gauss}} i_{\text{out}}$$

$$\sum_{\text{Boundary}} i_{\text{in}} = \sum_{\text{Boundary}} i_{\text{out}}$$

Inverses

Conductance:

$$G = \frac{1}{R} \text{ - measured in Siemens}$$

Inductance:

$$\Gamma = \frac{1}{L} \text{ - measured in } H^{-1}$$

gamma

Capacitance:

$$T = \frac{1}{C} \text{ - measured in } F^{-1}$$

Kirchoff's Voltage Law


- a loop is a closed path that only crosses a node once, ie: arrive in it and leave out of it

Window pane (Mesh)

- a loop that does not contain any loops inside

Neither in Series/Parallel

Triangle/Delta/Pi Config:

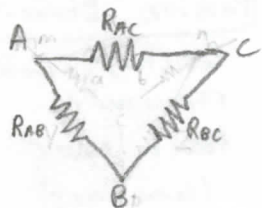

Addition Simplification

$$R_{eq} = R_1 + R_2 + \dots + R_n \text{ SERIES}$$

$$L_{eq} = L_1 + L_2 + \dots + L_n \text{ SERIES}$$

$$V_{\text{source}} = V_1 + V_2 + \dots + V_n \text{ SERIES}$$

$$C_{eq} = C_1 + C_2 + \dots + C_n \text{ PARALLEL}$$

$$i_{\text{source}} = i_1 + i_2 + \dots + i_n \text{ PARALLEL}$$

Inverse Simplification


$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \right)^{-1} \text{ PARALLEL}$$

$$L_{eq} = \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right)^{-1} \text{ PARALLEL}$$

$$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \right)^{-1} \text{ SERIES}$$

*midterm demonstrate not on slides

Star/Wye/tee config:

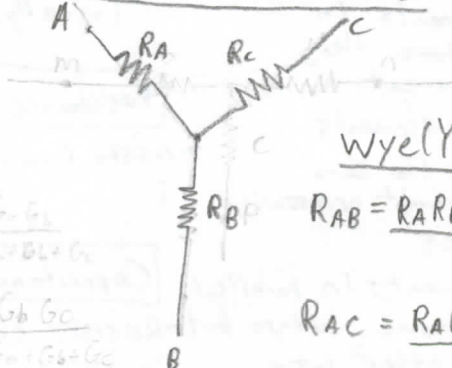

Wye(Y) → Delta:

$$R_{AB} = \frac{R_A R_B + R_A R_C + R_B R_C}{R_C}$$

$$R_{AC} = \frac{R_A R_B + R_A R_C + R_B R_C}{R_B}$$

$$R_{BC} = \frac{R_A R_B + R_A R_C + R_B R_C}{R_A}$$


Delta → Wye(Y):

$$R_A = \frac{R_{AB} R_{AC}}{R_{AB} + R_{AC} + R_{BC}}$$

$$R_B = \frac{R_{AB} R_{BC}}{R_{AB} + R_{AC} + R_{BC}}$$

$$R_C = \frac{R_{AC} R_{BC}}{R_{AB} + R_{AC} + R_{BC}}$$

Source Transformations

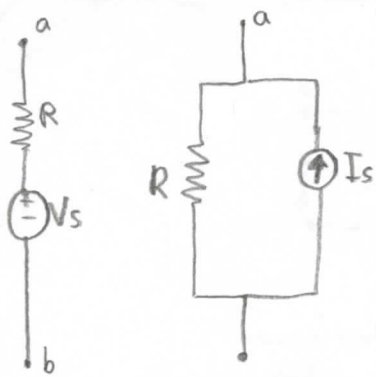


$$V_S = R I_S$$

$$I_S = \frac{V_S}{R}$$


Superposition

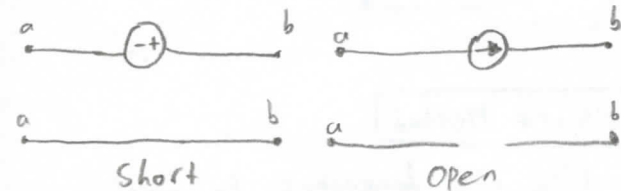Killing a V_{source} : killing a I_{source} :



Modified Nodal Analysis


Controlling Variable:

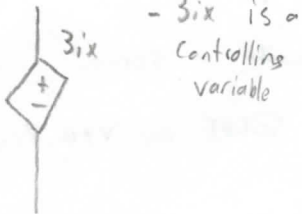

- $3i_x$ is a controlling variable

Evil currents:


- currents in evil branches

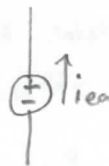

Solution Method

- ① Choose REF node
- ② Choose R/RV current directions
- ③ Label every true node (KCL)
- ④ Label every evil current (EVL)
- ⑤ Label every controlling variable (CTL)

Voltage Divider

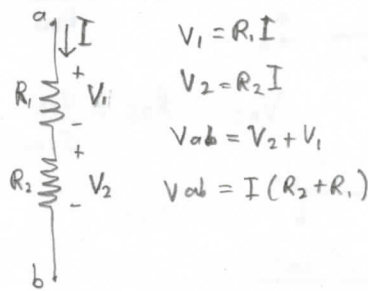

$$V_1 = R_1 I$$


$$V_2 = R_2 I$$

$$V_{ab} = V_2 + V_1$$

$$V_{ab} = I(R_2 + R_1)$$

$$\frac{V_1}{V_{ab}} = \frac{R_1}{R_{eq}} \quad \text{"Same \%"}$$

Current Divider

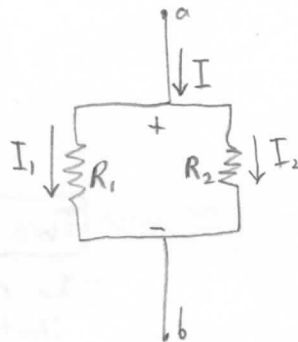

$$I_1 = \frac{V_{ab}}{R_1}$$


$$I_2 = \frac{V_{ab}}{R_2}$$

$$I = \frac{V_{ab}}{R_1} + \frac{V_{ab}}{R_2} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_{ab}$$

$$\frac{I_1}{I} = \frac{R_2}{R_1 + R_2} \quad \text{"Same \%"}$$

$$\frac{I_1}{I} = \frac{G_1}{G_1 + G_2}$$


Thevenin and Norton Equivalents

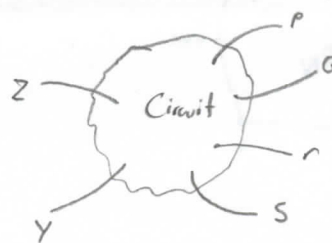


Two nodes = one port
(could be binary or true)

(4) New ideal Circuit Elements


Open circuit:

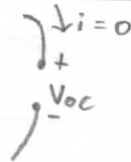

Short circuit:

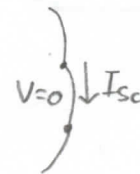

Ammeter:

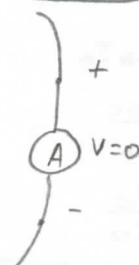


Voltmeter:




Classic Method

Open Circuit test:

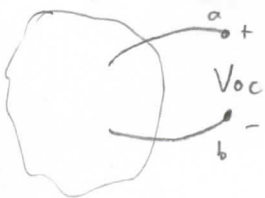



$$V_{TH} = V_{oc}$$

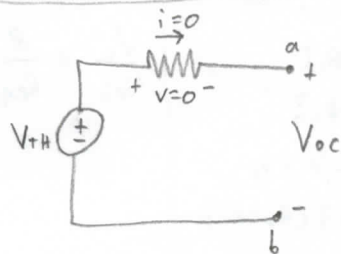

$$I_{sc} = \frac{V_{TH}}{R_{TH}}$$

$$R_{TH} = \frac{V_{TH}}{I_{sc}}$$

Short circuit test:

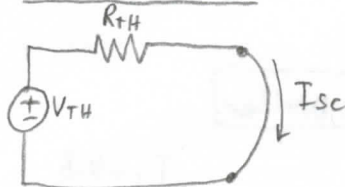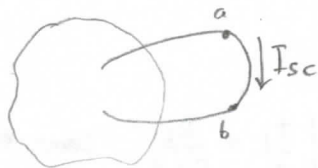


Kill Sources (All independent)

- Find $R_{eq} = R_{TH}$

Only controlled sources

$$V_{oc} = 0$$

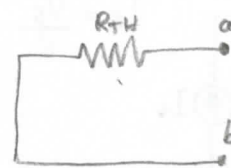



How....:

apply a 1Amp current between the nodes, solve for R_{TH}



Two Resistors Method

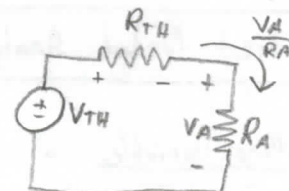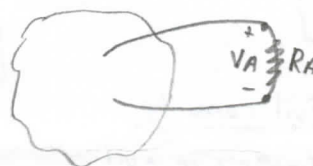"In real life its dangerous to apply short circuit test"



"Do this again with a second Resistor R_B "


SOLVE for V_{TH}, R_{TH}

$$V_{TH} - R_{TH} \frac{V_A}{R_A} = V_A$$

$$V_{TH} - R_{TH} \frac{V_B}{R_B} = V_B$$


Norton Mayer Equivalent

Short circuit test:

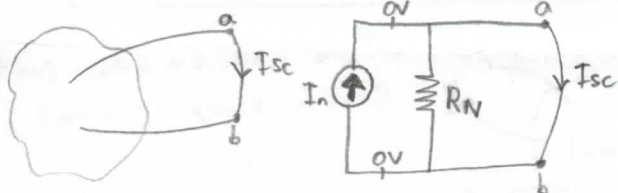

$$I_N = I_{sc}$$

Open circuit test:

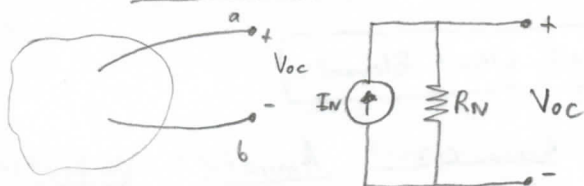

$$V_{oc} = R_N I_N$$

$$R_N = \frac{V_{oc}}{I_N}$$


$$R_N = \frac{V_{oc}}{I_{sc}}$$

Max Power Criterion

$$P_{MAX} = \frac{V_{th}^2}{4R_{th}}$$

$$P_{MAX} = \frac{I_{sc}^2 R_{th}}{4}$$

1A/2A (UBC) Method

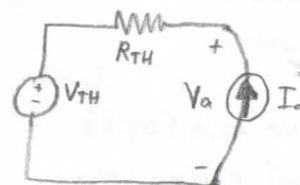


$$V_{th} + R_{th} I_a - V_a = 0$$

$$V_{th} + R_{th} I_b - V_b = 0$$

"Repeat with new I source"

First order Circuits


RL Circuit

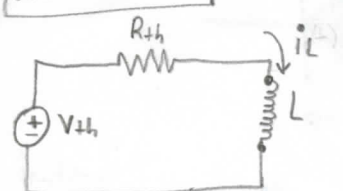

DE: $L \frac{di_L}{dt} + R i_L = V_s$

Sol'n: $i_L(t) = (I_0 - \frac{V_s}{R}) e^{-t/(L/R)} + \frac{V_s}{R}$

RC Circuit

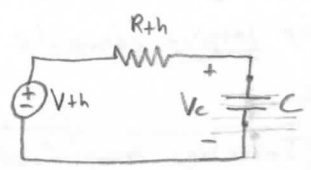

DE: $RC \frac{dV_c}{dt} + V_c = V_{th}$

Sol'n: $V_c(t) = (V_{c0} - V_{th}) e^{-t/RC} + V_{th}$


Impedance

$Z_L = Lp$ $* p = \frac{d}{dt}$
 $Z_C = \frac{1}{Cp}$ (s^{-1})
 $Z_R = R$


General Ohm's Law:

$V = Z \cdot i$
 Volts / impedance = Current

R/L/C Impedance

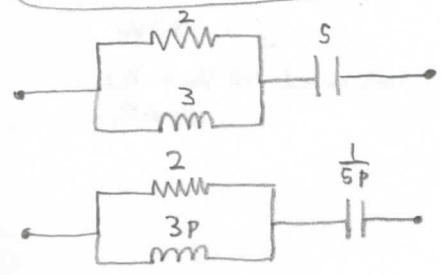

Right after we move a switch $t=0^+$

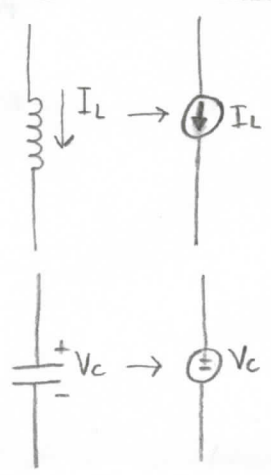

Capacitor

where V_0 is initial voltage


$V_C = V_0 e^{-t/RC}$
 $Q = CV_0 e^{-t/RC}$
 $I = \frac{V_0}{R+1} e^{-t/RC}$

Inductor

where V_b is final voltage


$V_L = V_b e^{-t/R/L}$
 $I = \frac{V_b}{R} (1 - e^{-t/R/L})$

Operational Amplifiers

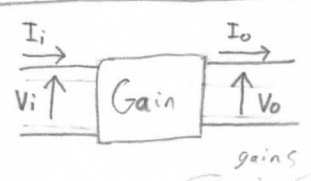

$A_v = \frac{V_o}{V_i}$ $A_I = \frac{I_o}{I_i}$ $A_p = \frac{P_o}{P_i}$

$A_v^{dB} = 20 \log_{10} \left| \frac{V_o}{V_i} \right|$ $A_I^{dB} = 20 \log_{10} \left| \frac{I_o}{I_i} \right|$ $A_p^{dB} = 10 \log_{10} \left| \frac{P_o}{P_i} \right|$

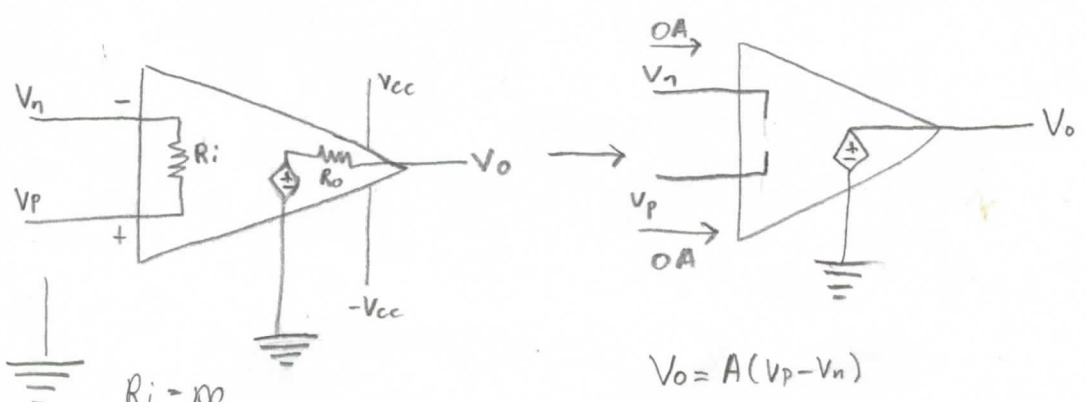

$R_i = \infty$
 $R_o = 0$
 $A = \infty$ (Voltage gain)


$V_o = A(V_p - V_n)$

$V_c(t) = (V_{c0} - V_{cf}) e^{-t/RC} + V_{cf}$

$I_L(t) = (I_{L0} - I_{Lf}) e^{-t/R/L} + I_{Lf}$

where V_{c0} and I_{L0} are DCSS of both
 $V_{cf} = V_{th}$ seen by capacitor
 $I_{Lf} = I_N$ seen by inductor

Negative Feedback

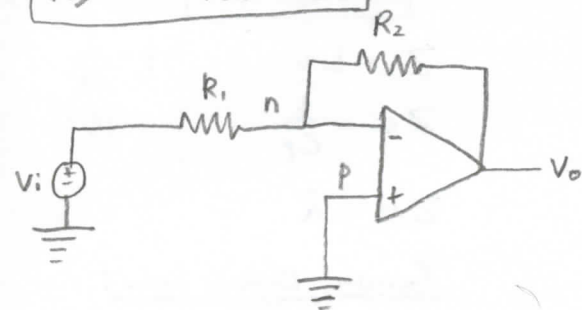

connecting the output to the inverting input by passive elements

Inverting amplifier

$V_p = V_n$
 $V_p = 0$ - Don't write a KCL for V_o **


$$V_p = V_n$$

- as long as no saturation

$$n: \frac{V_i - V_n}{R_1} = 0 + \frac{V_n - V_o}{R_2}$$

$$\therefore V_o = -\frac{R_2}{R_1} V_i$$

Non-Inverting Amplifier

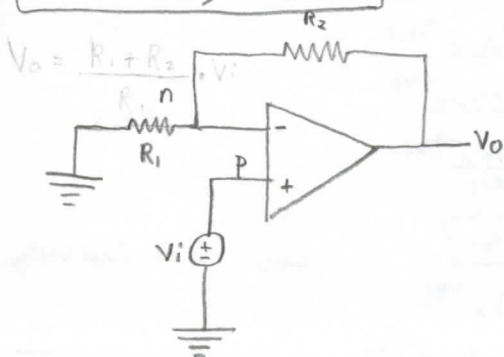


$$V_p = V_n$$

$$V_p = V_i$$

$$\therefore V_o = \frac{R_1 + R_2}{R_1} \cdot V_i$$

$$n: \frac{V_o - V_n}{R_2} = 0 + \frac{V_n}{R_1}$$

Ideal Diode

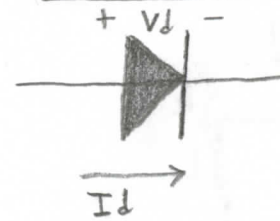

$$I_d = I_o e^{V_D / V_T} \quad \text{Constant}$$


Saturation

$$-V_{cc} \leq V_o \leq +V_{cc}$$

Positive Saturated $\rightarrow V_o = +V_{cc}$
 $V_p > V_n$

Negative Saturated $\rightarrow V_o = -V_{cc}$
 $V_p < V_n$

Rectifier Circuits

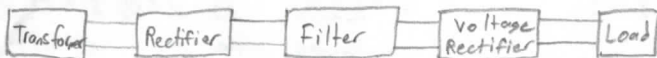


Types of Rectifiers

① Half-Wave

② Full-Wave:

- Center tap
- Bridge type


Half-Wave Rectifier

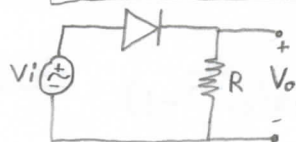


$$I = \frac{V_i - V_D}{R + r_D}$$

$$V_o = R \left(\frac{V_i - V_D}{R + r_D} \right)$$

↓ Equivalent

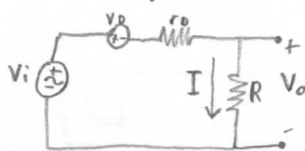

Rectifier Circuit with resistive load

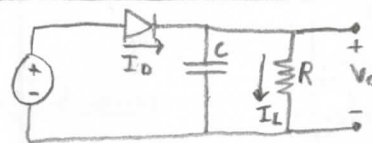

For Half Wave:

$$V_r = \frac{V_D T}{RC} = \frac{V_D}{fRC} = \frac{I_L}{fC}$$

For Full wave:

$$V_r = \frac{V_D T}{2RC} = \frac{V_D}{2fRC} = \frac{I_L}{2fC}$$

Load Voltage:

$$V_L = V_P - \frac{1}{2} V_r$$


Load current:

$$I_L = \frac{V_L}{R_L}$$


When ripple is small

$$I_L = \frac{V_P}{R_L}$$

Full Wave Bridge Rectifier

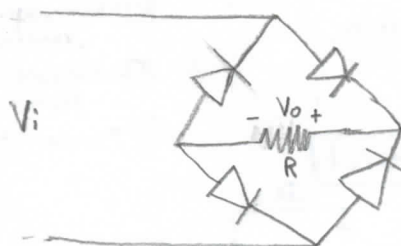

Zener diodes as Shunt Voltage regulators

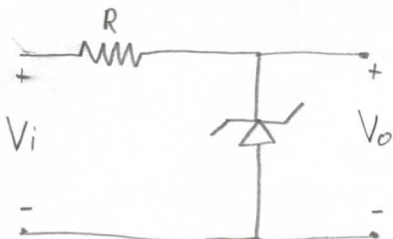


$$\text{Line regulation} = \frac{\Delta V_o}{\Delta V_{in}}$$

$$\text{Load regulation} = \left| \frac{\Delta V_o}{\Delta I_L} \right|$$

Diodes

Ideal diode

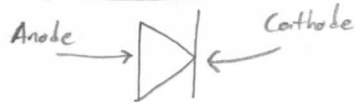

- Allows current to flow in one direction
- No voltage drop across terminals when allowing current to flow

Simplified eqn:

- Because usually $i \gg I_s$, $v \gg 10nV_T$
- $i \approx I_s e^{\frac{v}{nV_T}}$

Models

- 1 Ideal Model
- 2 Exponential Model
- 3 Constant Voltage Drop
- 4 Piecewise linear
- 5 Small signal Model


Small Signal Model

- 1 Solve the operating point of the diode in the DC circuit.

To get DC:


- Short all AC voltage sources
- Open all AC current sources
- Short all inductors
- Open all capacitors

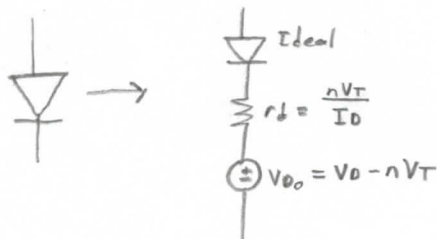- 2 Replace diode with its small signal equivalent in AC circuit



To get AC:

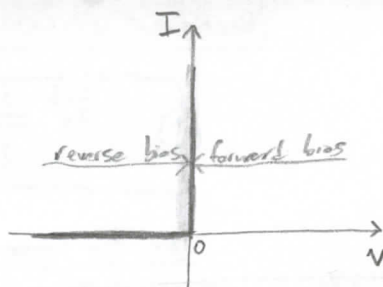- Short all DC voltage sources
- Open all DC current sources
- Open all inductors
- Short all capacitors



Real diode



- Allows a small amount of reverse current
- Has a small voltage drop when current flowing

Ideal Model

- Try all possibilities
- 2^n possibilities where n is the number of diodes

Constant Voltage Drop

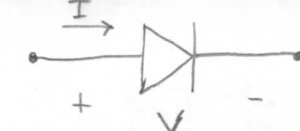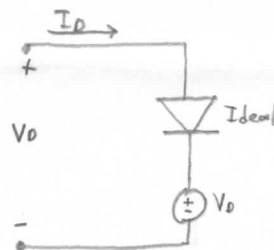- The diode can be replaced with an ideal diode and voltage source in series



$$i = I_s (e^{\frac{v}{nV_T}} - 1)$$

where: i = current through the diode
 v = voltage across the diode
 I_s = reverse saturation current, very small usually $10^{-12}A$ or $10^{-15}A$

n = empirical constant

V_T = Thermal Voltage

$$V_T = \frac{KT}{q}$$

where: k = Boltzmann's constant


T = absolute temperature

q = base charge

Equation Model

- Make a system of equations
- Most accurate
- Hard without a calculator
- Also called the exponential model

Piecewise Linear Model

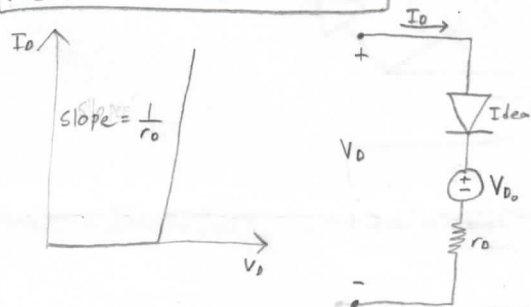


$$\frac{1}{r_D} = \frac{I_{mA} - 0mA}{0.7V - V_{D0}}$$

- To Find V_{D0}

Zener diode



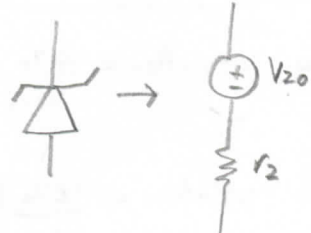
- allows current to flow in reverse at certain voltage




$$V_{Z0} = V_Z - r_z I_Z$$

BJT's

NPN transistor

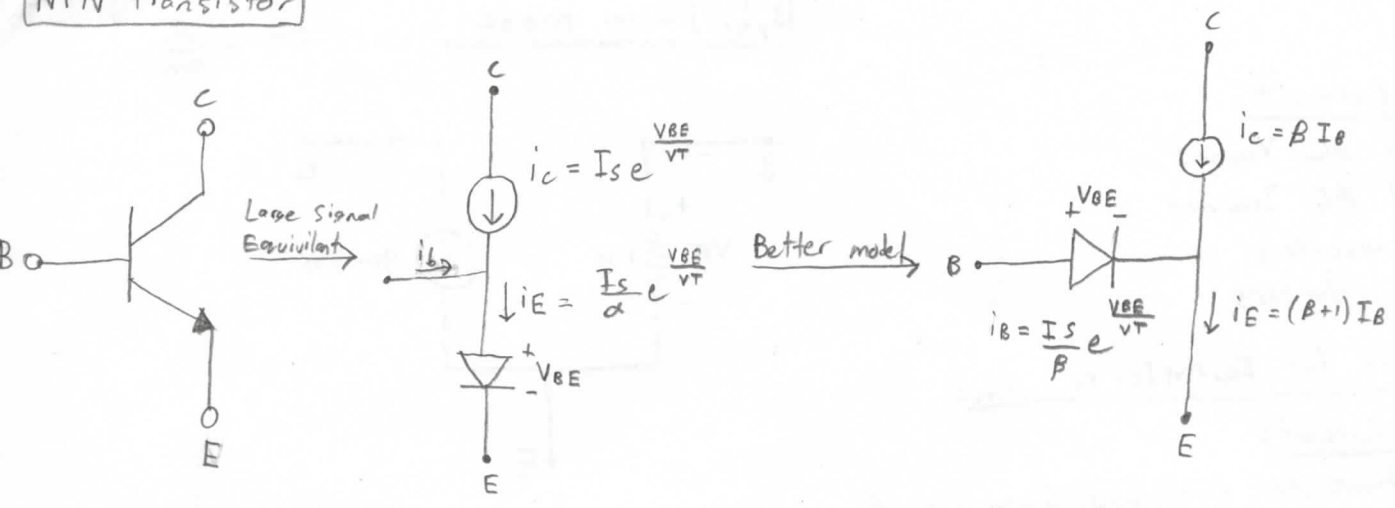

PNP Transistor

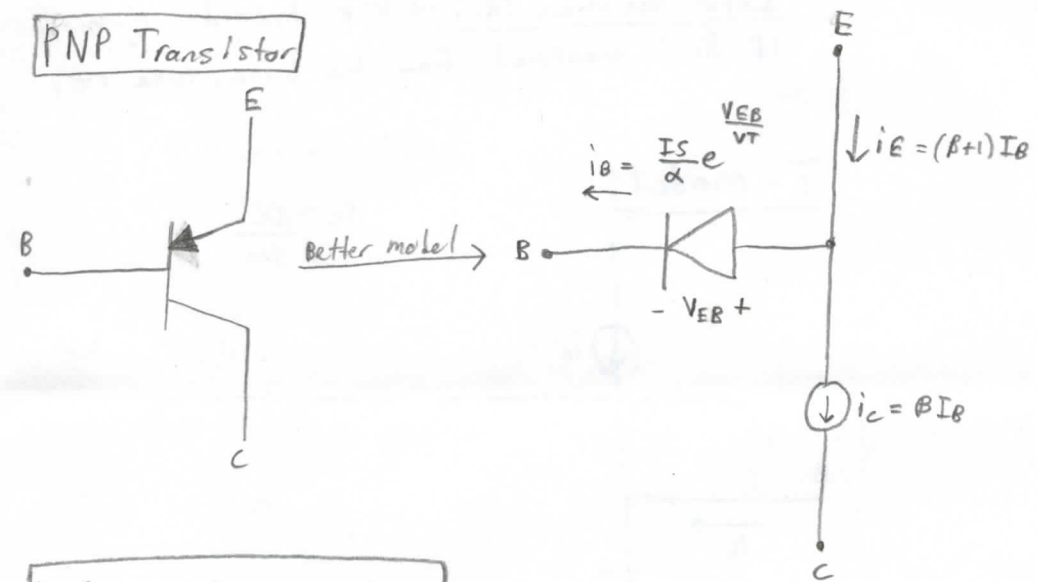

* only work in active region

Modes of Operation

BJT Mode

Collector Current (I_c)

- Cutoff $\rightarrow i_c = 0$
- Active $\rightarrow i_c = \beta \cdot I_B$
- Saturation $\rightarrow i_c < \beta \cdot I_B$


Relationships

$$I_E = I_B + I_C$$

$$I_C = \beta \cdot I_B$$


$$I_C = \alpha \cdot I_E$$
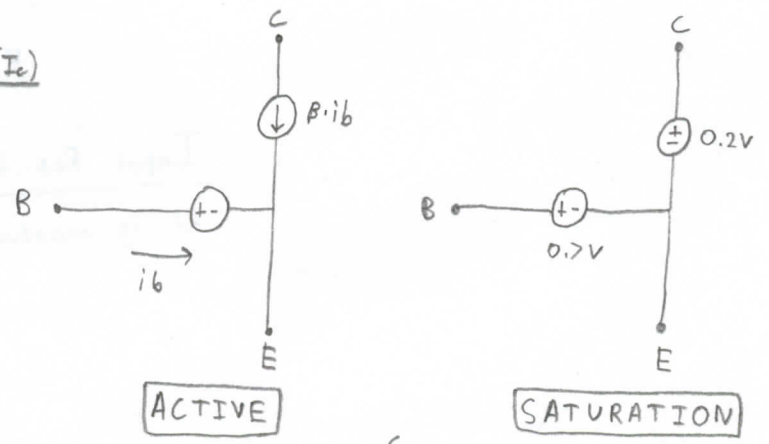
$$\alpha = \frac{\beta}{\beta + 1} \quad \beta = \frac{\alpha}{1 - \alpha}$$



ACTIVE

SATURATION

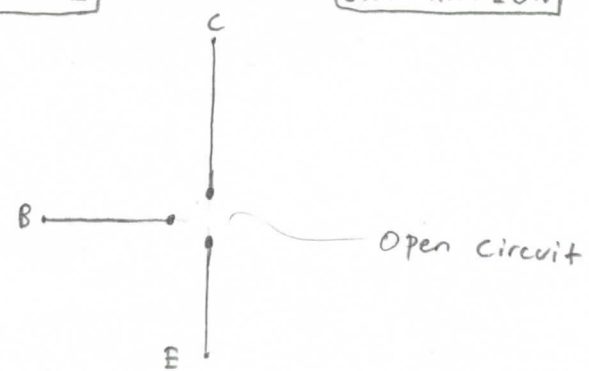

BJT Amplifiers

Models

$$g_m = \frac{I_c}{V_T}$$
$$r_{\pi} = \frac{\beta}{g_m}$$

Steps:

① Get DC circuit:

- Short all AC $V_{sources}$
- Open all AC $I_{sources}$
- open all capacitors
- short all inductors


② Solve circuit for I_c, r_{π} (or r_e), g_m :

③ Get AC Circuit:

- replace transistor with hybrid- π circuit
- Short all DC $V_{sources}$
- Open all DC $I_{sources}$
- Short all capacitors
- open all inductors

④ Solve AC circuit for (gain)


Hybrid- π model:

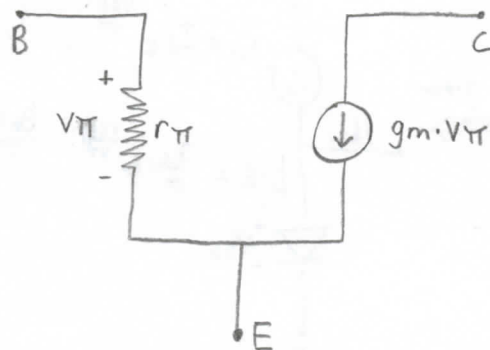

Input Resistance (R_i) \rightarrow use hybrid- π model if R_i is measured from the base. (use r_{π})

T-model:

$$r_e = \frac{\alpha}{g_m}$$

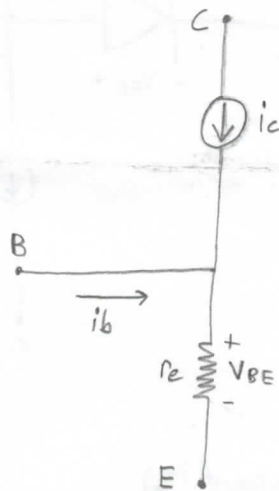


Input Resistance (R_i) \rightarrow use T-model if R_i is measured from the base. (use r_e)

Formulas

MOSFET

Enhancement N-MOSFET

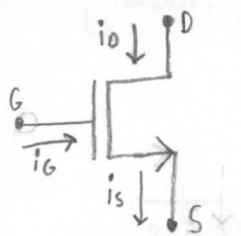

Triode Region $V_{DS} < V_{GS} - V_t$


$$i_D = i_S = k_n' \frac{W}{L} \left[(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

Saturation Region $V_{DS} > V_{GS} - V_t$

$$i_D = i_S = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2$$

Cutoff Region $V_{GS} < V_t$

$$i_D = 0$$

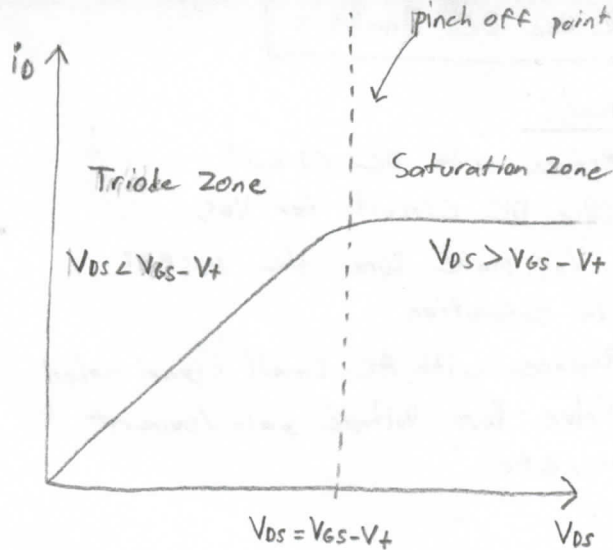

Small V_{DS} Assumption $V_{DS} < 0.2V$


* in Triode Region

$$i_D \approx k_n' \frac{W}{L} [(V_{GS} - V_t) V_{DS}]$$

Where: $i_D \approx \frac{1}{r_{DS}} \cdot V_{DS}$

$$r_{DS} = \frac{1}{N_A \cdot C_{ox} \frac{W}{L} (V_{GS} - V_t)}$$

Enhancement P-MOSFET

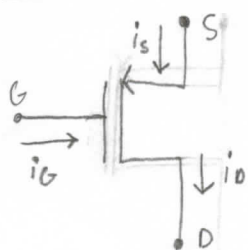

Triode Region $|V_{DS}| < |V_{GS} - V_t|$

$$i_D = i_S = k_p' \frac{W}{L} \left[(|V_{GS} - V_t|) |V_{DS}| - \frac{1}{2} V_{DS}^2 \right]$$

Saturation Region $|V_{DS}| > |V_{GS} - V_t|$

$$i_D = i_S = \frac{1}{2} k_p' \frac{W}{L} (V_{GS} - V_t)^2$$

• With Early Voltage:

$$\lambda = \frac{1}{V_A} \text{ where } V_A \neq \infty$$


$$i_D = i_S = \frac{1}{2} k_p' \frac{W}{L} (V_{GS} - V_t)^2 (1 + |\lambda| |V_{DS}|)$$

Cutoff Region $|V_{GS}| < |V_t|$

$$i_D = i_G = i_S = 0$$

Large Signal Model

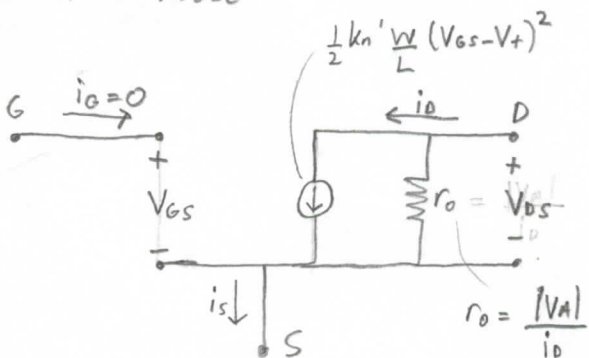* Enhancement N-MOSFET in Saturation mode




AC and DC Analysis

Steps:

- 1 Replace with DC circuit
- 2 Solve DC circuit for V_{GS} , i_D , V_{DS} . Make sure the MOSFET is in saturation
- 3 Replace with AC small signal model
- 4 Solve for Voltage gain / current gain, etc

AC small signal model

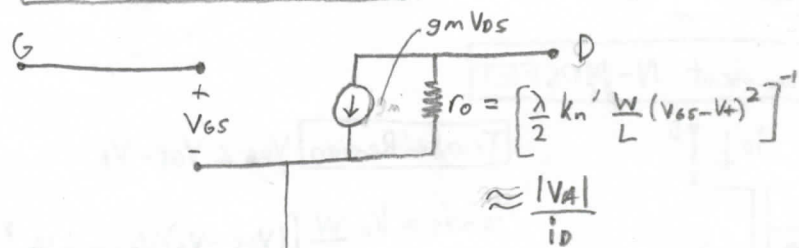

Formulas

$$\lambda = \frac{1}{V_A}$$

$$g_m = \frac{\partial i_D}{\partial V_{GS}} = k_n' \frac{W}{L} (V_{GS} - V_t)$$