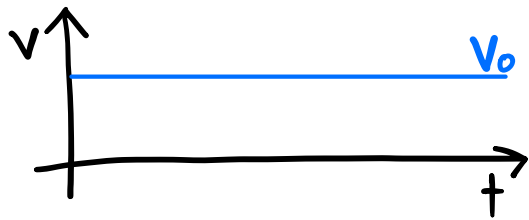


Power Electronics Fundamentals:


- Source Generates power
- Power Electronics (Delivers power Source - Load)
- Load Consumes power

Power Converters:

① DC Power



Ex: Charger (Laptop)

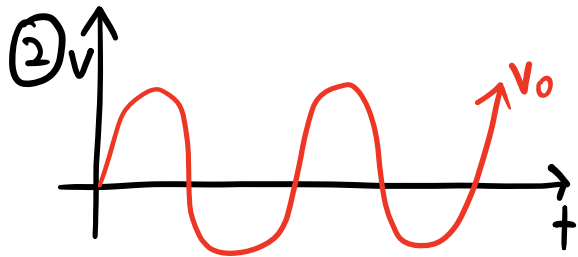

Ex: Wall outlet

Convert between these two types of power depending on what source/load needs

TYPES:


① **AC-DC** → "Rectifier"
source - load

② **DC-DC** → "Switch Mode"
change Voltage level

③ **DC-AC** → "Inverter"

④ **AC-AC**
Exists, uncommon

Periodic Waveform (it repeats):

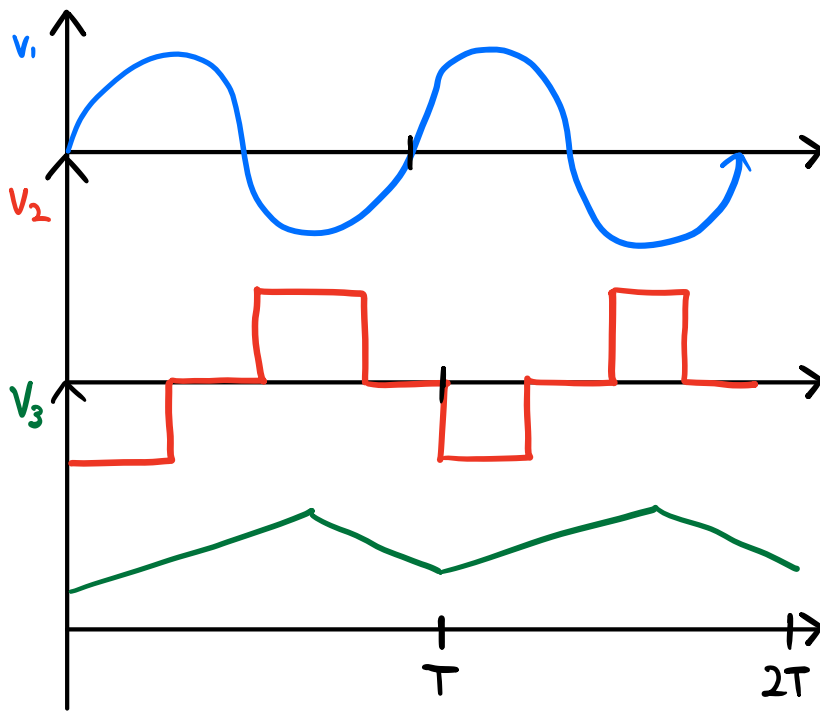

Average : (Mean)

$$V_{avg} = \frac{1}{T} \int_0^T v(t) dt$$

Notation :

$$\langle v(t) \rangle = V_{avg}$$

$$V = V(t)_{RMS}$$

Root Mean Square (RMS) :

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$


- Power seen over a resistor

$$\langle P \rangle = \left\langle \frac{v(t)^2}{R} \right\rangle = \frac{V_{rms}^2}{R}$$

$$\langle v(t)^2 \rangle = V_{RMS}^2 \quad \text{TRUE}$$

$$\langle v(t) \rangle^2 = V_{RMS}^2 \quad \text{NOT TRUE}$$

Sine Wave:

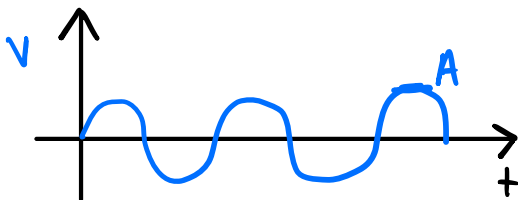

$$\text{Average} = 0 \quad v(t) = A \sin\left(\frac{2\pi t}{T}\right)$$

$$RMS = \frac{A}{\sqrt{2}}$$

$$*A = V_{peak}$$

Types of Power:

Real Power

P

(Watts)

Reactive Power

Q


Volt-Amp-Reactive


Apparent Power (Vector)

S

Volt-Amps

Power Triangle:

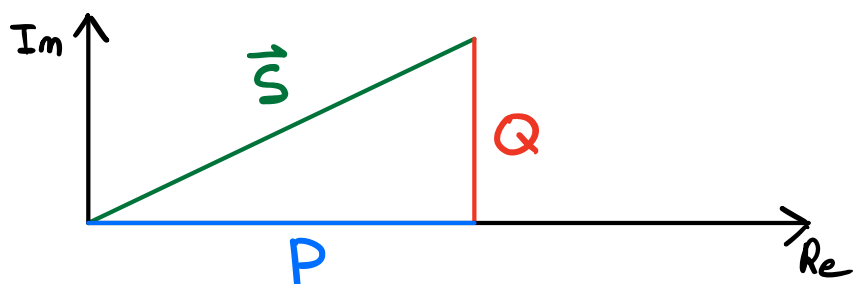

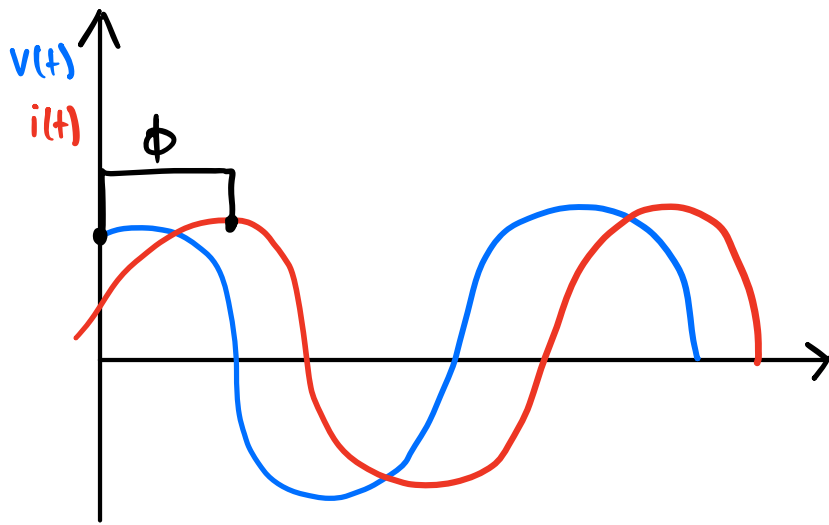

$$V(t) = \sqrt{2} V_{RMS} \cos(\omega t)$$

$$i(t) = \sqrt{2} I_{RMS} \cos(\omega t - \phi)$$

$$\phi = \phi_v - \phi_i$$

Instantaneous Power:

$$P(t) = V(t) i(t)$$

$$= \underbrace{V_{RMS} I_{RMS} \cos(\phi)}_{DC} + \underbrace{V_{RMS} I_{RMS} \cos(2\omega t - \phi)}_{\text{oscillation}}$$

$$P_{avg} = V_{RMS} I_{RMS} \cos(\phi)$$

Power Factor: $PF = \frac{\text{Real Power}}{\text{Apparent Power}}$

For General Periodic Waveforms: $PF = \frac{\langle P(t) \rangle}{V_{RMS} I_{RMS}}$


For Sine Waves: $PF = \frac{P_{RMS}}{|S|} = \frac{\cancel{V_{RMS}} \cancel{I_{RMS}} \cos(\phi)}{\cancel{V_{RMS}} \cancel{I_{RMS}}} = \cos(\phi)$

Fourier Series Expansion:



$$I_{RMS} = \sqrt{I_0^2 + I_1^2 + I_2^2 + \dots}$$

$$V_{RMS} = \sqrt{\underbrace{V_0^2}_{DC} + \underbrace{V_1^2}_{\text{Fundamental}} + \underbrace{V_2^2 + \dots}_{\text{Higher-order harmonics}}}$$

Total Harmonic Distortion:

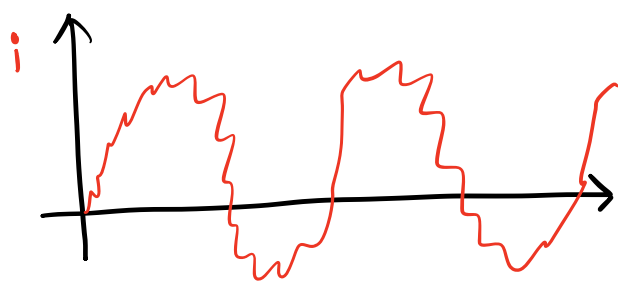


$$i = i_f + \underline{i_h + I_{DC}}$$

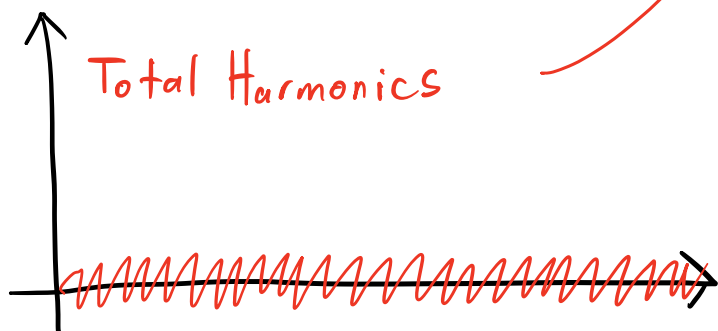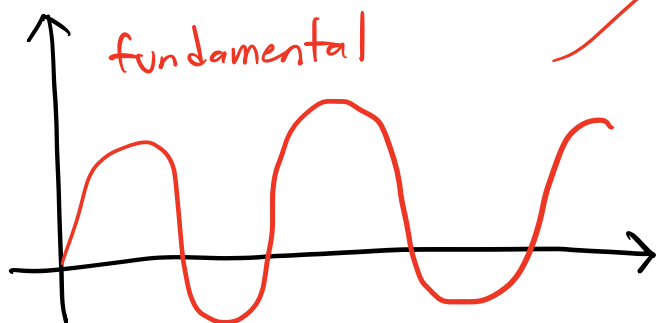


$$THD = \frac{\text{RMS of Total Harmonics}}{\text{RMS value of fundamental}}$$

- $THD \geq 0$
- No units

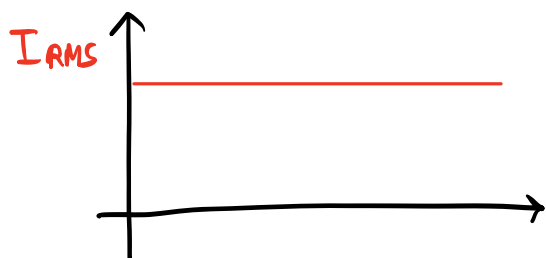


$$THD = \frac{\sqrt{I^2 - I_1^2}}{I_1}$$

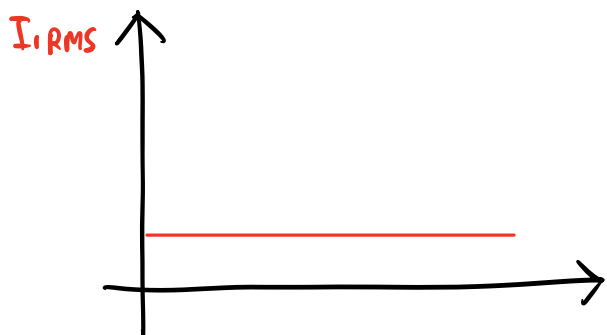



$$THD_v = \frac{\sqrt{V^2 - V_1^2}}{V_1}$$

For a perfect Sinusoid:

$$THD = 0$$

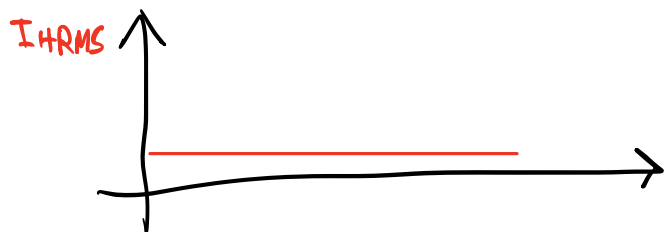

Ideal Diode:

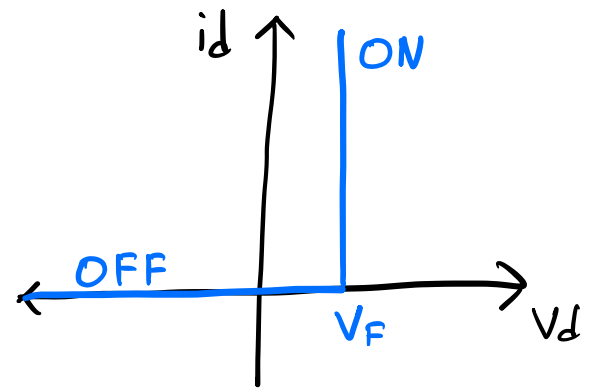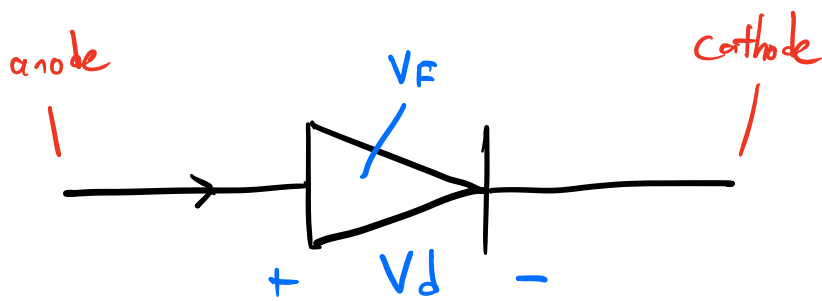


Conduction Losses:


$$P = IV$$

$$P_{\text{cond}} = i_d \cdot V_F \rightarrow 0 \text{ if Ideal}$$


Single Diode AC-DC Converter:

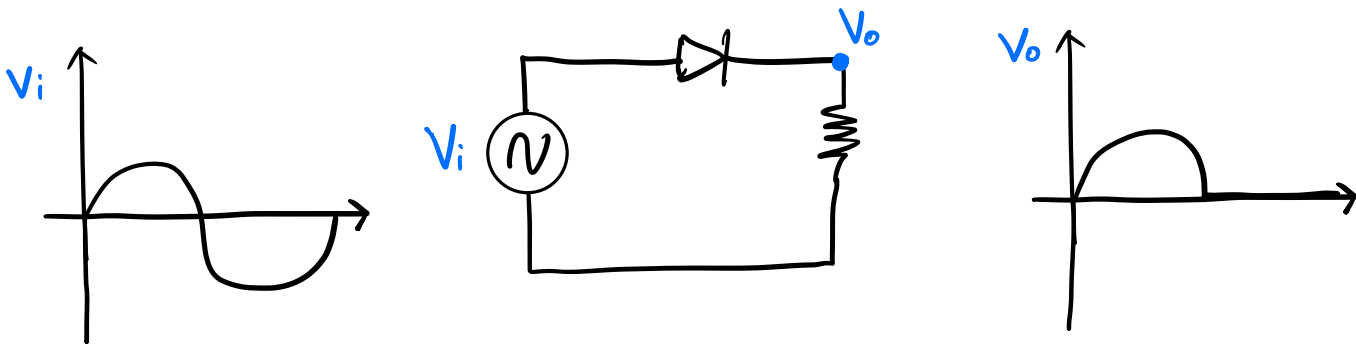

Diode and Capacitor AC-DC Converter:

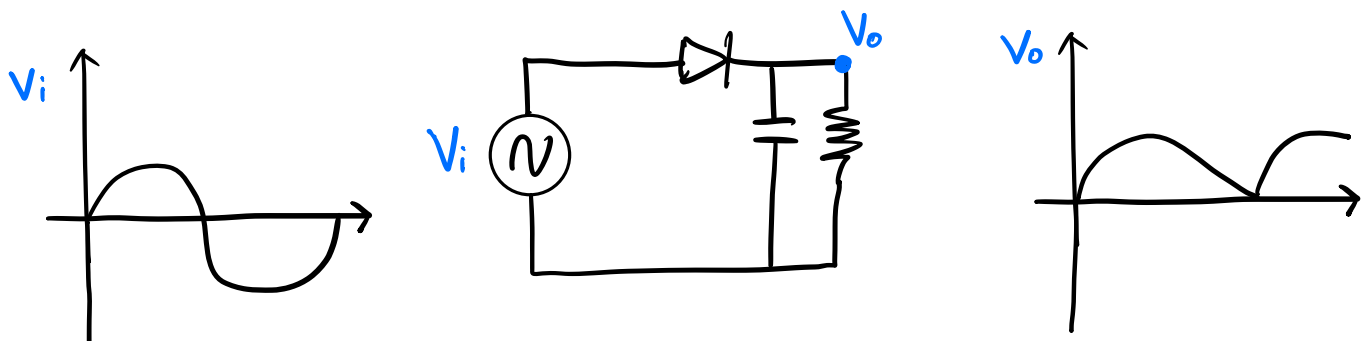

4 Diode Rectifier : Full-Bridge

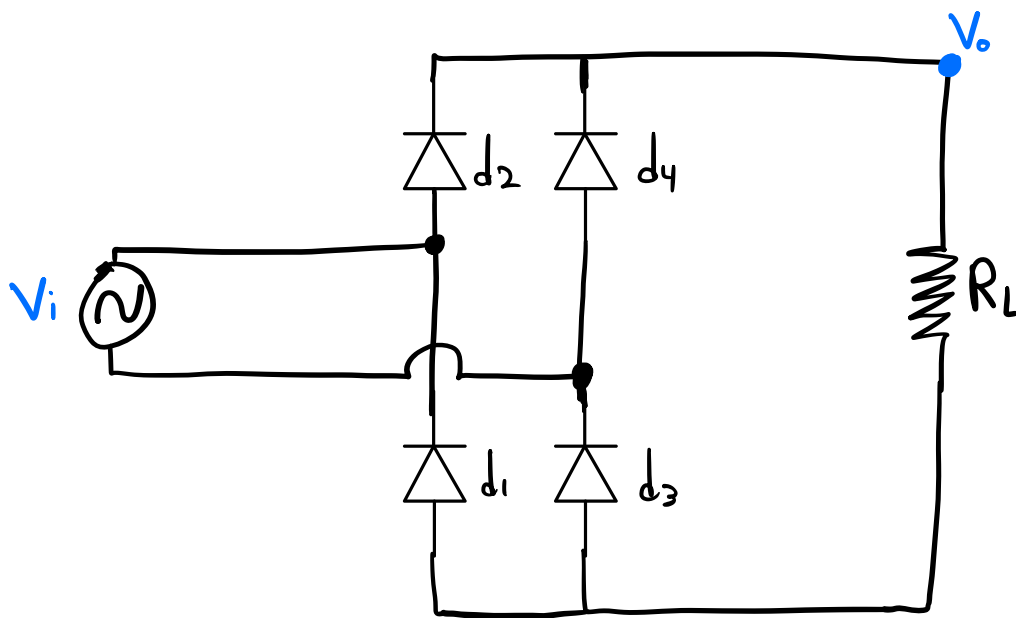

$$V_o = |V_i|$$

Positive Flow:

$D_2 \rightarrow D_3$


Negative Flow:

$D_4 \rightarrow D_1$


Legend:

Positive Cycle

Negative Cycle

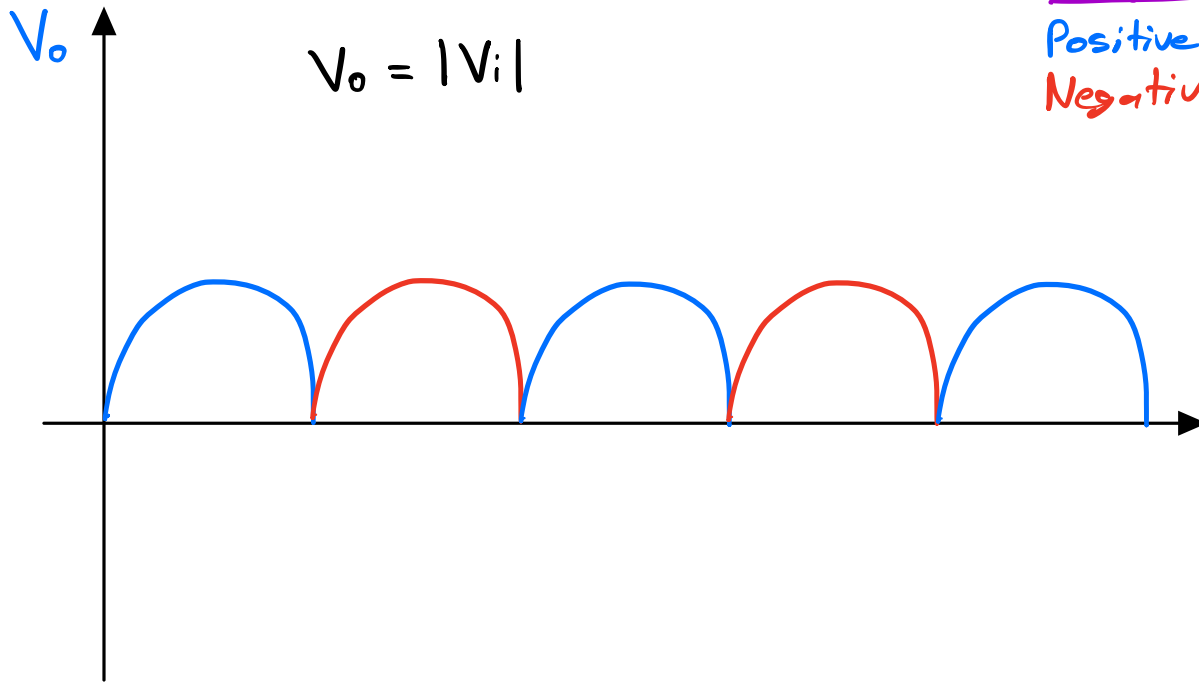

Full Bridge w/ Capacitor: Wave

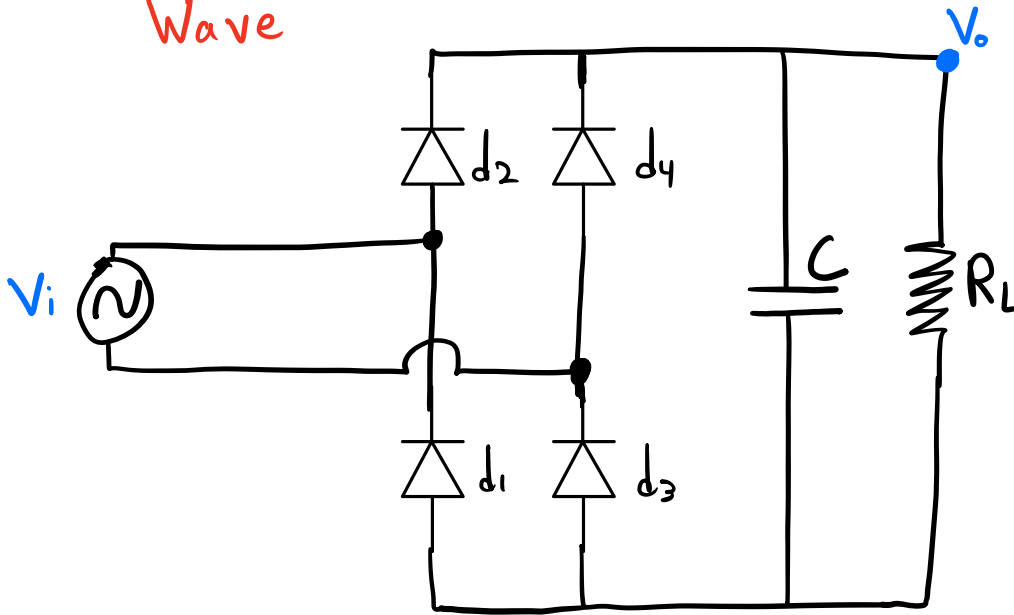

Positive Flow:

$D_2 \rightarrow D_3$

Negative Flow:

$D_4 \rightarrow D_1$


Regions:

① $d_2 \rightarrow d_3$



② RC CW (Cap discharge)

③ $d_4 \rightarrow d_1$ (Cap charge)

④ RC CW (Cap discharge)

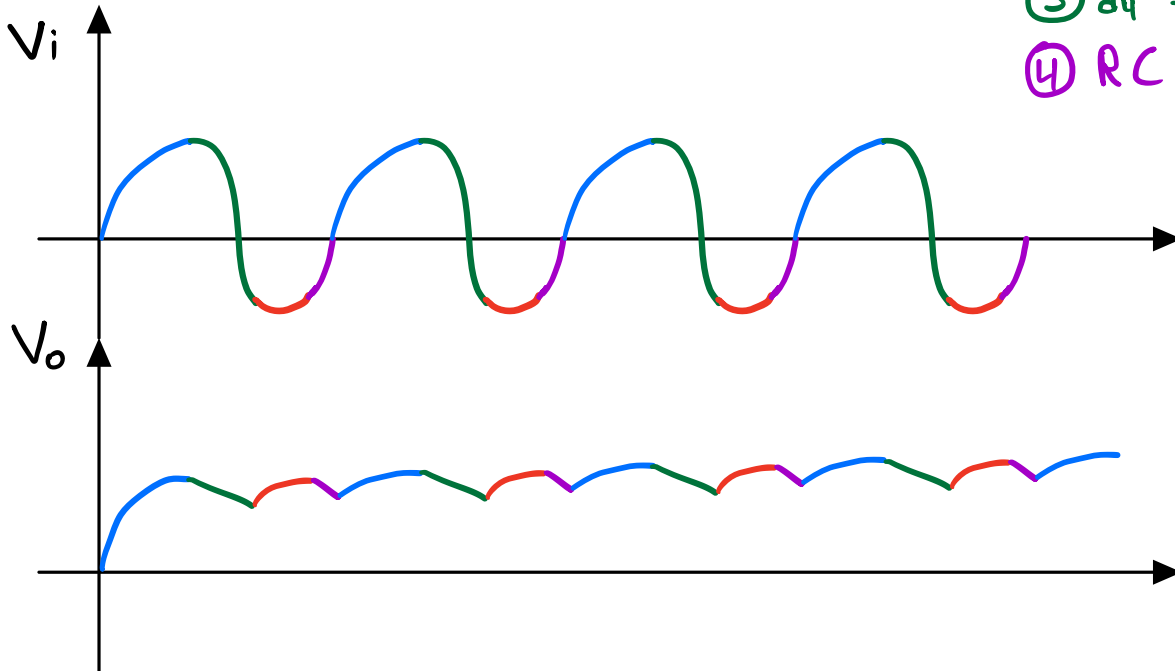

Half-Wave Rectifier w/capacitor:

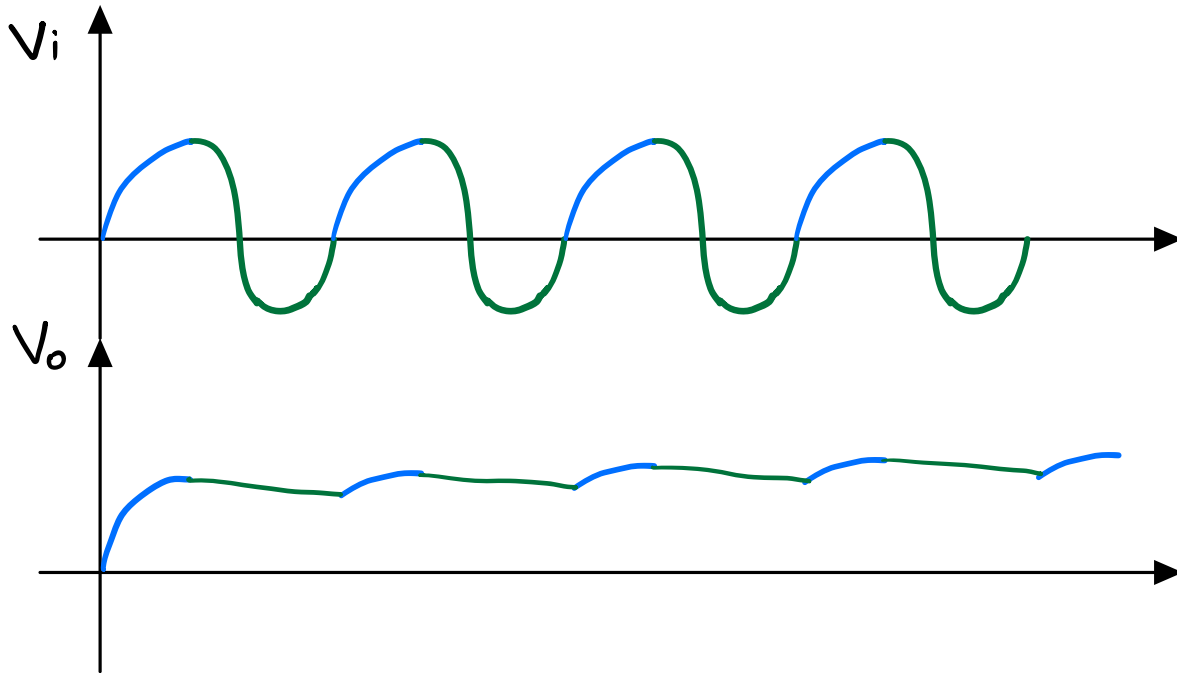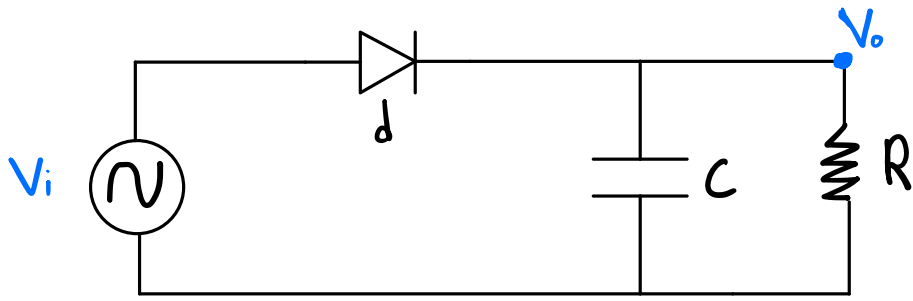

20