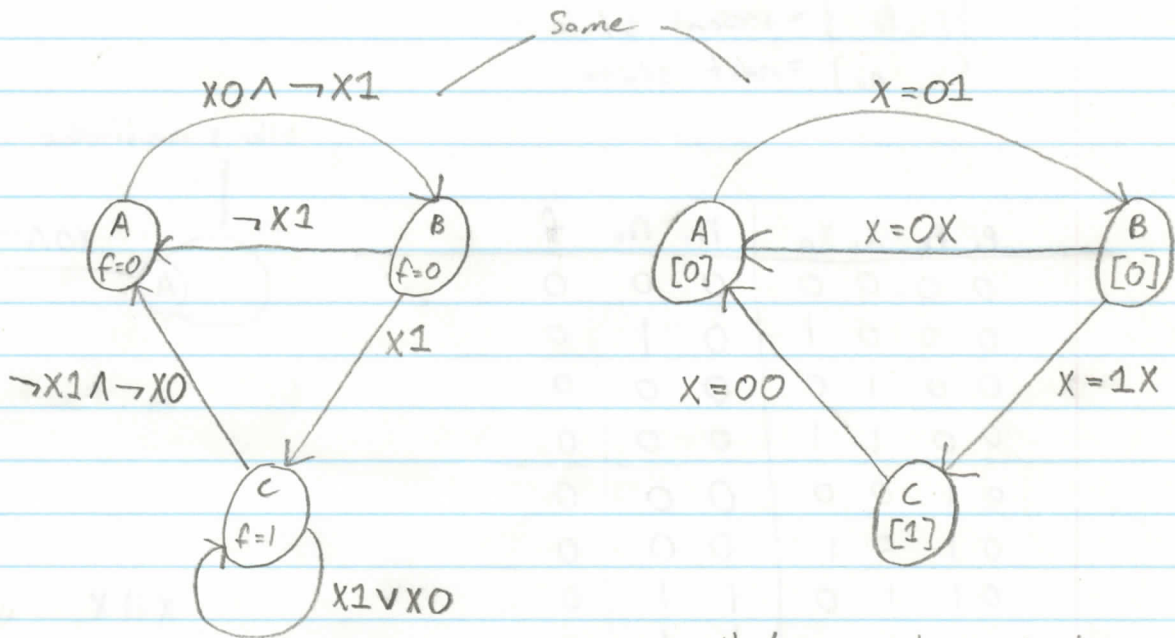


# Sequential Logic Flipped Lecture

Q3:

Create a digital circuit that implements the following finite state machine using a binary code for the states. Put your final answer in the form of a logic diagram using logic gates




What were trying to do :


## SOLUTION

Notes:


- circles are states
- arrows are edges
- X0 and X1 are inputs

$\square$  = Flip Flop

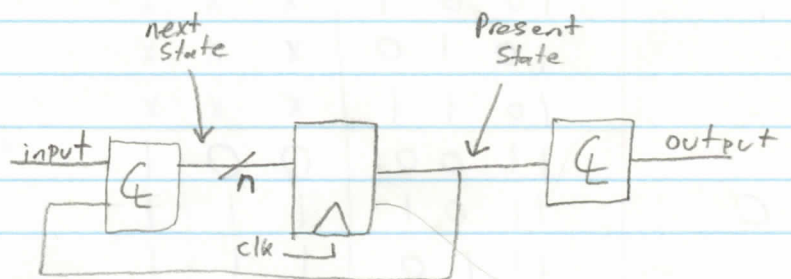

CLK   
"Transition on rising edge of the clock"

2 Flip Flops

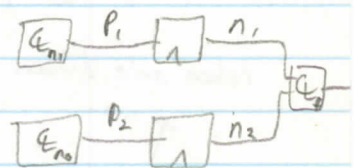

## Step 1: State assignment

A: 00


B: 01

C: 11

$\{p_1, p_0\}$  = present state

$\{n_1, n_0\}$  = next state

other 3 possibilities

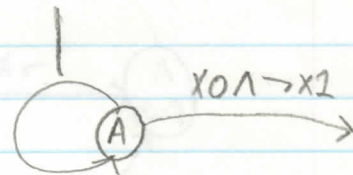

	$p_1, p_0$	$x_1, x_0$	$n_1, n_0$	$f$
A	0 0	0 0	0 0	0
	0 0	0 1	0 1	0
	0 0	1 0	0 0	0
	0 0	1 1	0 0	0
B	0 1	0 0	0 0	0
	0 1	0 1	0 0	0
	0 1	1 0	1 1	0
	0 1	1 1	1 1	0
?	1 0	0 0	x x	x
	1 0	0 1	x x	x
	1 0	1 0	x x	x
	1 0	1 1	x x	x
C	1 1	0 0	0 0	1
	1 1	0 1	1 1	1
	1 1	1 0	1 1	1
	1 1	1 1	1 1	1

$x_1 x_0$   
1 x x 1  
↑

$n_1$	00	01	11	10
00	0	0	0	0
01	0	0	1	1
11	0	1	1	1
10	X	X	X	X

reduce gate diagram

↑  
Same as  
 $n_1$   
 $x_0 0 1$

$n_0$	00	01	11	10
00	0	1	0	0
01	0	0	1	1
11	0	1	1	1
10	X	X	X	X

$f$	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	X	X	X	X

$1 x x x$

$A=00$   
 $B=01$   
 $C=11$   
 $D=10$

# Truth table

A

$p_1$	$p_2$	$u$	$v$	$n_1$	$n_2$	$s$	$t$
0	0	0	0	0	1	X	X
0	0	0	1	1	0	1	1
0	0	1	0	1	1	1	X
0	0	1	1	0	0	X	0
0	1	0	0	1	1	0	0

B

0	1	0	1	0	1	X	0
0	1	1	0	1	1	0	0
0	1	1	1	0	1	X	0

D

1	0	0	0	1	0	1	0
1	0	0	1	1	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	0	0	1

C

1	1	0	0	1	1	0	0
1	1	0	1	1	1	0	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	0	0

$n_1$   $uv$   
 $p_1 p_2$

0	1	0	1
1	0	0	1
1	1	1	1
1	1	0	0

$x001$   
 $0x10$   
 $x1x0$   
 $11xx$   
 $1x0x$

$s$   $uv$   
 $p_1 p_2$

X	1	X	1
0	X	X	0
0	0	0	0
1	1	0	0

$00xx$   
 $x00x$