
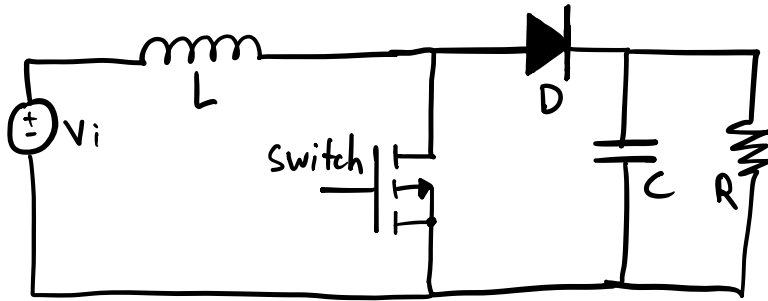


BOOST

Practical:

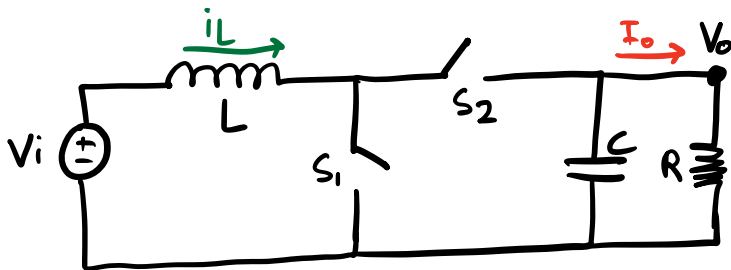

Ideal:



Case 1:

- Switch is ON, short circuit through the switch so $I_o = 0$. Inductor is being charged and will hold a voltage

Case 2:


- Switch is OFF, Diode is conducting,
 $V_o = V_i + V_L$


Case 3:

- Switch is ON, But diode is reverse biased. Inductor is being charged and we have a RC capacitor discharge circuit at the output

$$-T_{ON} = DT$$

$$-T_{OFF} = (1-D)T$$

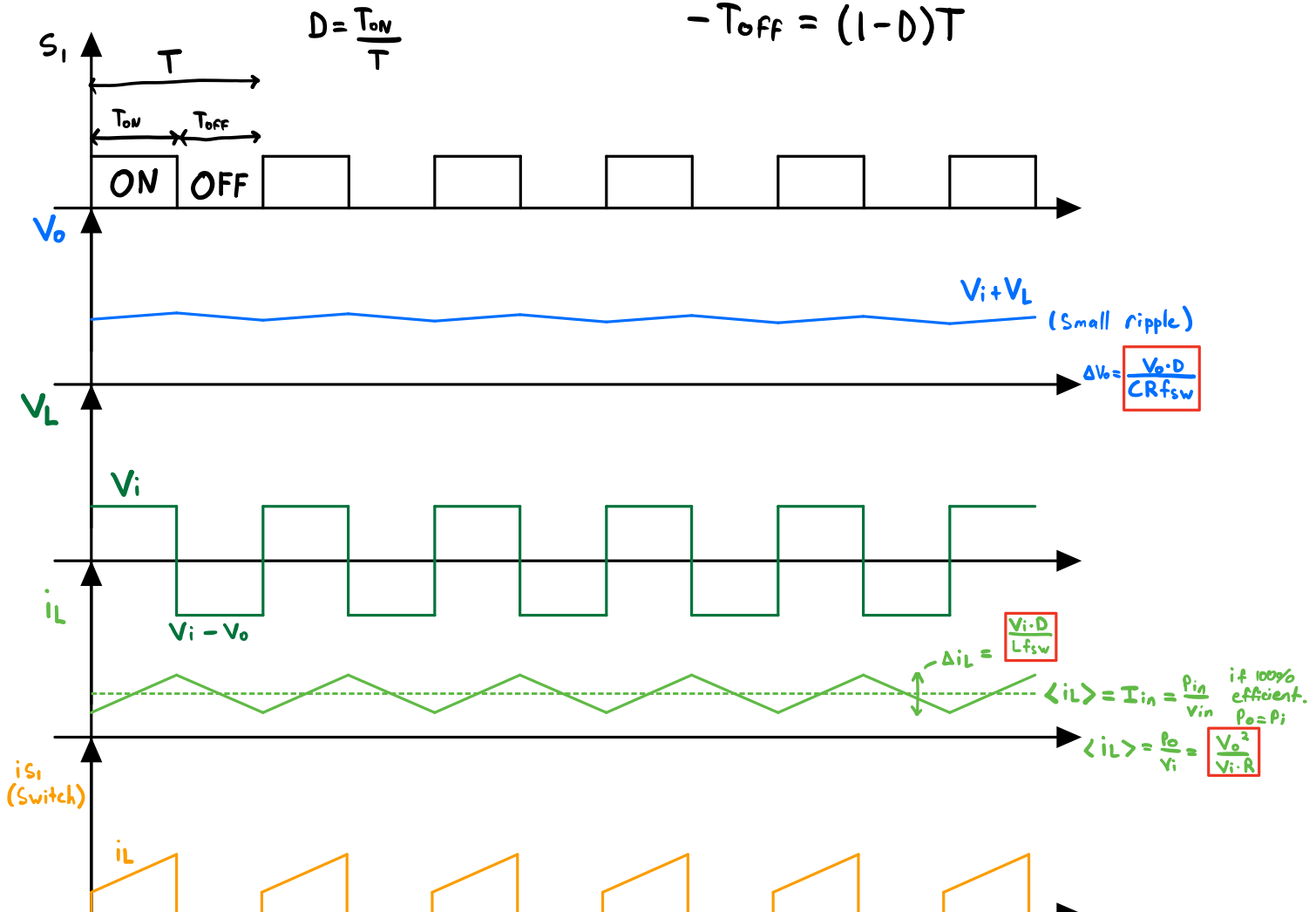

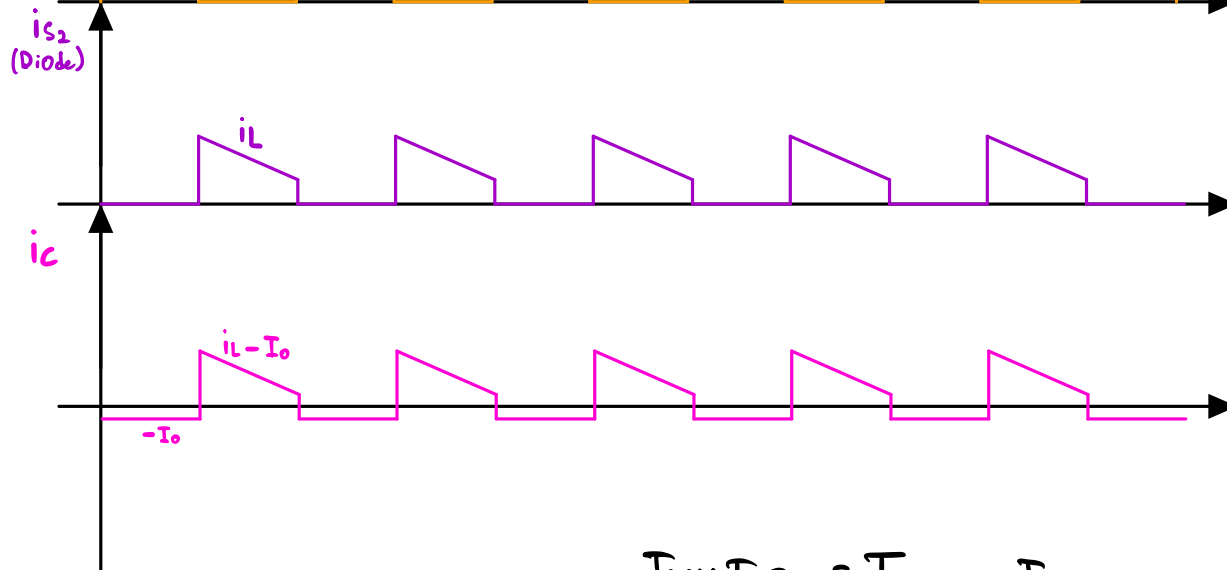

Gain Equation:

$$V_i \cdot T_{ON} = (V_o - V_i) T_{OFF}$$

$$T_{ON} + T_{OFF} = T$$

$$T_{OFF} = T - T_{ON}$$

$$\frac{T_{ON}}{T} = D$$

$$V_i T_{ON} = V_o T_{OFF} - V_i T_{OFF}$$

$$V_i D T = V_o (1-D) T - V_i (1-D) T$$

$$V_i D T = V_o T - V_o D T - V_i T + V_i D T$$


$$V_i T = V_o T - V_o D T$$

$$V_i = V_o - V_o D$$

$$V_i = V_o (1-D)$$



$$\frac{V_o}{V_i} = \frac{1}{(1-D)}$$

Discontinuous Conduction Mode:

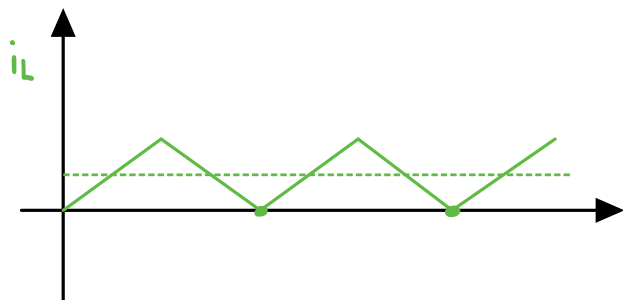

Occurs when $\langle i_L \rangle = \frac{\Delta i_L}{2}$

BUCK

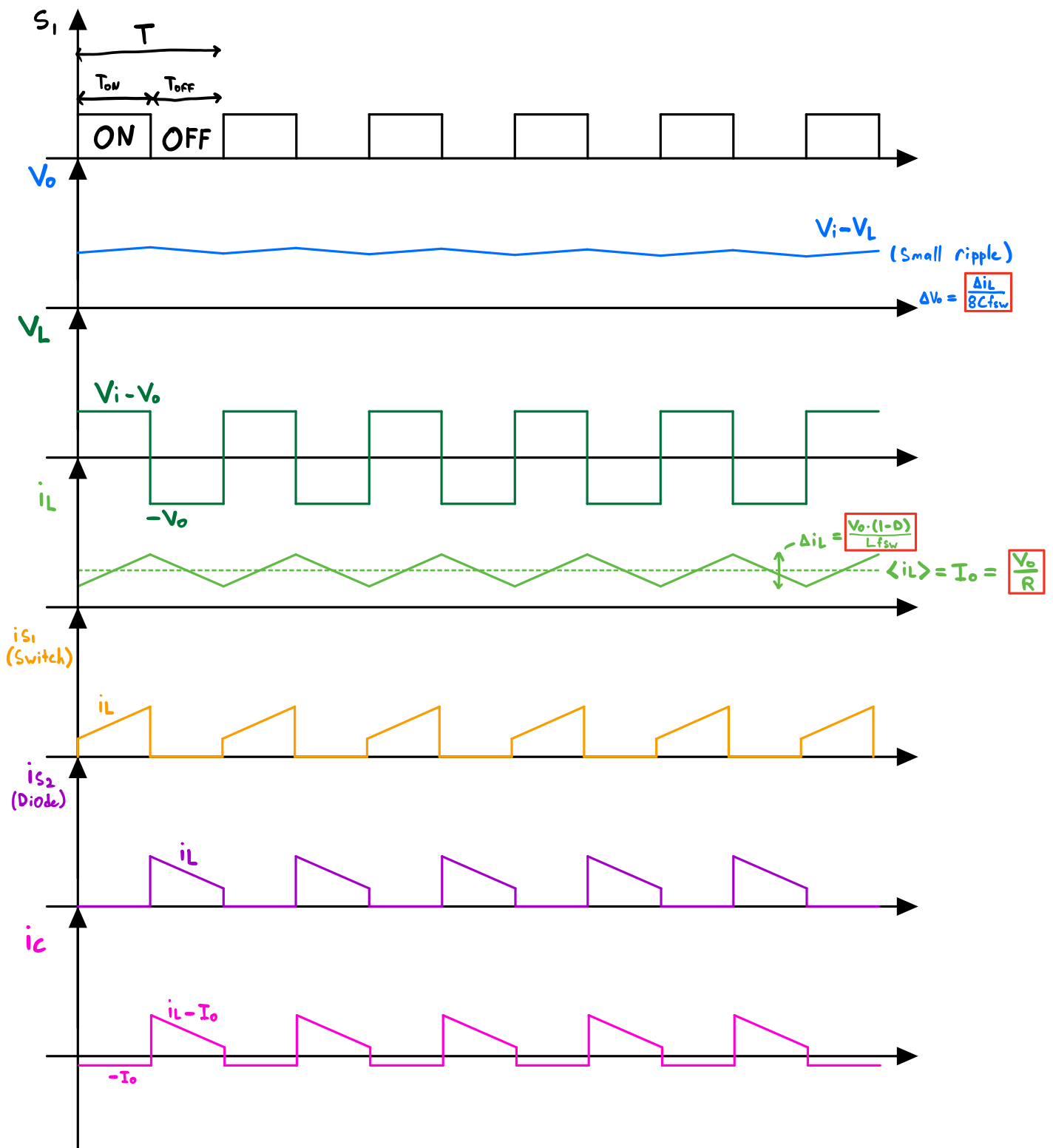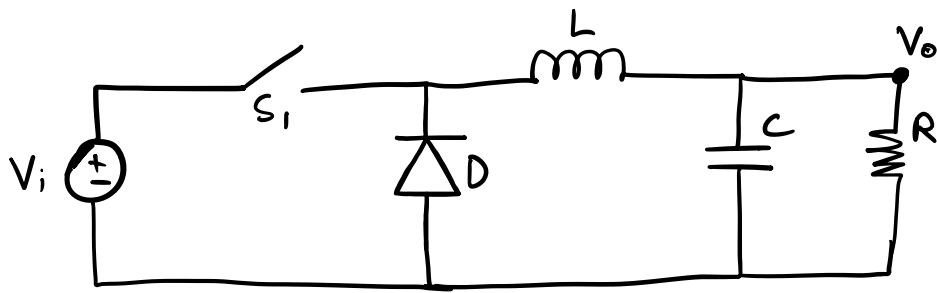

Gain Equation:



$$(V_i - V_o)DT = V_o(1-D)T$$


$$V_i DT - \cancel{V_o DT} = V_o T - \cancel{V_o DT}$$

$$V_i D = V_o$$

$$\frac{V_o}{V_i} = D$$

BUCK-BOOST

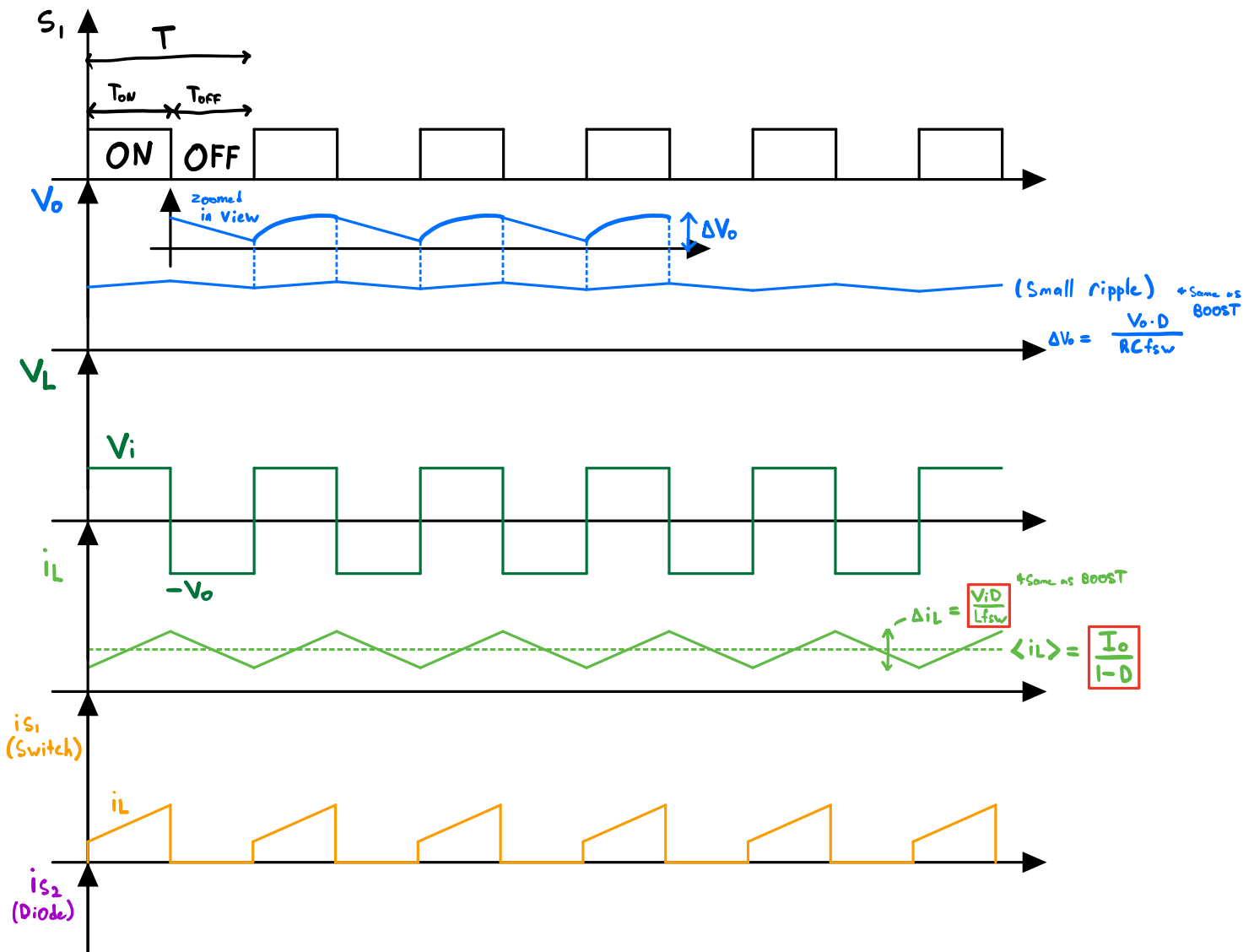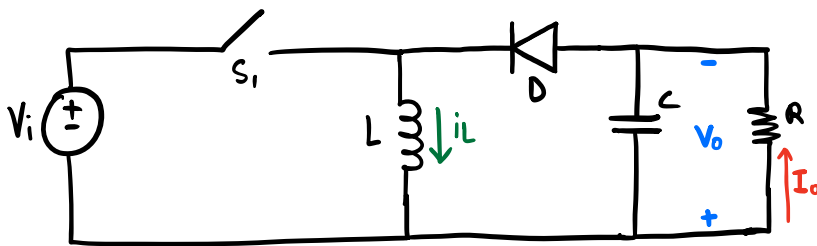

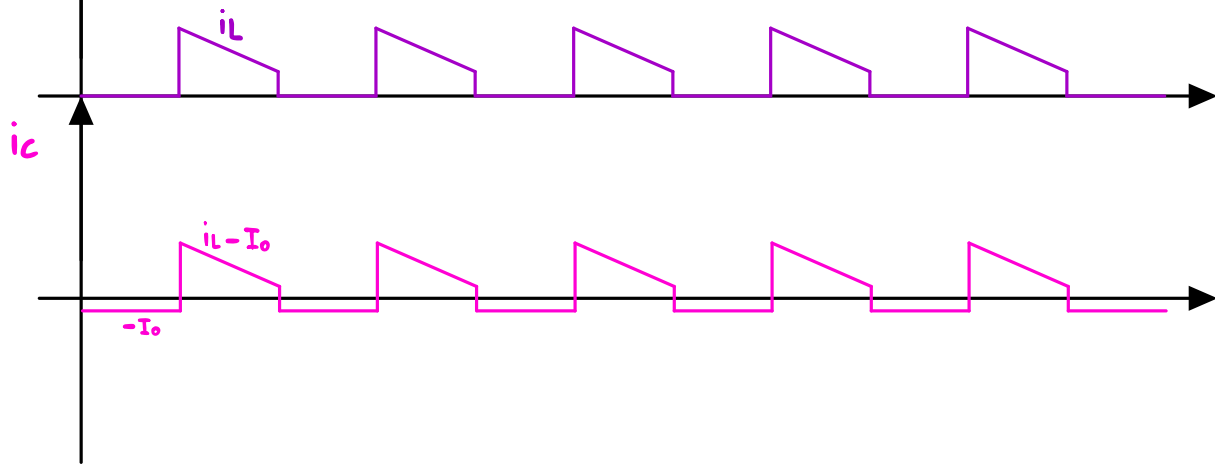

Gain Equation :

$$V_i D T = V_o (1-D) T$$

$$V_i D = V_o - V_o D$$

$$V_i D = V_o (1-D)$$

$$\frac{V_o}{V_i} = \frac{D}{(1-D)}$$