OPAMP Non-Idealities

November 19, 2017 21:09

Slew Rate: Maximum rate of change of output waveform:

$$SR = \left.\frac{dV_o}{dt}\right|_{max} = \omega_t V_i$$

ω_t ← max. frequency before distortion

Common-Mode Rejection Ratio

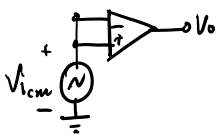

Ideally, $V_o = 0$.

But no, $\boxed{A_{cm} = \frac{V_o}{V_{icm}}}$

$CMRR = 20\log\left(\frac{|A_d|}{|A_{cm}|}\right)$, $A_{cm} = \frac{\Delta R_e}{2R}$, $V_d = -g_m R_c$