ELEC 201 Videos

Charge/Current/Voltage

Charge

$q_e = -1.602\times10^{-19}\,C$

$q_p = 1.602\times10^{-19}\,C$

q

- measured in Coulombs (C)

$q = \int_{t_1}^{t_2} i\,dt$

Current

i

- measured in A

ampere = C/s

Voltage

V

- measured in Volts
- Electric height

Volt = J/C

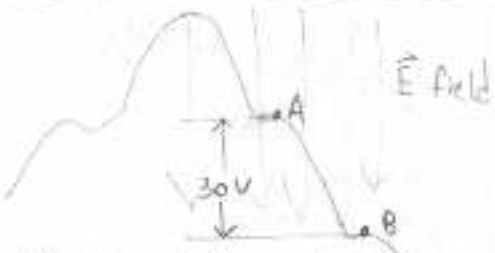

- if A and B are both 2C of charge
- A → B, delivers 30J of energy
- B → A, costs 30J of energy

Average Current

$q(t)$

- How many net C of charge have passed the checkpoint to the right at a given time

$i_{avg} = \frac{\Delta q}{\Delta t}$

Instantaneous Current

$i(t) = \lim_{\Delta t \to 0} \frac{\Delta q}{\Delta t}$

$i = \frac{dq}{dt}$

Energy

W

- measured in Joules

$W = \int_{t_1}^{t_2} Vi\,dt$

Power

P

- measured in Watts

Watt = J/s

$P = Vi$

$P = \frac{dW}{dt}$; $t = \frac{W}{Vi}$

$W = \int_{t_1}^{t_2} P\,dt$

Current flowing:

uphill → Delivering power

downhill → absorbing power

Tellegens theorem

$\sum P_{abs} - \sum P_{del} = 0$

- Total absorbed power equals total delivered power in a circuit

$P_{abs} = (V_a - V_b)\,i$

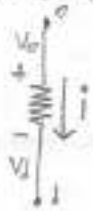

Circuits

Branch

- a link between two proper nodes
- may have zero or more binary nodes

Binary Node

- Does not affect the shape of the circuit

Atomic Branch

- Branch with no binary nodes

Branch

- The path that joins two true nodes. Atomic if no binary nodes inside

Binary Node

(True) Node

- 3 or more

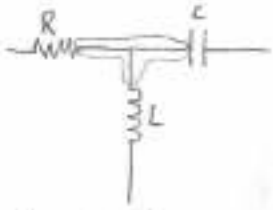

Series

- Elements in the same branch are in series

Parallel

① Both elements are in atomic branches

② Both atomic branches share the same true nodes. Must share both

Series/Parallel

- Two elements in series have the same current. <u>But</u> two elements that have the same current aren't necessarily in series
- Two elements in parallel have the same voltage but not the other way

Circuit with no true Nodes

- Promote one B-node to rank of true node (arbitrary)

Active Element

Battery, generator, etc, sources

Deliver power (usually)

Passive Element

Resistor, inductor, capacitor

Absorb power (sometimes)

Resistance

- resists currents i

Inductance

- resists changes in currents $\frac{di}{dt}$

Capacitance

- Resists changes in voltages $\frac{dV}{dt}$

Passive element

- Assume water falls down the sky

Ohm's Law

- R in ohms (Ω)

$\Omega = V/A$

① Resistance
② Power rating

Inductor

- L in Henrys (H)

$V = L\frac{di}{dt}$

① Inductance
② Current rating

Capacitor

- C in Farads (F)

$i = C\frac{dV}{dt}$; $V = \frac{q}{C}$

① Capacitance
② Voltage rating

Active (Sources)

Independent:

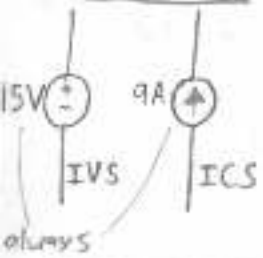

Dependent:

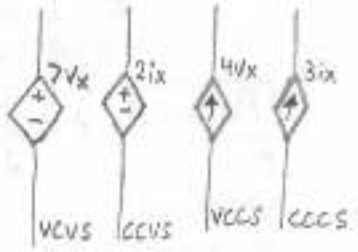

Kirchoff's Current Law

$\sum_{node} i_{in} = \sum_{node} i_{out}$ $\quad \sum_{Gauss} i_{in} = \sum_{Gauss} i_{out}$

$\sum_{Body} i_{in} = \sum_{Body} i_{out}$

Super Nodes

- gaussian surface that may cover many nodes

Inverses

Conductance:

$G = \frac{1}{R}$ - measured in Siemens

Inductance^{-1}:

$\Gamma = \frac{1}{L}$ - measured in H^{-1}

gamma

Capacitance^{-1}:

$T = \frac{1}{C}$ - measured in F^{-1}

Kirchoff's Voltage Law

$\sum_{loop} V_{up} = \sum_{loop} V_{down}$

- a loop is a closed path that only crosses a node once, ie: arrive in it and leave out of it

Window pane (Mesh)

- a loop that does not contain any loops inside

Addition Simplification

$R_{eq} = R_1 + R_2 \ldots + R_n$ SERIES

$L_{eq} = L_1 + L_2 \ldots + L_n$ SERIES

$V_{source} = V_1 + V_2 \ldots + V_n$ SERIES

$C_{eq} = C_1 + C_2 \ldots + C_n$ PARALLEL

$i_{source} = i_1 + i_2 \ldots + i_n$ PARALLEL

Inverse Simplification

$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} \ldots + \frac{1}{R_n}\right)^{-1}$ PARALLEL

$L_{eq} = \left(\frac{1}{L_1} + \frac{1}{L_2} \ldots + \frac{1}{L_n}\right)^{-1}$ PARALLEL

$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} \ldots + \frac{1}{C_n}\right)^{-1}$ SERIES

midterm demonstrate not on slides

Neither in Series/Parallel

Triangle/Delta/Pi Config:

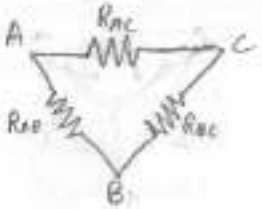

Star/Wye/tee config:

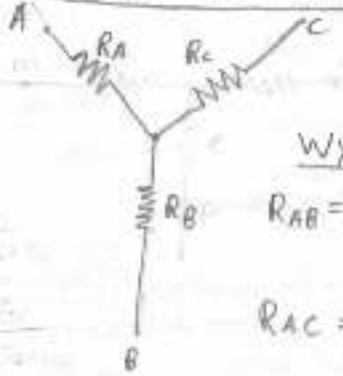

Δ Delta → Wye (Y):

$R_A = \frac{R_{AB}R_{AC}}{R_{AB}+R_{AC}+R_{BC}}$

$R_B = \frac{R_{AB}R_{BC}}{R_{AB}+R_{AC}+R_{BC}}$

$R_C = \frac{R_{AC}R_{BC}}{R_{AB}+R_{AC}+R_{BC}}$

Wye (Y) → Δ Delta:

$R_{AB} = \frac{R_AR_B + R_AR_C + R_BR_C}{R_C}$

$R_{AC} = \frac{R_AR_B + R_AR_C + R_BR_C}{R_B}$

$R_{BC} = \frac{R_AR_B + R_AR_C + R_BR_C}{R_A}$

Source Transformations

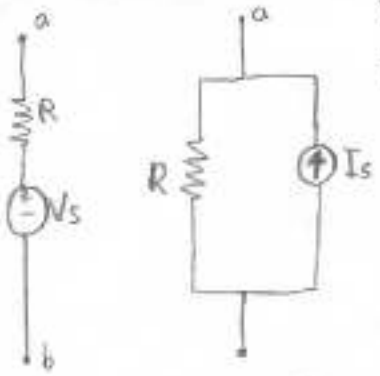

$V_S = R I_S$

$I_S = \frac{V_S}{R}$

Voltage Divider

$V_1 = R_1 I$

$V_2 = R_2 I$

$V_{ab} = V_2 + V_1$

$V_{ab} = I(R_2 + R_1)$

$\frac{V_1}{V_{ab}} = \frac{R_1}{R_{eq}}$ "Same %"

Superposition

killing a Vsource:

killing a Isource:

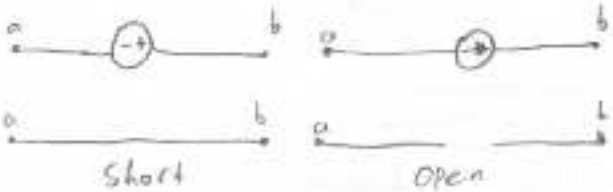

Current Divider

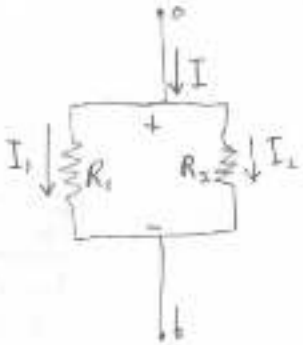

$I_1 = \frac{V_{ab}}{R_1}$

$I_2 = \frac{V_{ab}}{R_2}$

$I = \frac{V_{ab}}{R_1} + \frac{V_{ab}}{R_2} \left(\frac{1}{R_1} + \frac{1}{R_2}\right) V_{ab}$

$\frac{I_1}{I} = \frac{R_2}{R_1 + R_2}$ "Same %"

$\frac{I_1}{I} = \frac{G_1}{G_1 + G_2}$

Modified Nodal Analysis

Controlling Variable:

- 3ix is a controlling variable

Evil currents:

- currents in evil branches

Thenevin and Norton Equivilants

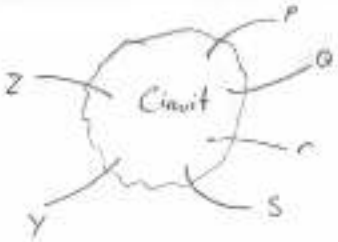

Two nodes = one port (could be binary or trive)

Solution Method

1. Choose REF node
2. Choose R/RV current directions
3. Label every true node (KCL)
4. Label every evil current (EVL)
5. Label every controlling variable (CTL)

(4) New ideal Circuit Elements

Open circuit:

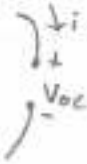

Short circuit:

Ammeter:

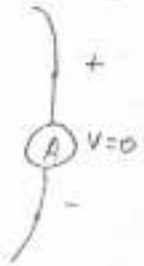

Voltmeter:

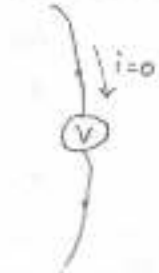

Classic Method

Open Circuit test:

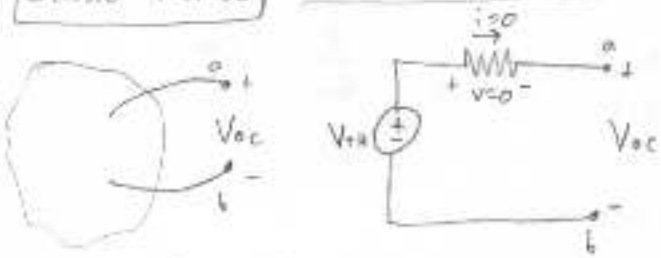

$V_{TH} = V_{oc}$

Short circuit test:

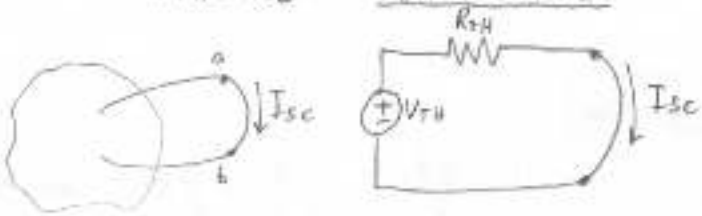

$I_{sc} = \frac{V_{TH}}{R_{TH}}$

$R_{TH} = \frac{V_{TH}}{I_{sc}}$

Kill Sources (All independent)

- Find $R_{eq} = R_{TH}$

Only Controlled Sources

$V_{oc} = 0$

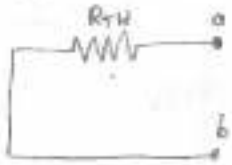

How.....:

only a 1Amp current between the nodes, solve for R_{TH}

Two Resistors Method

"In real life its dangerous to apply Short circuit test"

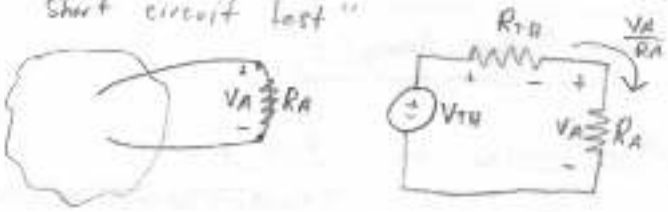

"Do this again with a second Resistor R_B"

SOLVE for V_{TH}, R_{TH}

$V_{TH} - R_{TH}\frac{V_A}{R_A} = V_A$

$V_{TH} - R_{TH}\frac{V_B}{R_B} = V_B$

Norton Mayer Equivalent

Short circuit test:

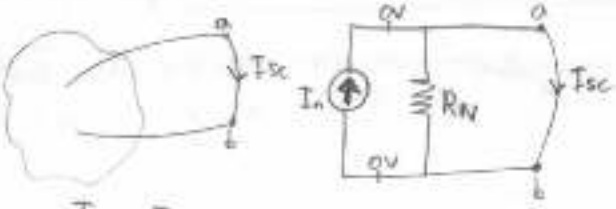

$I_N = I_{sc}$

Open circuit test:

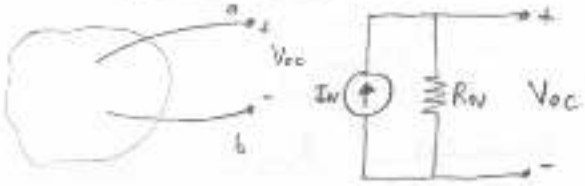

$V_{oc} = R_N I_N$

$R_N = \frac{V_{oc}}{I_n}$

$R_n = \frac{V_{oc}}{I_{sc}}$

1A/2A (UBC) Method

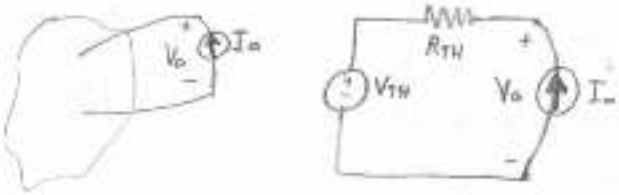

"Repeat with new Iwire

$V_{th} + R_{th} I_a - V_a = 0$

$V_{th} + R_{th} I_b - V_b = 0$

Max Power Criterion

$P_{MAX} = \frac{V_{th}^2}{4R_{th}}$

$P_{MAX} = \frac{I_{sc}^2 R_{th}}{4}$

First order Circuits

RL Circuit

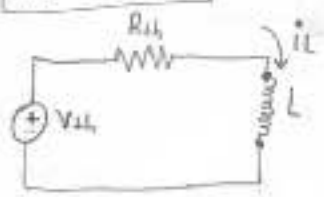

DE: $L\frac{di_L}{dt} + Ri_L = V_s$

Sol'n: $i_L(t) = \left(I_0 - \frac{V_s}{R}\right)e^{-t/\left(\frac{L}{R}\right)} + \frac{V_s}{R}$

RC Circuit

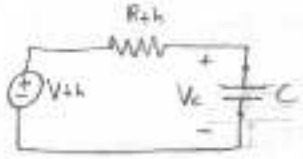

DE: $RC\frac{dV_c}{dt} + V_c = V_{th}$

Sol'n: $V_c(t) = (V_{c_0} - V_{th})e^{-t/RC} + V_{th}$

Impedance

$Z_L = Lp$ $\quad * p = \frac{d}{dt}$ (s^{-1})

$Z_C = \frac{1}{Cp}$

$Z_r = R$

General Ohm's Law:

$V = Z \cdot i$

volts, impedance, current

R/L/C Impedance

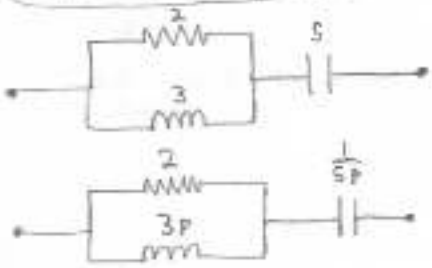

Right after we move a switch $t = 0^+$

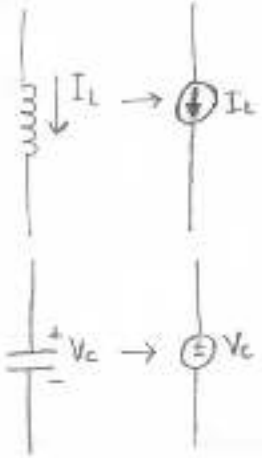

Capacitor where V_0 is initial voltage

$V_C = V_0 e^{-t/RC}$

$Q = CV_0 e^{-t/RC}$

$I = \frac{V_0}{R_{th}} e^{-t/RC}$

Inductor where V_b is final voltage

$V_L = V_b e^{-tR/L}$

$I = \frac{V_b}{R}(1 - e^{-tR/L})$

$V_C(t) = (V_{C0} - V_{Cf})e^{-t/RC} + V_{Cf}$

$I_L(t) = (I_{L0} - I_{Lf})e^{-tR/L} + I_{Lf}$

where V_{C0} and I_{L0} are DCSS of both

$V_{Cf} = V_{TH}$ seen by capacitor

$I_{Lf} = I_N$ seen by inductor

Operational Amplifiers

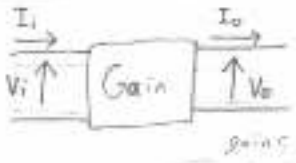

$A_V = \frac{V_o}{V_i}$ (V/V) $\quad A_I = \frac{I_o}{I_i}$ (A/A) $\quad A_P = \frac{P_o}{P_i}$ (W/W)

$A_V^{DB} = 20\log_{10}\left|\frac{V_o}{V_i}\right|$ $\quad A_I^{DB} = 20\log_{10}\left|\frac{I_o}{I_i}\right|$ $\quad A_P^{DB} = 10\log_{10}\left|\frac{P_o}{P_i}\right|$

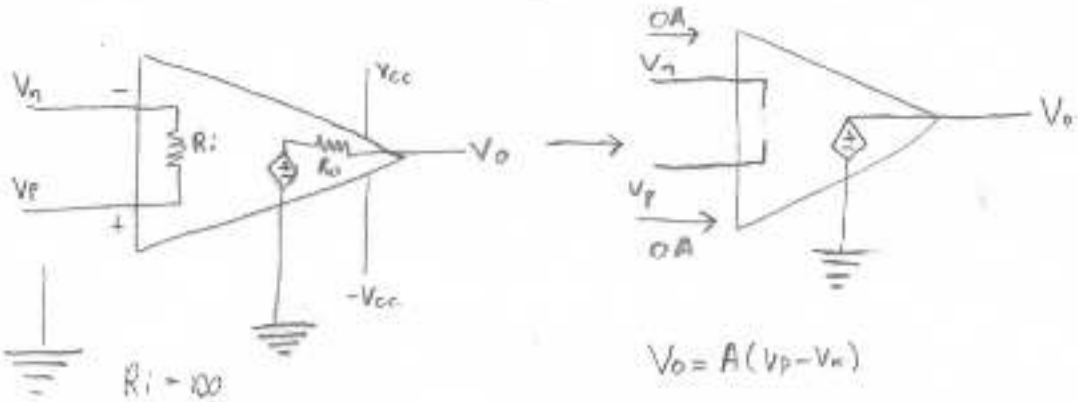

$V_o = A(V_p - V_n)$

$R_i = \infty$

$R_o = 0$

$A = \infty$ (voltage gain)

Negative feedback

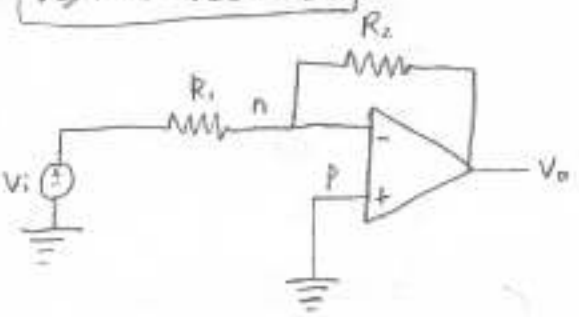

$V_p = V_n$

- as long as no saturation

- connecting the output to the inverting input by passive elements

Inverting amplifier

$V_p = V_n$

$V_p = 0$

- Don't write a KCL for V_o

$n: \frac{V_i - V_n}{R_1} = 0 + \frac{V_n - V_o}{R_2}$

$\therefore V_o = -\frac{R_2}{R_1} V_i$

Ideal Diode

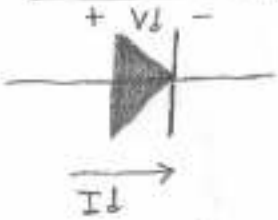

$I_d = I_o e^{V_D/V_T}$ — constant

Saturation

$-V_{cc} \le V_o \le +V_{cc}$

Positive Saturated $\rightarrow V_o = +V_{cc}$, $V_p > V_n$

Negative Saturated $\rightarrow V_o = -V_{cc}$, $V_p < V_n$

Non-Inverting Amplifier

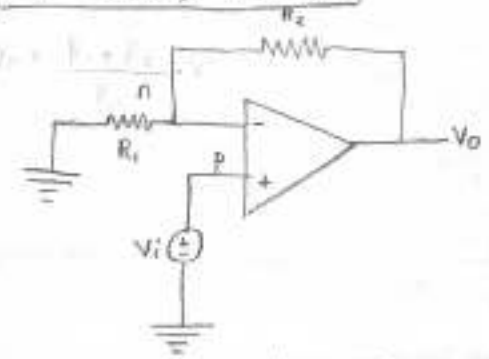

$V_p = V_n$

$V_p = V_i$

$n: \frac{V_o - V_n}{R_2} = 0 + \frac{V_n}{R_1}$

$\therefore V_o = \frac{R_1 + R_2}{R_1} \cdot V_i$

Rectifier Circuits

Types of Rectifiers

1. Half-Wave
2. Full-Wave:
   - Center tap
   - Bridge type

Half Wave Rectifier

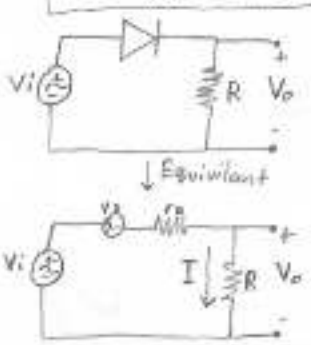

$$I = \frac{V_i - V_D}{R + r_D}$$

$$V_o = R\left(\frac{V_i - V_D}{R + r_D}\right)$$

Full Wave Bridge Rectifier

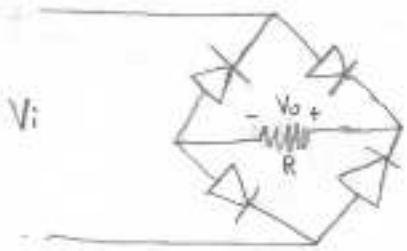

Zener diodes as Shunt Voltage regulators

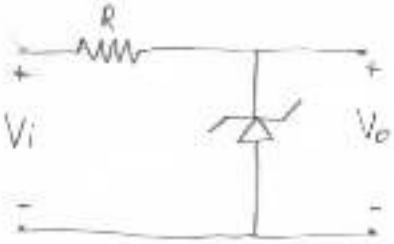

Line regulation $= \frac{\Delta V_o}{\Delta V_{in}}$

Load regulation $= \left|\frac{\Delta V_o}{\Delta I_L}\right|$

Rectifier Circuit with resistive load

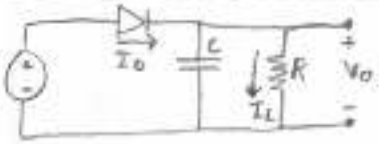

For Half Wave:

$$V_r = \frac{V_p T}{RC} = \frac{V_p}{fRC} = \frac{I_L}{fC}$$

For Full wave:

$$V_r = \frac{V_p T}{2RC} = \frac{V_p}{2fRC} = \frac{I_L}{2fC}$$

Load Voltage:

$$V_L = V_p - \frac{1}{2}V_r$$

Load Current:

$$I_L = \frac{V_L}{R_L}$$

When ripple is small $I_L = \frac{V_p}{R_L}$

Diodes

Ideal diode

- Allows current to flow in one direction
- No voltage drop across terminals when allowing current to flow

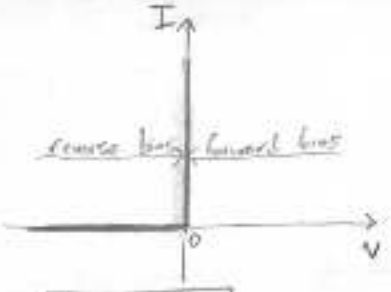

Real diode

- Allows a small amount of reverse current
- Has a small voltage drop when current flowing

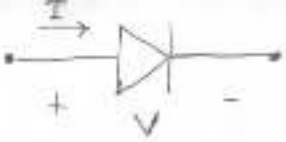

(2) modes of operation:

① Reverse bias $V<0, I=0$, behaves like open circuit

② Forward bias: $V=0, I>0$, behaves like short circuit

$$i = I_s\left(e^{\frac{v}{nV_T}}-1\right)$$

where: i = current through the diode
v = voltage across the diode
I_s = reverse saturation current, very small usually $10^{-13}A$ or $10^{-15}A$
n = empirical constant
V_T = Thermal voltage

$$V_T = \frac{kT}{q}$$

where: k = Boltzmann's constant
T = absolute temperature
q = base charge

Models

① Ideal Model
② Exponential Model
③ Constant Voltage Drop
④ Piecewise linear
⑤ Small signal Model

Ideal Model

- Try all possibilities
- 2^n possibilities where n is the number of diodes

Equation Model

- Make a system of equations
- Most accurate
- Hard without a calculator
- Also called the exponential model

Constant Voltage Drop

- The diode can be replaced with an ideal diode and voltage source in series

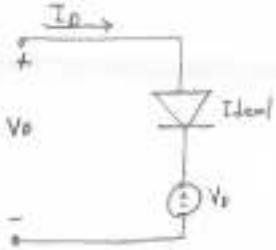

Piecewise Linear Model

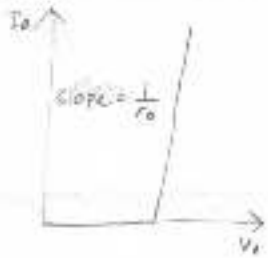

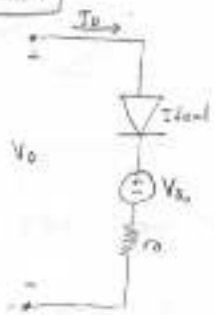

$$\frac{1}{r_D} = \frac{1mA - 0mA}{0.7V - V_{D0}}$$

- To Find V_{D0}

Small Signal Model

① Solve the operating point of the diode in the DC circuit.

To get DC:

- Short all AC voltage sources
- Open all AC current sources
- Short all inductors
- Open all capacitors

② Replace diode with its small signal equivalent in AC circuit

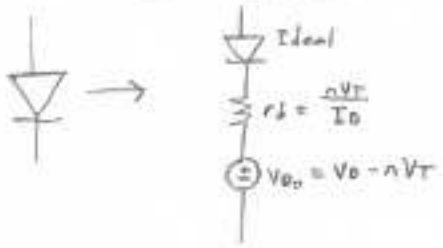

To get AC:

- Short all DC voltage sources
- open all DC current sources
- open all inductors
- Short all capacitors

Zener diode

- allows current to flow in reverse at certain voltage

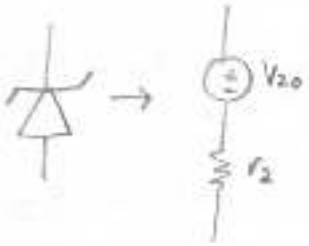

$$V_{Z0} = V_Z - r_Z I_Z$$

BJT's

NPN transistor

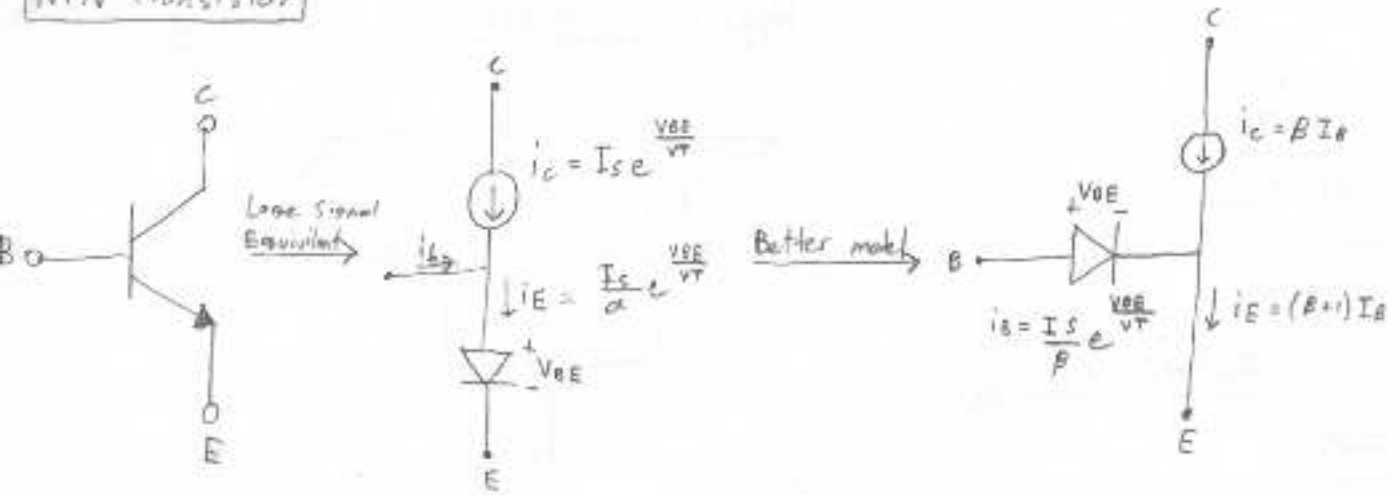

PNP Transistor

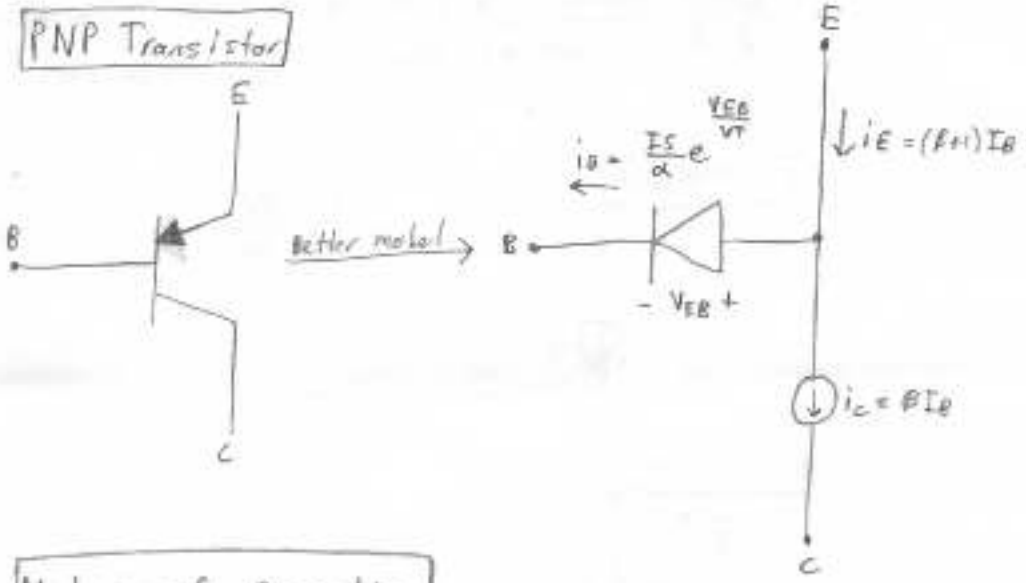

* only work in active region

Modes of Operation

BJT Mode	Collector Current (I_c)
Cutoff →	$i_c = 0$
Active →	$i_c = \beta \cdot I_B$
Saturation →	$i_c < \beta \cdot I_B$

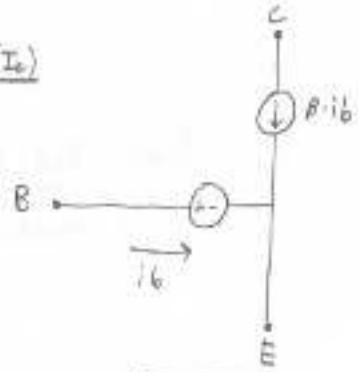

ACTIVE

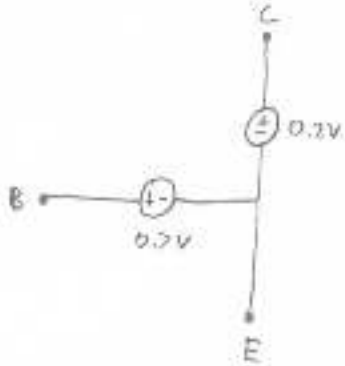

SATURATION

Relationships

$I_E = I_B + I_c$

$I_c = \beta \cdot I_B$

$I_c = \alpha \cdot I_E$

$\alpha = \frac{\beta}{\beta+1}$ $\beta = \frac{\alpha}{1-\alpha}$

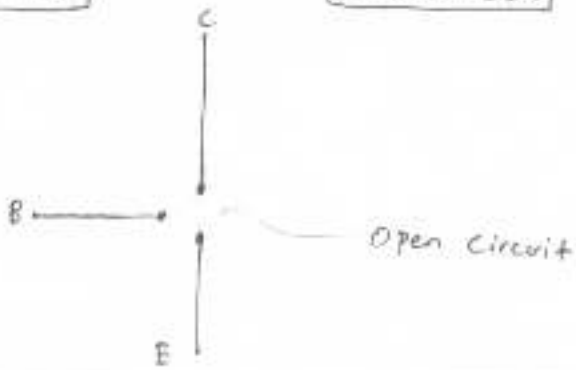

BJT Amplifiers

Steps:

① Get DC circuit:
- Short all AC Vsources
- Open all AC Isources
- open all capacitors
- Short all inductors

② Solve circuit for I_c, r_π (or r_e), g_m:

③ Get AC circuit:
- replace transistor with hybrid-π circuit
- Short all DC Vsources
- Open all DC Isources
- Short all capacitors
- open all inductors

④ Solve AC circuit for (gain)

Models

$$g_m = \frac{I_c}{V_T}$$

$$r_\pi = \frac{\beta}{g_m}$$

Hybrid-π model:

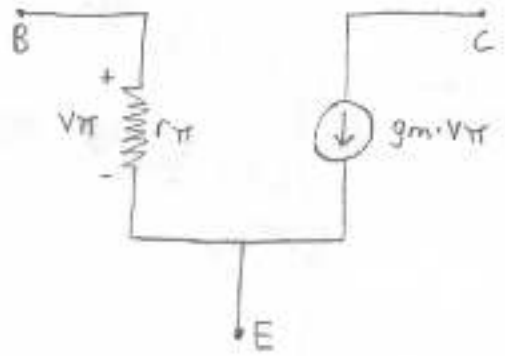

Input Resistance (R_i) → use hybrid-π model if R_i is measured from the base. (use r_π)

T-model:

$$r_e = \frac{\alpha}{g_m}$$

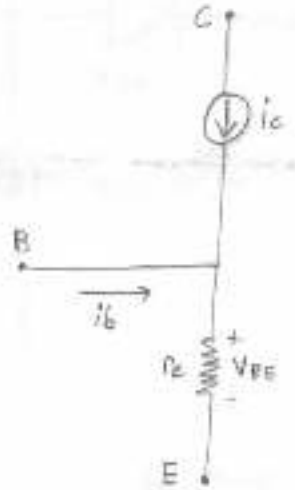

Input Resistance (R_i) → use T-model if R_i is measured from the base. (use r_e)

MOSFET

Enhancement N-MOSFET

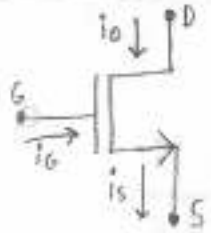

Triode Region $V_{DS} < V_{GS} - V_t$

$$i_D = i_S = k_n' \frac{W}{L}\left[(V_{GS} - V_t)V_{DS} - \frac{1}{2}V_{DS}^2\right]$$

Saturation Region $V_{DS} > V_{GS} - V_t$

$$i_D = i_S = \frac{1}{2} k_n' \frac{W}{L}(V_{GS} - V_t)^2$$

Cutoff Region $V_{GS} < V_t$

$$i_D = 0$$

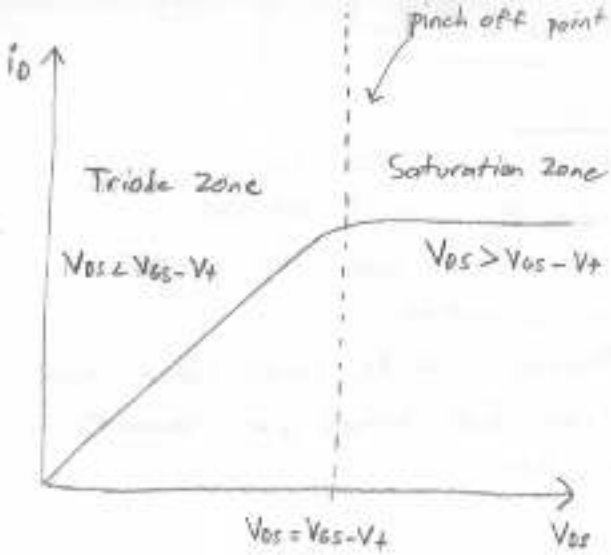

Small V_{DS} Assumption $V_{DS} < 0.2V$

*in Triode Region

$$i_D \approx k_n' \frac{W}{L}\left[(V_{GS} - V_t)V_{DS}\right]$$

<u>where</u>: $i_D \approx \frac{1}{r_{DS}} \cdot V_{DS}$

$$r_{DS} = \frac{1}{\mu_n C_{ox} \frac{W}{L}(V_{GS} - V_t)}$$

Enhancement P-MOSFET

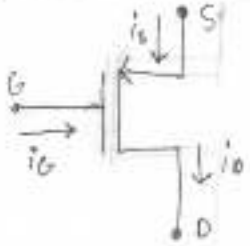

Triode Region $|V_{DS}| < |V_{GS} - V_t|$

$$i_D = i_S = k_p' \frac{W}{L}\left[(|V_{GS} - V_t|)|V_{DS}| - \frac{1}{2}V_{DS}^2\right]$$

Saturation Region $|V_{DS}| > |V_{GS} - V_t|$

$$i_D = i_S = \frac{1}{2} k_n' \frac{W}{L}(V_{GS} - V_t)^2$$

*<u>with Early Voltage</u>:

$\lambda = \frac{1}{V_A}$ where $V_A \neq \infty$

$$i_D = i_S = \frac{1}{2} k_n' \frac{W}{L}(V_{GS} - V_t)^2(1 + |\lambda||V_{DS}|)$$

Cutoff Region $|V_{GS}| < |V_t|$

$$i_D = i_G = i_S = 0$$

Large Signal Model

*Enhancement N-MOSFET in Saturation mode

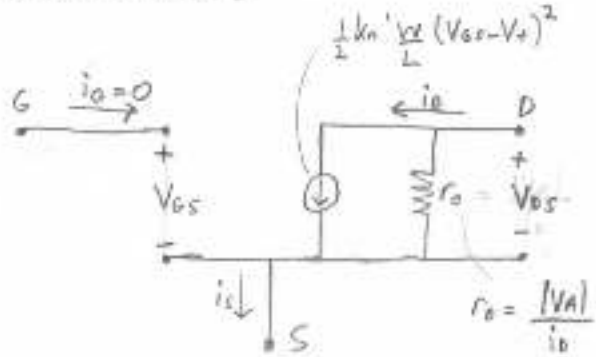

AC and DC Analysis

Steps:

1. Replace with DC circuit
2. Solve DC circuit for V_{GS}, i_D, V_{DS}. Make sure the MOSFET is in saturation
3. Replace with AC small signal model
4. Solve for Voltage gain / current gain, etc

AC Small signal model

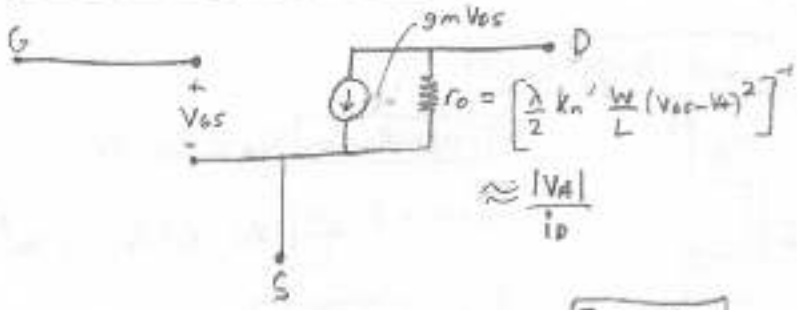

Formulas

$\lambda = \frac{1}{V_A}$

$g_m = k_n' \frac{W}{L}(V_{GS}-V_t)$