Full Bridge

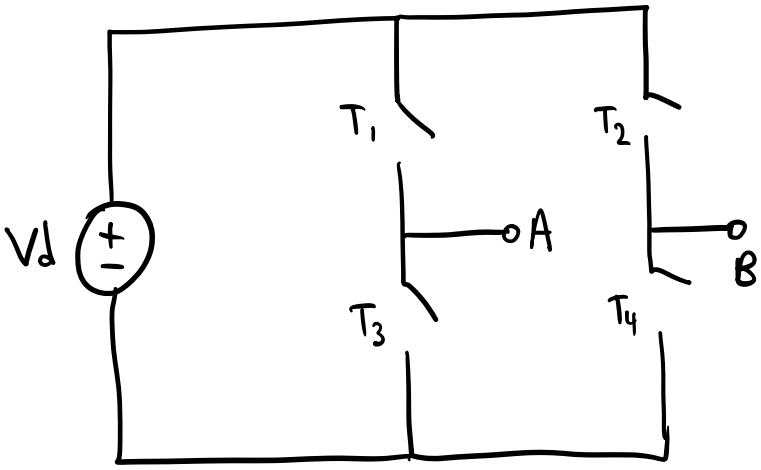

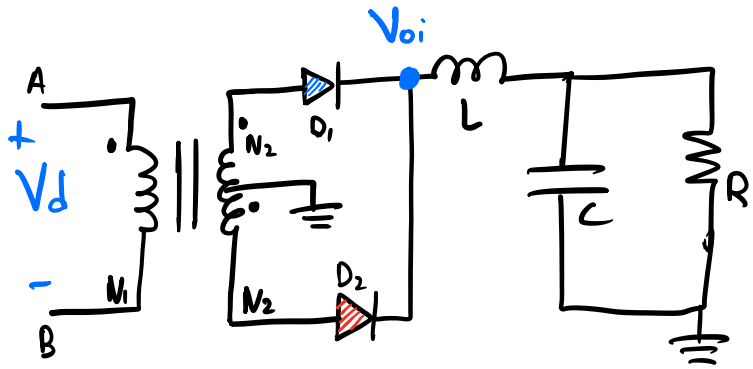

when T_1, T_2 or T_3, T_4 are in ON state

↳
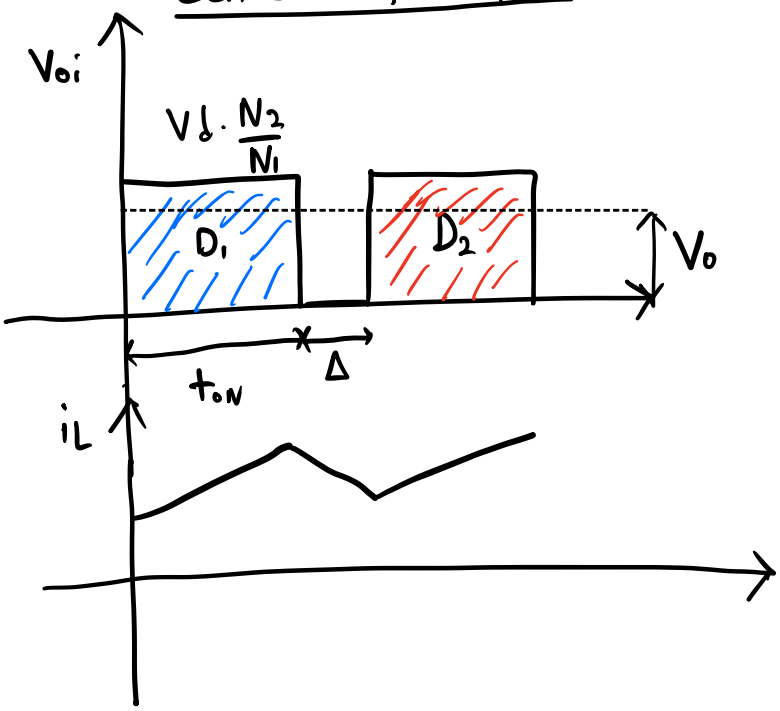
Center Tap Output